

## PASSIVE LOSSLESS SNUBBERS FOR HIGH FREQUENCY PWM CONVERTERS

Sam Ben-Yaakov and Gregory Ivensky

Power Electronics Laboratory  
Department of Electrical and Computer Engineering  
Ben-Gurion University of the Negev

P. O. Box 653, Beer-Sheva 84105, ISRAEL  
Tel: +972-7-646-1561; Fax: +972-7-647-2949

Email: [sby@ee.bgu.ac.il](mailto:sby@ee.bgu.ac.il)

March 1999

## OUTLINE

### Chapter 1. Introduction

1. Seminar objectives
2. Hard versus soft switching
3. Diode reverse recovery
4. IGBT behavior under hard switching
5. Why soft switching?
6. Soft switching terminology
7. Soft switching by passive lossless snubbers
8. Simulation tools

### Chapter 2. Passive lossless snubbers perspective

1. Passive lossless snubber approaches
2. Snubbers evolution
3. The switched inductor (SIM) model
4. Basic switching cell of common PWM converters
5. Fundamental principles
6. Practical aspects

### Chapter 3. Basics of resonant networks

1. Reset of resonant elements
2. Resonant networks - the vehicle of snubbing and energy circulation
3. Basic resonant network parameters
4. Ideal LC-network with ideal diode fed by a voltage source  $V_s$
5. Some trivial cases and practical aspects
6. Resonant inductor design

## Chapter 4. Switch turn-off lossless snubbers

1. The 'one way' capacitor. Versions 1 and 2 (SNB1 & SNB2)
2. Switch turn-off lossless snubber (SNB3)
3. Applying snubber SNB3 in a flyback converter
4. Applying snubber SNB3 in a forward converter
5. A switch turn-off lossless snubber for a boost converter (SNB4)

## Chapter 5. Switch turn-on and diode turn-off snubbers

1. Flyback reset snubber. Versions 1 and 2 (SNB5 & SNB6).  
Practical aspects
2. Low stress turn-on snubber (SNB7). Experimental results.  
Implementation in APFC
3. RMS current of the snubber inductor in a boost converter  
implemented in APFC

## Chapter 6. Turn-on and turn-off single switch snubbers

1. Generic LCC 'turn off' & 'turn on' snubber topology
2. Boost converter with LCC snubber: D type 'on' and S type  
'off' (SNB8)
3. Some additional recent turn-on & turn-off passive lossless  
LCC snubbers (SNB9 - SNB12)
4. LCC snubbers with improved reset (SNB13)
5. Boost converter with LLC-type snubber (SNB14)

6. Buck converter with LC-type snubber (SNB15)
7. Turn-on, turn-off and turn-on - turn-off snubbers. Can parasitic elements be used?

## Chapter 7. Rectifier diodes lossless snubbers

1. Phase shifted PWM (PSPWM) converters
2. Residual issues in PSPWM
  - 2.1. Circulating current. Lossless output snubbers SNB16 & SNB17
  - 2.2. Rectifier's diodes reverse recovery. Possible remedy-saturable reactor. Snubber SNB18
3. Experimental PSPWM converter
4. Improved magnetic snubber for rectifier diodes in DC/DC converters (SNB19)

## Chapter 8. Combining snubber and power supply functions

1. Turn-off snubber with energy recovery back to the input or into a local power supply (SNB20)
2. A local power supply with turn off snubber features
3. Application of proposed power supply in a boost APFC

## Conclusions

## References



Chapter 1

INTRODUCTION

## SEMINAR OBJECTIVES

- To demonstrate the use and benefits of passive lossless snubbers in modern high frequency power electronics design.
- Relevant topologies
- Soft switching
- Parasitic effects
- Limitation - pros & cons

## HARD VERSUS SOFT SWITCHING

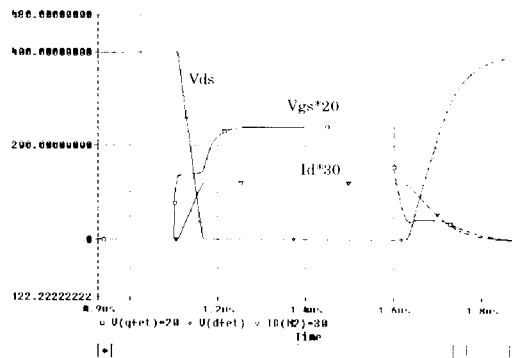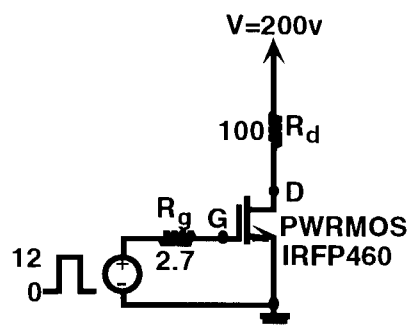


MOSFET switching stage

Switching waveforms  
(simulation)


- Switching losses are proportional to switching frequency



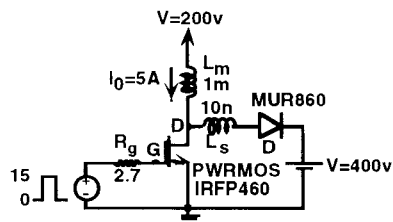Modern simulators include switching behavior




### Hard switched boost stage

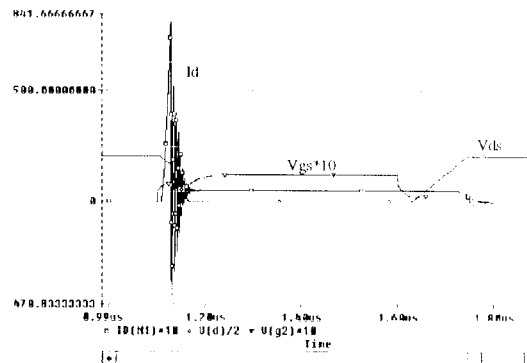

Basic waveforms  
(simulation)


- ☛ Diode reverse current and parasitic oscillations
- ☛ Natural 'softening' at 'turn off'
  - 'Turn On' more troublesome in MOSFETS
  - 'Turn On' & 'Turn off' problematic for IGBT → ZCS

## Diode Reverse Recovery [25, 39]

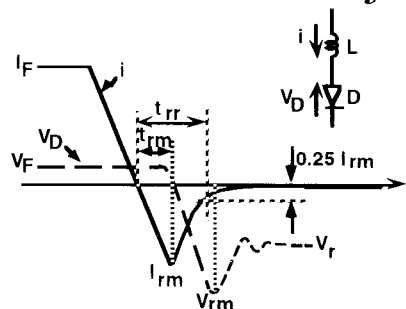


- Low voltage drop on diode in reverse recovery period
- $\frac{di}{dt} = \frac{V}{L}$
- High reverse currents
- High reverse voltage
- Parasitic oscillations
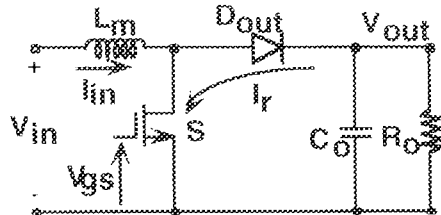
## The reverse recovery problem in Boost topology



- Short circuit against  $V_{out}$
- Occurs in all topologies

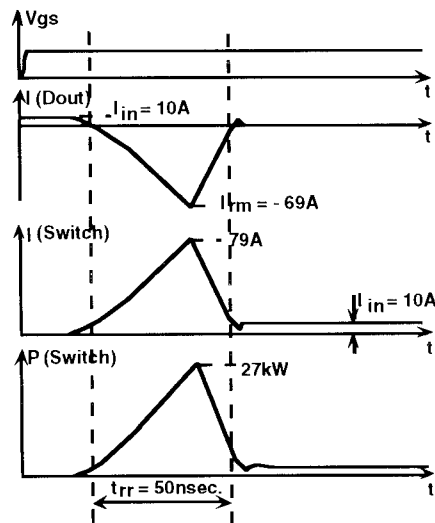
## The reverse recovery problem in Boost topology



- High reverse currents
- High losses
- EMI emission




## Dependence on L

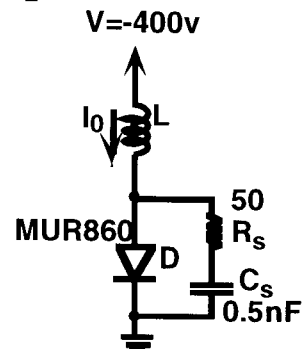

Diode switching circuit - reverse recovery

## Dependence on L - Simulation

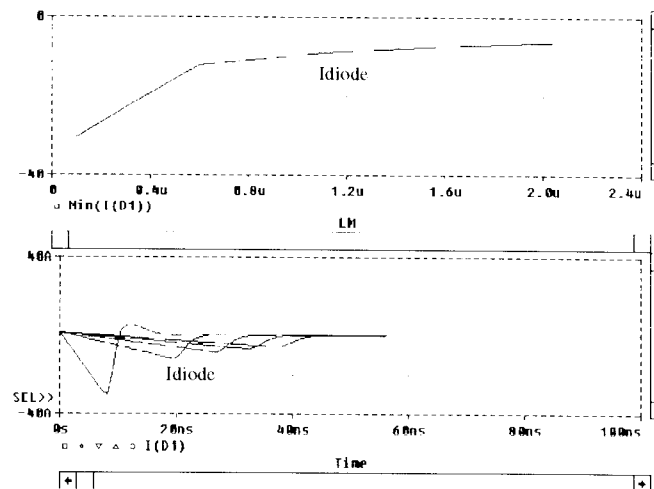

Diode reverse recovery switching waveforms

- 👁 Very high reverse currents
- 👁 A function of series inductance
- 👁 Detrimental effect in isolated and non isolated converters
- 👁 Becomes very important in high switching frequency converters

## Trapped Energy as L becomes Larger


Assume:  $t_{rm}$  constant

Peak reverse current :  $I_{rm} = \frac{V}{L} t_{rm}$

Trapped energy  $E = \frac{1}{2} (I_{rm})^2 L = \frac{(V t_{rm})^2}{2L}$


- Trapped energy decreases as L becomes larger
- Adding inductance ---> Advantageous

## Center Tap Rectifier

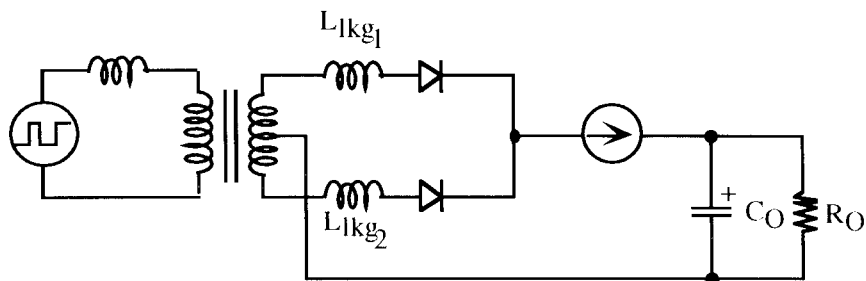

Leakage inductance at secondary

16N6410 P.1 Ape 1, 1987

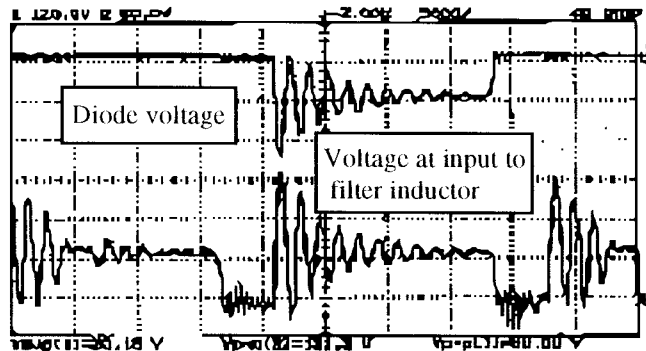


Experimental waveforms (no diode snubber)

- Greatly influenced by transformer leakage
- Forces the use of high voltage diodes


## IGBT BEHAVIOR UNDER HARD SWITCHING

[5, 16, 20, 21, 38]

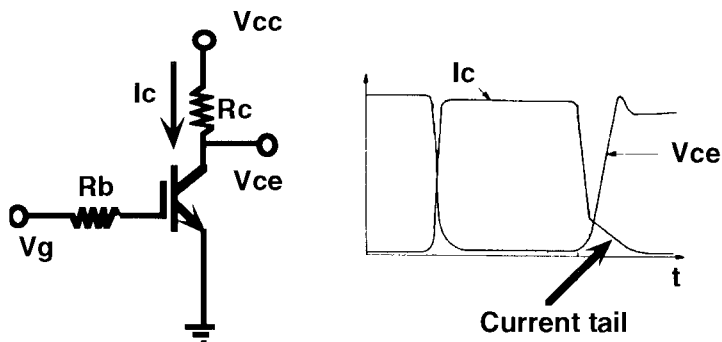


- Current tail due to stored minority carriers
- Switching losses increase linearly with switching frequency
- Switching frequency limit is at about 25 kHz


## Why Soft Switching ?

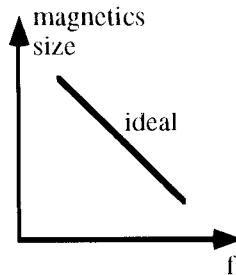

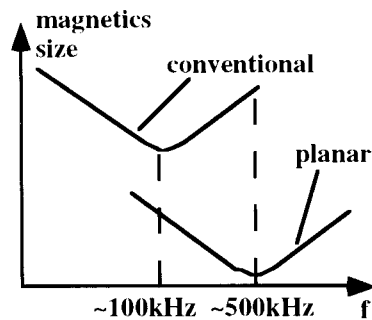Ideal Size/Switching frequency relationships



Practical size realization

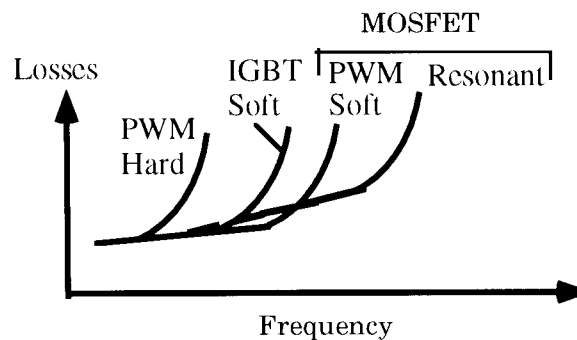

Losses




Conflicting constraints



Soft switching helps to reduce EMI emission ???

## SOFT SWITCHING TERMINOLOGY

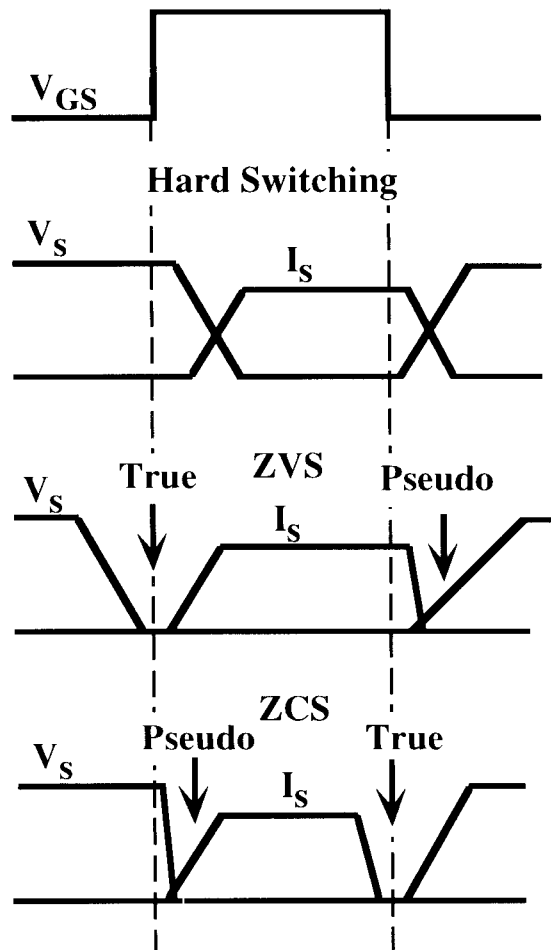


'True' soft switching calls for external active circuitry



'Pseudo' soft switching by lossless snubbers
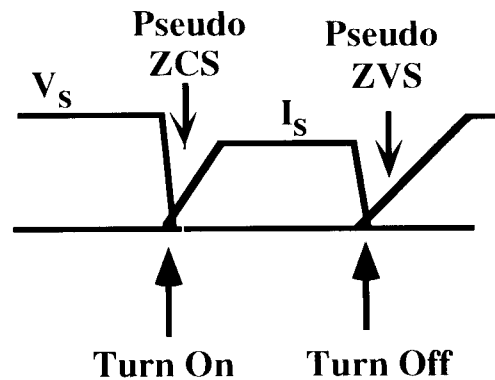
## Soft Switching by Passive Lossless Snubbers



- For MOSFETs -> OK
- For IGBTs -> ZCS at 'turn off' might be more desirable (current tail)
- This can not be accomplished with a Passive Snubber unless operating in constant 'off' time (quasi-resonant)

## SIMULATION TOOLS

- ✓ Modern device models account for switching behavior
  - ☛ Old Models DO NOT account for switching behavior
  - ☛ Difficult to account for PCB parasitics
  - ☛ Simulation of switching losses is still unreliable
  
- ☆ Cycle-by-Cycle simulation
  - ✓ Can faithfully describe the basic switching phenomena
  - ✓ Very useful tool to examine snubber operation
  
- ☆ Average Simulation [3]
  - ✓ Can account for snubber effect on dynamics
  - ✓ Can be used to design the feedback loop

MODEL MUR860 D (IS=783U RS=30M N=4.82 BV=600  
IBV=10U  
+ CJO=330P VJ=.75 M=.333 TT=79.2N)  
\* Motorola 600 Volt 8 Amp 55M us Si Diode 02-24-1994

MODEL DN5406 D (IS=2.68P RS=7.31M N=1.17 BV=900  
IBV=10U  
+ CJO=124P VJ=.6 M=.333 TT=14.4U)  
\* Motorola 600 Volt 3 Amp 15 us Si Diode 11-23-1990


- Parameters can be changed to test various aspects, e.g. TT for reverse recovery

```
.SUBCKT IRF150 10 20 30
*   TERMINALS: D G S
M1 1 2 3 3 DMOS L=1U W=1U
RG 20 2 5.35
RD 10 1 4.3M
RDS 1 3 635K
CGD 4 1 2.75N
RCG 4 1 10MEG
MCG 4 5 2 2 SW L=1U W=1U
ECG 5 2 2 1 1
DGD 2 6 DCGD
MDG 6 7 1 1 SW L=1U W=1U
EDG 7 1 1 2 1
DDS 3 1 DSUB
LS 30 3 7.5N
.MODEL DMOS NMOS (LEVEL=3 VMAX=1.6MEG THETA=265.6M
VTO=3.3
+ KP=9 RS=8.12M IS=2.01P CGSO=2.65M)
.MODEL SW NMOS (LEVEL=3 VTO=0 KP=.45)
.MODEL DCGD D (CJO=2.75N M=.5 VJ=.41)
.MODEL DSUB D (IS=2.01P RS=5.20M VJ=.8 M=.4 CJO=2.60N
TT=720N)
.ENDS
* IR 100 Volt 28 Amp 45M Ohm N-Channel Power MOSFET 11-20-
1990
```

## Chapter 2
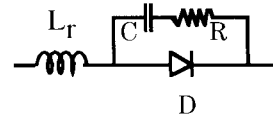
### PASSIVE LOSSLESS SNUBBERS PERSPECTIVE





RC SNUBBERS - Diode RC snubber

👁 LOSSES  $P_{d(\min)} = \left\{ \frac{(2V_o)^2 C}{2} \right\} f_s$ ;  $P_{d(lkg)} = \left\{ \frac{(I_{pkr})^2 L_{lkg}}{2} \right\} f_s$

$P_{d(\min)}$  = minimum losses

$V_o$  = output voltage

$C$  = snubber capacitor

$I_{pkr}$  = peak reverse current

$f_s$  = switching frequency

$L_{lkg}$  = leakage inductance



Resistor dissipation may reach 10's of Watts

## PASSIVE LOSSLESS SNUBBER APPROACHES

1. Snubbing in multiple switch configuration (e.g. half bridge)
2. Auxiliary (dual) switch snubbers [4, 15, 33, 37]
3. Snubbers in single switch configuration (references given below)

No. # 1: Most effective

- Few extra components => economical

No. # 2: Effective but costly

- Calls for extra switches and drives
- Diminishing return

No. # 3: Good compromise

- Only passive elements needed
- Proven to improve efficiency
- Potentially lowers EMI emission

- ☛ This seminar will concentrate on single switch and diode snubbers for PWM converters

## Snubbers Evolution


- SCR (1): RC snubbers - high losses
- SCR (2): Lossless Snubbers - help to turn off devices
- PWM (1): RC Snubbers - high losses
- PWM (2): Quasi Resonant - high stresses and conduction losses
- PWM (3): Auxiliary Switch - complex
- PWM (4): Lossless Snubbers - optimal (as of now)




Passive Lossless Snubbers are comparable in performance to the Dual Switch approaches but are less expensive !

## The Switched Inductor (SIM) Model
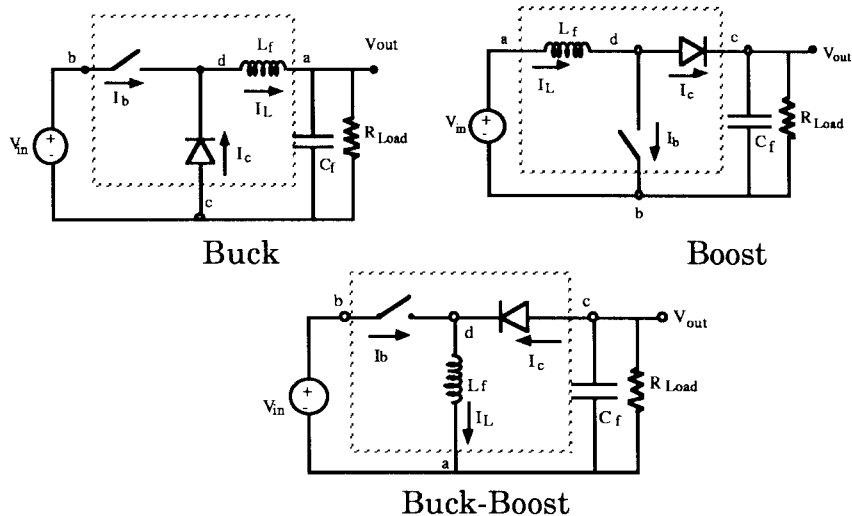
### BASIC SWITCHING CELL OF COMMON PWM CONVERTERS




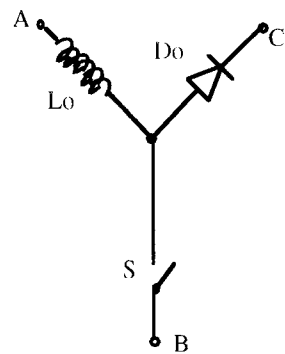
BASIC SWITCHING CELL OF COMMON PWM CONVERTERS



Topology	$V_{in}$	$V_o$	Topology	$V_{AB}$	$V_{CB}$
Buck	$V_{CB}$	$V_{CA}$	Buck	$V_{in}-V_o$	$V_{in}$
Boost	$V_{AB}$	$V_{CB}$	Boost	$V_{in}$	$V_o$
Buck-Boost	$V_{AB}$	$-V_{CA}$	Buck-Boost	$V_{in}$	$V_{in}+V_o$


Fundamental Principles

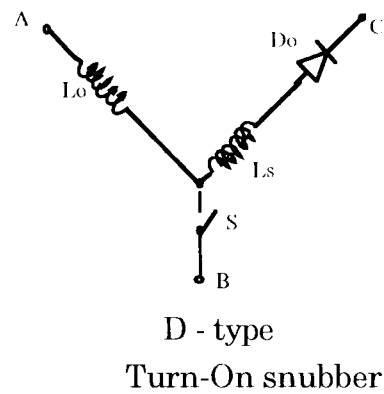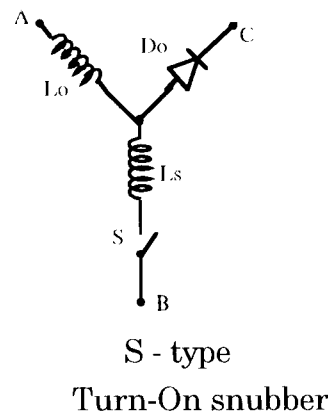1. Controlling  $\frac{dI}{dt}$  at 'Turn On' -> Pseudo ZCS




## Fundamental Principles

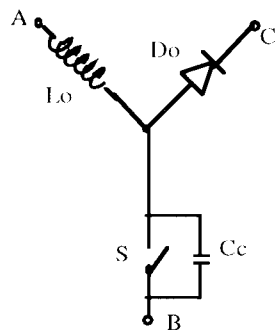2. Controlling  $\frac{dV}{dt}$  at 'Turn Off' -> Pseudo ZVS




S - type

Turn-Off snubber

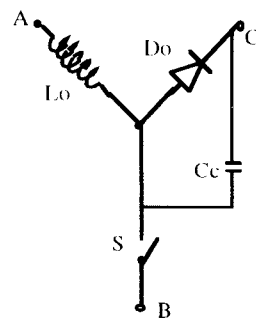

D - type

Turn-Off snubber

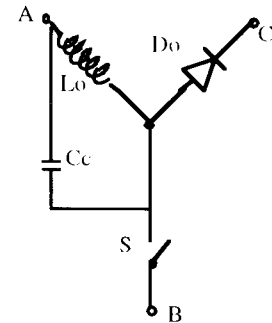

L - type

Turn-Off snubber



The major objective: to circulate the trapped energy

- In a lossless manner
- Without increasing the switch and diode stresses
- As quickly as possible ( $D_{on}$  &  $D_{off}$  limitations)
- Without generating new parasitic effects (of extra components)
- Inexpensive to implement




Use the followings as check points for comparison

$I_{pk}(\text{switch})$

$V_{max}(\text{switch})$

$V_{max}(\text{diode})$


## General Observation

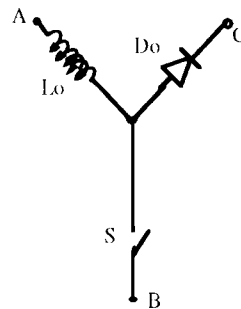


Snubber solution is independent of (PWM) topology if confined to the 'A-B-C' domain

## Practical Aspects (1)

Snubber inductor rms current:

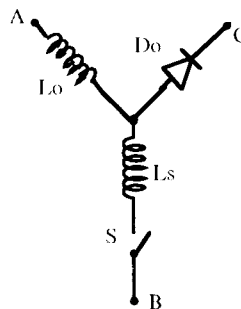

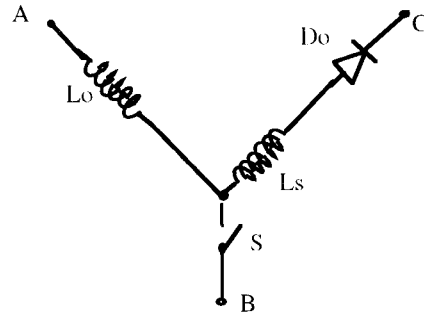
- Snubber inductor carries switch plus reverse recovery currents



- Snubber inductor carries diode plus reverse recovery currents

## Practical Aspects (2)

Stirring capacitor's ripple current

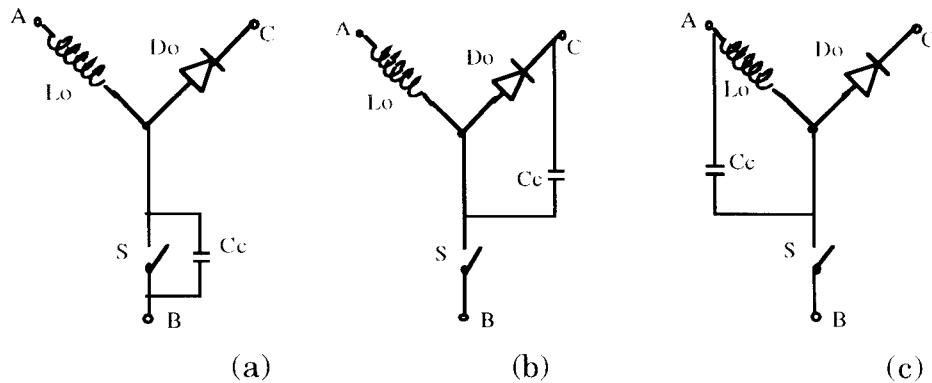

- (a) Ripple stirred to 'ground' - in Boost topology
- (b) Ripple stirred to output - in Boost topology
- (c) Ripple stirred to input - in Boost topology

## Chapter 3

### BASICS OF RESONANT NETWORKS

## Reset of Resonant Elements

At steady-state:

- Volt-Sec of resonant inductor over switching cycle must be zero

$$\int_{T_s} V_{L_r} dt = 0$$

- Ampere- Sec of resonant capacitor over switching cycle must be zero

$$\int_{T_s} I_{C_r} dt = 0$$

- Sufficient time must be available for reset
  - This will cause restriction on duty cycle min & max


## Resonant Networks

-the vehicle of Snubbing and Energy Circulation

- Energy circulation in passive lossless snubbers is made possible by lossless energy exchange of reactive elements (i.e. C, L)
- When the exchange is between L & C one deals with resonant phenomena




## Basic Resonant Network Parameters

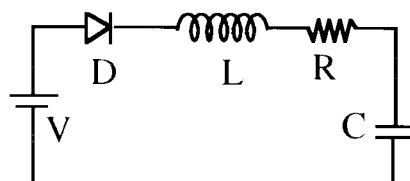

- Typical equivalent circuit of a lossless snubber
- Series resonance
- R is normally small (to make the snubber "lossless")
- May or may not include diode
- Peak current equal or higher than main currents
- Resonant frequency need to be shorter than switching frequency


## Basic Resonant Network Parameters

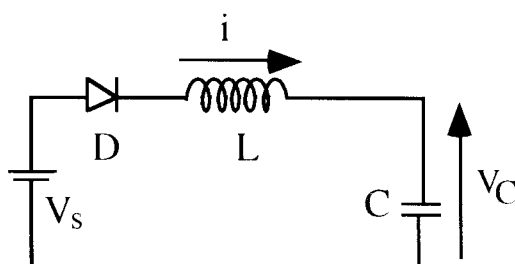

- Resonant frequency:  $f_r = \frac{1}{2\pi\sqrt{LC}}$ ;  $\omega_r = \frac{1}{\sqrt{LC}}$ ;  $T_r = \frac{2\pi}{\omega_r}$
- Characteristic impedance:  $Z_r = \sqrt{\frac{L}{C}}$

Ideal LC-network with ideal diode fed by a voltage source  $V_s$

$$i(0) = I_0 \quad v_C(0) = V_{C0}$$

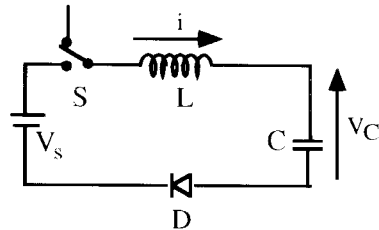

$$i = \frac{V_s - V_{C0}}{Z_r} \sin(\omega_r t) + I_0 \cos(\omega_r t)$$


$$v_C = (V_s - V_{C0})[1 - \cos(\omega_r t)] + I_0 Z_r \sin(\omega_r t) + V_{C0}$$

$$V_{Cp} = (V_s - V_{C0})[1 - \cos \psi] + I_0 Z_r \sin \psi + V_{C0}$$

$$\psi = \tan^{-1}\left(-\frac{I_0 Z_r}{V_s - V_{C0}}\right) + \pi \quad \psi < \pi$$


If  $V_{C0} = 0$  and  $I_0 = 0$   $\psi = \pi$  and  $V_{Cp} = 2 V_s$

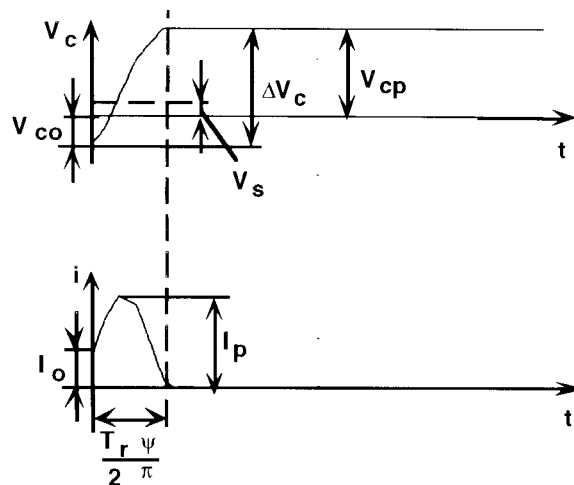If  $V_{C0} < 0$  and  $I_0 = 0$   $\psi = \pi$  and  $V_{Cp} > 2 V_s$



## SOME TRIVIAL CASES


- Linear inductor discharge

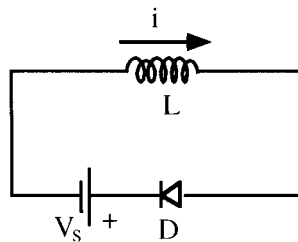

$$\frac{dI_L}{dt} = \frac{V_s}{L}; \quad i_L = I_L(0) - \frac{V_s}{L} t$$

✌ Large capacitor acts as  $V_s$


- Linear capacitor discharge

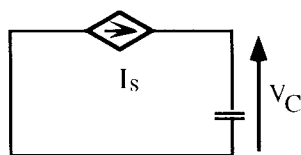


$$\frac{dV_C}{dt} = \frac{I_s}{C}; \quad v_C = V_C(0) + \frac{I_s}{C} t$$

✌ Large inductor acts as  $I_s$

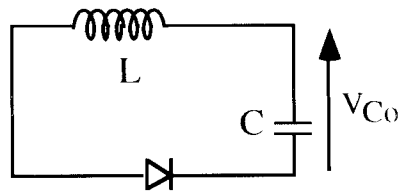- Capacitor voltage reversal  $i(0)=0$   $v_C(0)=V_{C0}$



Beginning

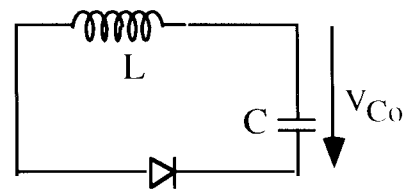


End


## Practical Aspects (3)

### Practical Snubber Components

- Reverse recovery of snubber diodes

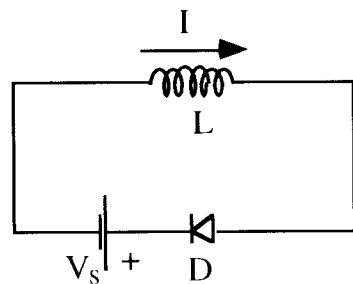

Before reset

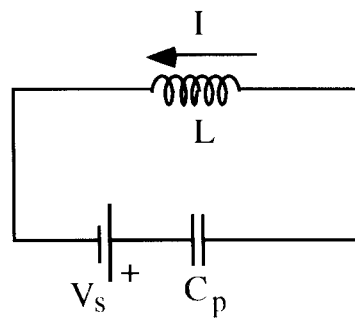

Diode snapped



Parasitic oscillations



Remedy -> Saturable Reactor

## Practical Aspects (4)


### Practical Snubber Components

- ESR of resonant Capacitor

👁 High losses, high temperature

✓ Remedy -> Low ESR capacitors:  
Polypropylene  
Mica (the best !!)

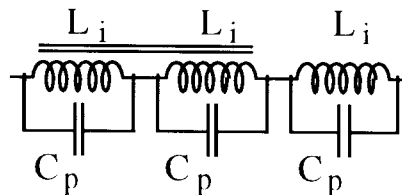- Interwinding capacitance of resonant inductor



👁 Parasitic oscillations , high losses, EMI emission

✓ Remedy -> Careful design, toroidal configuration,  
good coupling between windings

- Printed circuit layout



Parasitic oscillations , high losses, EMI emission



Remedy -> Careful design

## Resonant Inductor Design

Typical characteristics

- Low inductance ; Typical range 3μH - 10μH
- High current ; Typical range 1A -30A

Some basic relationships:

$$B_{\max} = \frac{L I_{pk}}{n A_e}; \quad L = \frac{n^2 \mu_o \mu_r A_e}{l_e};$$

$$\Delta B = \frac{\int V_L dt}{n A_e}$$

L - inductance (H)

I<sub>pk</sub> - peak inductor current (A)

V<sub>L</sub> - voltage across inductor (V)

t - time (Sec)

n - number of turns

B<sub>max</sub> - limit of magnetic flux density (T)

A<sub>e</sub> - effective core area (m<sup>2</sup>)

l<sub>e</sub> - effective magnetic length (m)

μ<sub>o</sub> - permeability (1.25 10<sup>-6</sup> H/m)

μ<sub>r</sub> - relative permeability


From above

$$\frac{I_{pk}}{L} = \frac{1}{L} \frac{B_{max} l_e}{n \mu_o \mu_r}$$

For high  $\frac{I_{pk}}{L}$  ratios:

- Long  $l_e$
- Small number of turns  $n$
- Low relative permeability  $\mu_r$
- Winding window will not be full

## Typical Construction

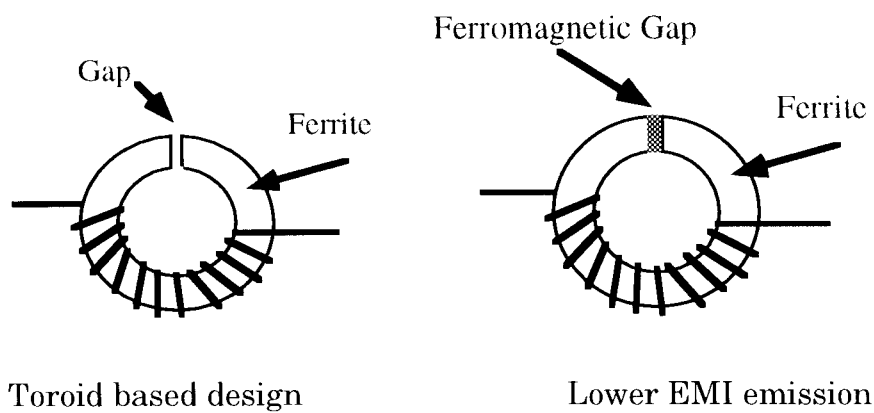

## Suggested Design Procedure

1. Choose  $\Delta B_{\max}$  based of acceptable losses (mW/gr) from ferrite data (losses as a function of  $\Delta B$  and frequency). Use  $f_r$  as an indicator but take into account the short period of snubbing by dividing the data sheet losses by  $(f_r/f_s)$
2. Estimate  $\{V \text{ Sec}\}$  across resonant inductor  $\int V_L dt$  or by an approximation e.g.  $V_L * t_{rr}$
3. Calculate  $nA_e$  from the relationship:

$$nA_e = \frac{\int V_L dt}{\Delta B_{\max}}$$

4. Select wire cross section according to rms current
5. Based on calculated  $nA_e$  and wire size, choose a core for a single layer winding
6. Gap the core for required L value



## Chapter 4

### SWITCH TURN-OFF LOSSLESS SNUBBERS




## SWITCH 'TURN OFF' LOSSLESS SNUBBER (SNB1)

The 'One Way' Capacitor : Version 1 [35]

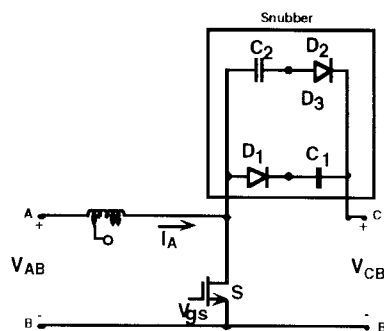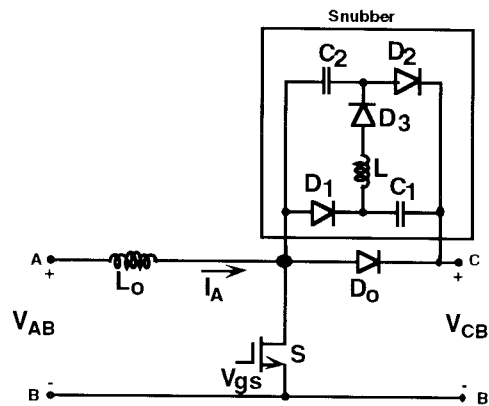

Snubbing

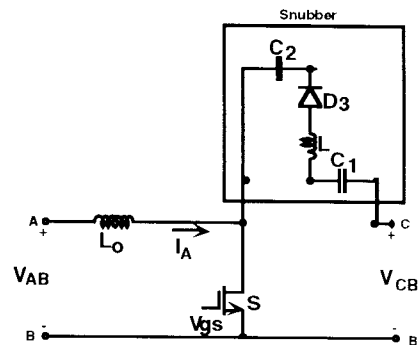


Reset

- Snubber capacitor  $C_1 + C_2$
- Resonant reset (  $C_1 + C_2, L$  )


## General Observations (1)

### 1. Snubbing

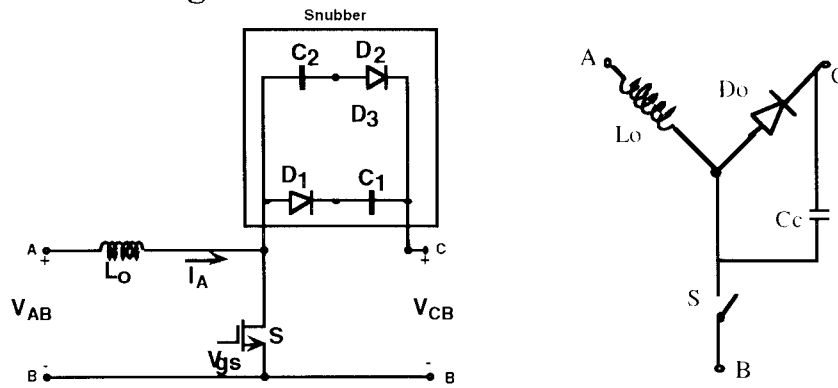

- Prior to 'turn-off',  $C_1$  &  $C_2$  must be charged to  $V_{CB}$


### 2. Reset

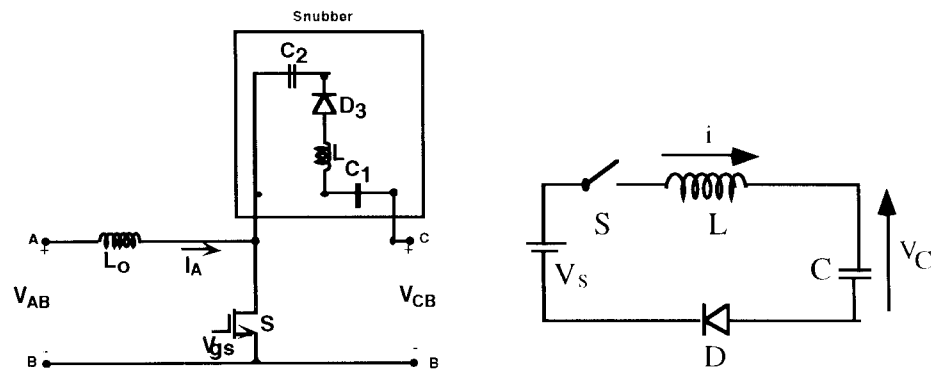


$$V_C = 2 V_{CB}$$

$$\text{if } C_1 = C_2 \rightarrow V_{C1} = V_{C2} = V_{CB}$$

## General Observations (2)

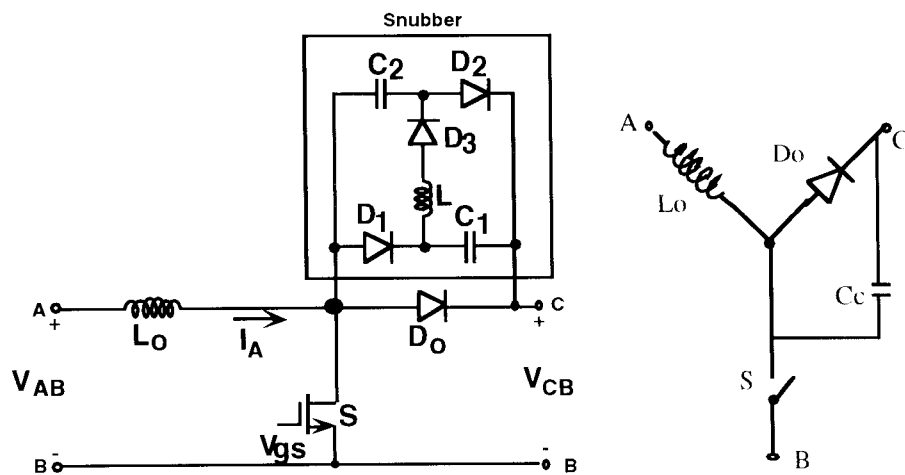

- Topology independent

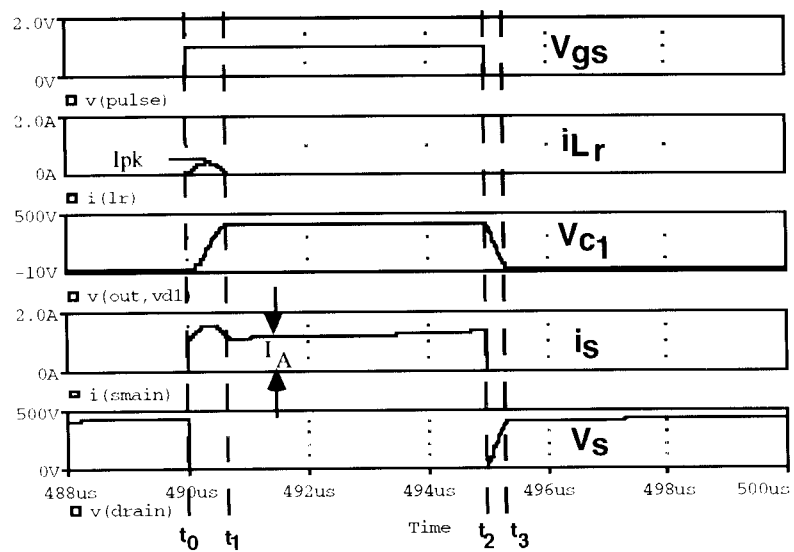

Waveforms of SNB1 (simulation)

Interval  $t_0-t_1$

Assuming:  $C_1=C_2=C$

$$t_1-t_0 = \frac{T_r}{2} = \pi \sqrt{\frac{LC}{2}} ;$$

$$i_L = i_{D3} = I_{pk} \sin(2\pi \frac{t}{T_r})$$

$$I_{pk} = \frac{V_{CB}}{\sqrt{\frac{2L}{C}}} ; \quad i_S = I_A + i_L$$

$$v_{C1} = v_{C2} = 0.5 V_{CB} [1 - \cos(2\pi \frac{t}{T_r})]$$

Interval  $t_1-t_2$

$$i_S = I_A ; \quad i_{D0} = i_{D1} = i_{D2} = i_{D3} = 0$$

Interval  $t_2-t_3$

$$v_{C1} = v_{C2} = V_{CB} \frac{I_A}{2C} (t-t_2) ;$$

$$v_{C1}(t_3) = v_{C2}(t_3) = 0$$

$$\text{from which: } t_3-t_2 = \frac{2CV_{CB}}{I_A} \quad \text{and hence } (\frac{dv_S}{dt})_{t_2-t_3} = \frac{I_A}{2C}$$

$$\text{Interval } t_3-(t_0+T_s) \quad i_{D0} = I_A ; i_S = i_{D1} = i_{D2} = i_{D3} = 0$$

Typical Design

Given:  $V_{CB}$ ,  $I_A$ ,  $(\frac{dv_S}{dt})_{t_2-t_3}$ ,  $D_{min}$ ,  $D_{max}$

$$1. \quad C \geq \frac{I_A}{2(\frac{dv_S}{dt})_{t_2-t_3}} ; \quad 2. \quad t_{2-3} = \frac{2CV_{CB}}{I_A}$$

$$3. \quad f_s \leq \frac{1-D_{max}}{t_{2-3}} \quad 4. \quad L = \frac{2(\frac{D_{min}}{f_s})^2}{\pi^2 C}$$

$$5. \quad I_{pk} = \frac{V_{CB}}{\sqrt{\frac{2L}{C}}} \Rightarrow \quad \frac{I_{pk}}{I_A} = \frac{\pi V_{CB}}{t_{on \min} (\frac{dv_S}{dt})_{t_2-t_3}}$$

The diodes  $D_1$  &  $D_2$  must be very fast and have a very low storage charge.

Example:

Assuming:  $f_s \approx 100\text{KHz}$ ;  $t_{\text{on min}} \approx 1\mu\text{S}$ ;  $(\frac{dv_S}{dt})_{t_2-t_3} \approx 400\text{V}/\mu\text{S}$

$$\frac{I_{\text{pk}}}{I_A} = 0.78$$

✓ Check points


$$I_{\text{pk}}(\text{switch}) = I_A + \frac{I_A \pi V_{\text{CB}}}{t_{\text{on min}} (\frac{dv_S}{dt})_{t_2-t_3}}$$

$V_{\text{max}}(\text{switch}) = \text{Same as original}$

$V_{\text{max}}(\text{diode}) = \text{Same as original}$
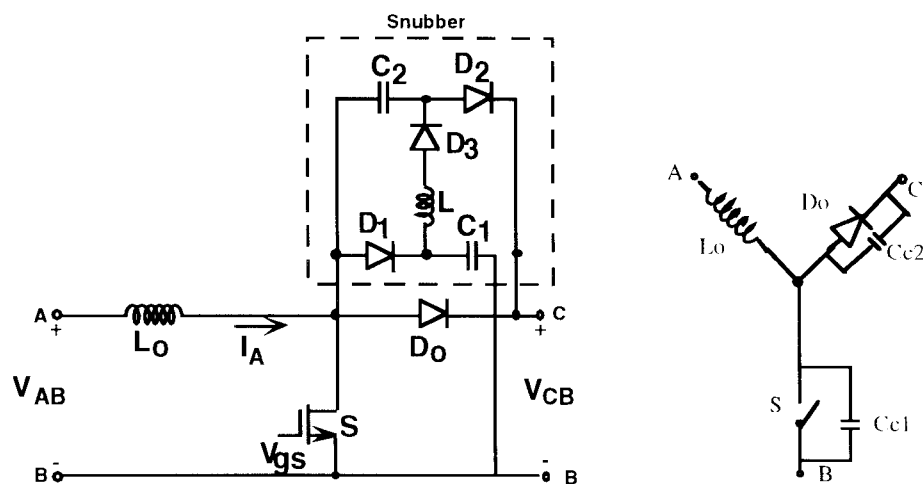
## SWITCH 'TURN OFF' LOSSLESS SNUBBER



The 'One Way' Capacitor : Version 2 (SNB2) [35]





- Identical to Version 1 (normally drawn differently)

SWITCH 'TURN OFF' LOSSLESS SNUBBER (SNB3) [35]

Reset to Input

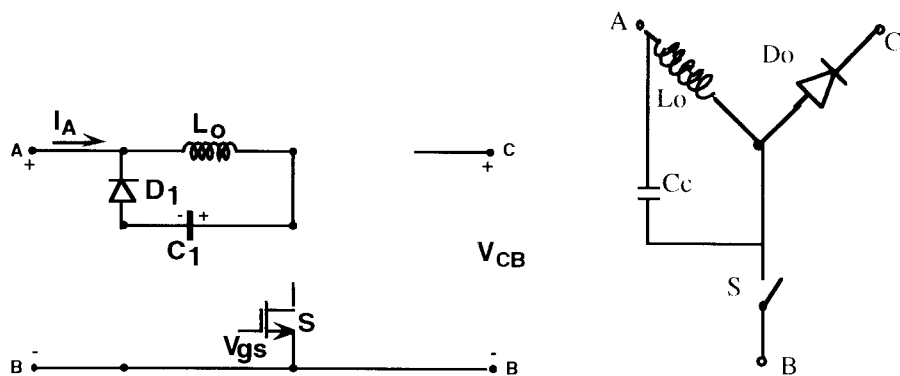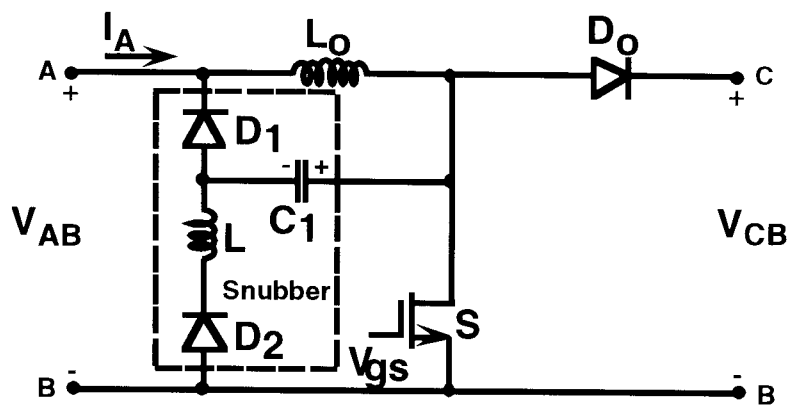

Snubbing

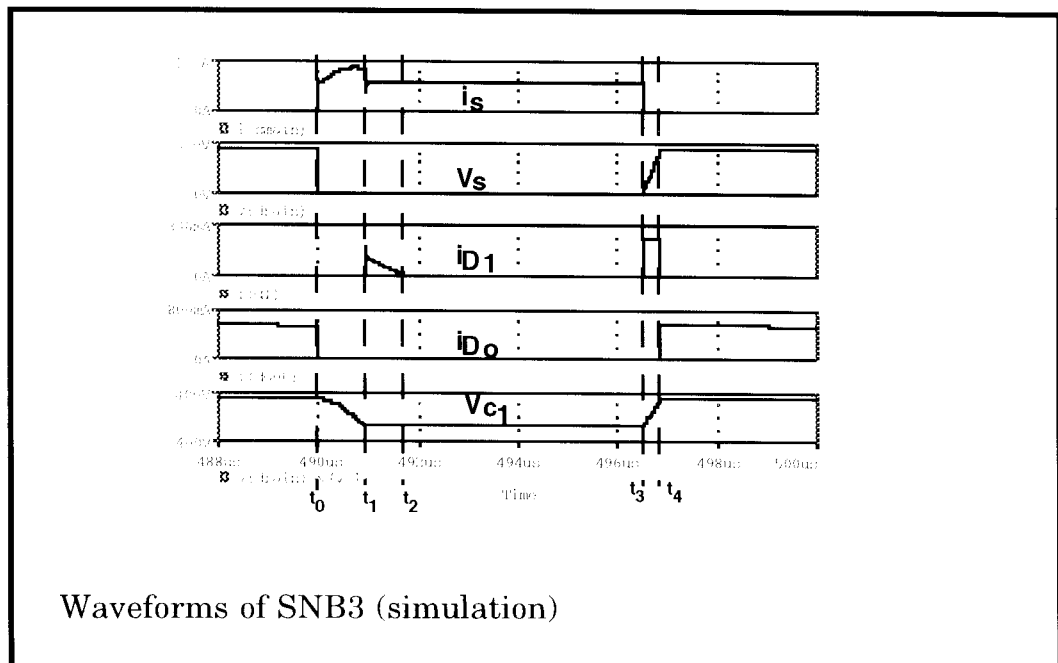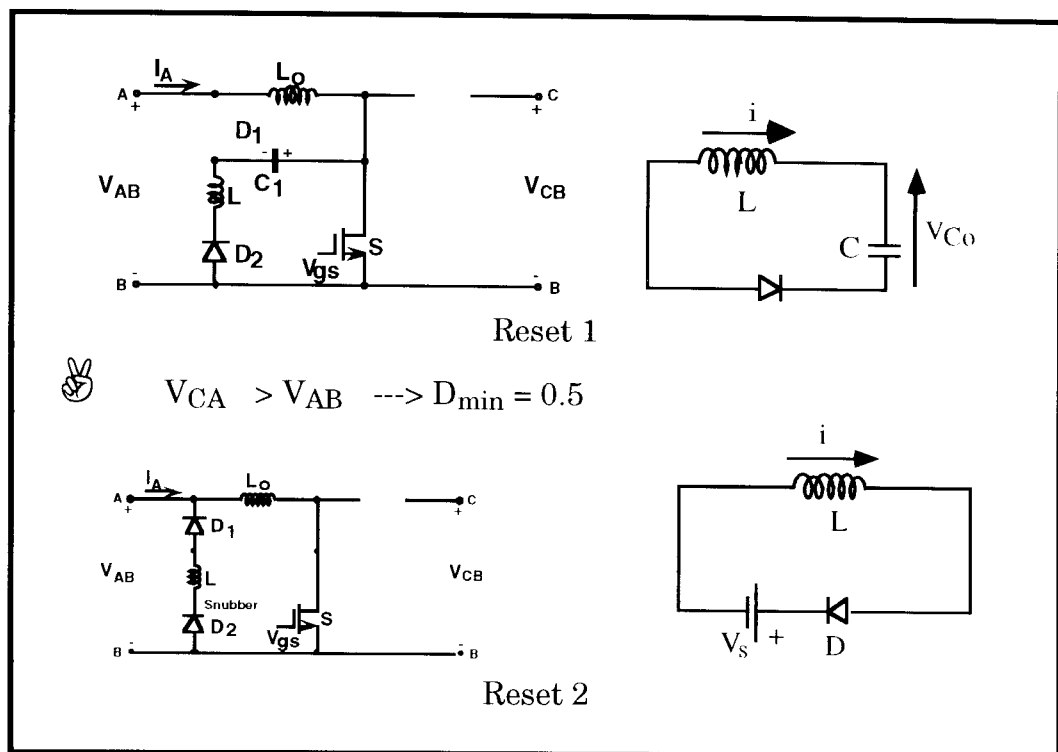

Case  $V_{CB}-V_{AB} > V_{AB}$ , i.e.  $V_{CB} > 2V_{AB}$

Interval  $t_0-t_1$   $i_L=i_{D2}=I_{pk}\sin(2\pi\frac{t}{T_r})$

where

$$T_r=2\pi\sqrt{LC_1}$$

$$I_{pk}=\frac{V_{CB}-V_{AB}}{\sqrt{\frac{L}{C_1}}}$$

$$i_S=I_A+i_L$$

$$v_{C1}=(V_{CB}-V_{AB})\cos(2\pi\frac{t}{T_r})$$

$t_1$  is found from the condition:

$$(v_{C1})_{t_1}=-V_{AB}$$

$$t_1=\frac{T_r}{2\pi}\cos^{-1}\left(\frac{V_{AB}}{V_{CB}-V_{AB}}\right)$$

Interval  $t_1-t_2$   $i_L=i_{D1}=i_{D2}=I_{pk}\sin(2\pi\frac{t_1}{T_r})-\frac{V_{AB}}{L}(t-t_1)$

$t_2-t_1$  is found from the condition:  $(i_L)_{t_2}=0$

$$t_2-t_1=\frac{I_{pk}L\sin(2\pi\frac{t_1}{T_r})}{V_{AB}}$$

$$i_A=I_{A0}-i_L$$

Interval  $t_2-t_3$   $i_S=I_A$  ;  $i_{D0}=i_{D1}=i_{D2}=0$

Interval  $t_3-t_4$   $i_S=i_{D0}=i_{D2}=0$

$$v_{C1}=-V_{AB}+\frac{I_{A0}}{C_1}(t-t_3)$$

$t_4-t_3$  is found from the condition:

$$(v_{C1})_{t_4}=V_{CB}-V_{AB}$$

$$t_4-t_3=\frac{C_1V_{CB}}{I_{A0}}$$

Interval  $t_4-(t_0+T_s)$   $i_S=i_{D1}=i_{D2}=0$  ;  $i_{D0}=I_{A0}$



## Typical Design

Given:  $V_{CB}$ ,  $I_{Lo}$ ,  $(\frac{dv_S}{dt})_{t_3-t_4}$ ,  $D_{min} \geq 0.5$ ,  $D_{max}$

$$1. C_1 \leq \frac{I_{Lo}}{(\frac{dv_S}{dt})_{t_3-t_4}} ; \quad 2. t_{3-4} = \frac{C_1 V_{CB}}{I_{Lo}} ; \quad 3. f_s \leq \frac{1-D_{max}}{t_{3-4}} ;$$

$$4. L \approx \frac{(\frac{D_{min}}{f_s})^2}{\pi^2 C_1} \quad (\text{assumption: } i_L \text{ has a sine waveform not only during interval } t_0-t_1 \text{ but also during } t_1-t_2)$$

$$5. I_{pk} = \frac{V_{CB} D_{max}}{\sqrt{\frac{L}{C_1}}}$$

✓ Check points

$$I_{pk}(\text{switch}) = I_{Lo} + \frac{\pi D_{max} V_{CB} I_{Lo}}{t_{on \min} (\frac{dv_S}{dt})_{t_3-t_4}} \quad (\text{no free lunch})$$


$V_{pk}(\text{switch}) = \text{Same as original}$

$V_{pk}(\text{diode}) = \text{Same as original}$


$$\text{Limitation: } V_{AB} \leq \frac{V_{CB}}{2}$$

In Boost Power Factor, hard switching when  $V_{in} \geq \frac{V_o}{2}$
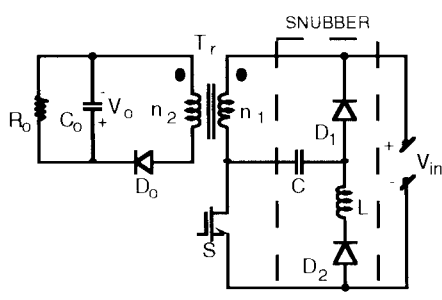
## Applying snubber SNB3 in a flyback converter [6, 26, 28]




Basic topology

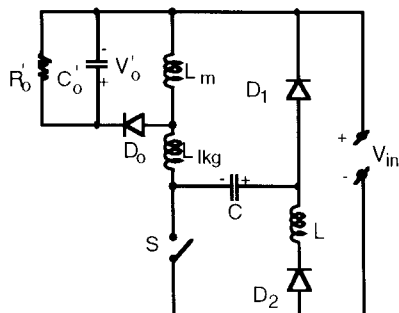


Equivalent circuit

- $L_m$  - output transformer magnetizing inductance
- $L_{lkg}$  - output transformer leakage inductance
- $C$  - snubber capacitance
- $L$  - snubber inductance
- $R_0'$  - reflected load resistance
- $C_0'$  - reflected capacitance of the output filter
- $S$  - switching transistor
- $D_0$  - output diode
- $D_1, D_2$  - snubber diodes
- $V_{in}$  - input voltage
- $V_0'$  - reflected output voltage

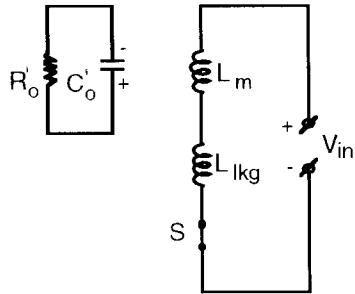
## Equivalent circuit at different time intervals



1. ON

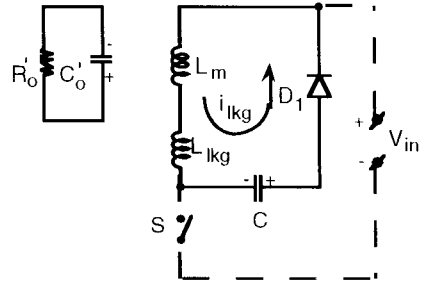

2. Snubbing 1

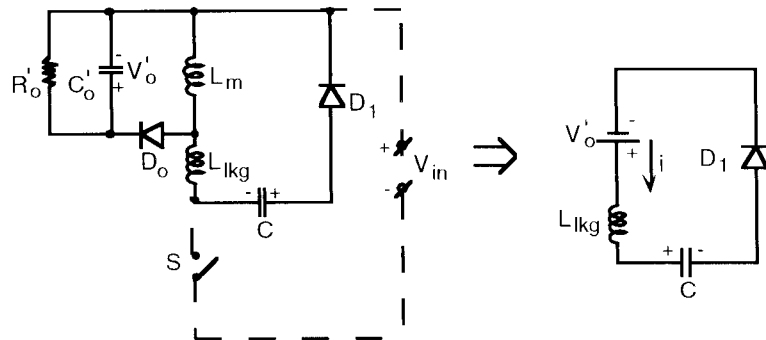


3. Snubbing 2



## General Observation
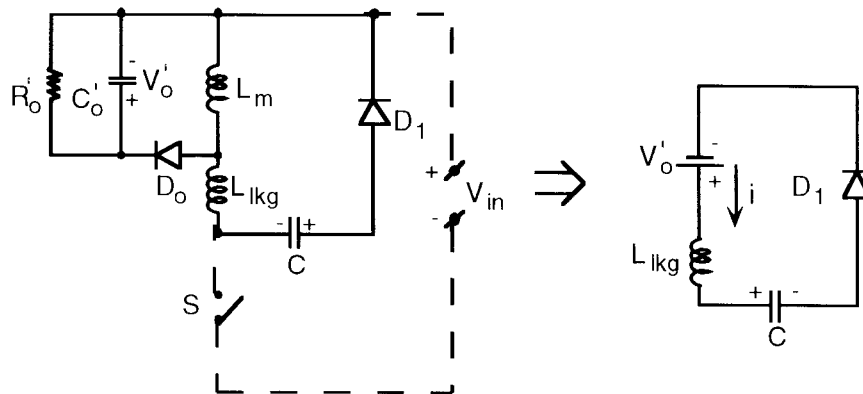
### 1. Switch maximum voltage ( $V_{s\text{ pk}}$ )



Capacitor's initial voltage  $\rightarrow V_C(0) = V_{in}$

Capacitor maximum voltage  $\rightarrow V_{Cpk} > 2 V_o' + V_{in}$

{ additional voltage contributed by energy removed from  $L_{lkg}$  }

Switch maximum voltage  $\rightarrow V_{s\text{ pk}} > 2 (V_{in} + V_o')$


#### Advantages

- The snubber is simple and inexpensive [28]
- The operational duty cycle range is wider than in the case when this snubber is used in a boost converter

#### Disadvantage


- High voltage stress on the transistor  $V_{s\text{ pk}}$

## Reverse recovery of snubber diode

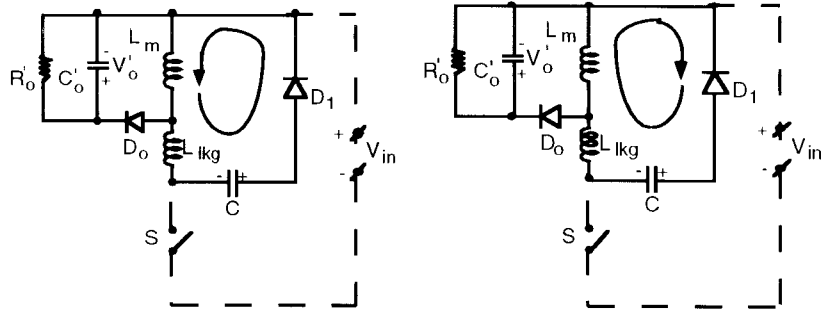

Resonant reset


Reverse recovery

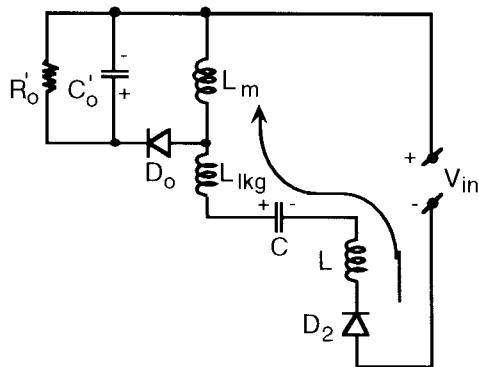

Linear discharge

- Loss of  $C$  charge
- $C$  must retain a voltage of at least  $V_{in}$  for proper ZVS at 'turn-off'
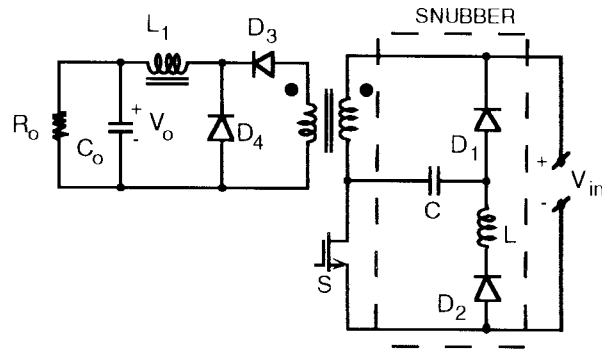
## Applying snubber SNB3 in a forward converter [40]



Same advantages and disadvantages as for the flyback converter case:

- the snubber is simple and inexpensive
- high voltage stress  $V_{s\text{ pk}}$  on transistor.

$$V_{s\text{ pk}} = V_{in} + V_{Cp}$$

where

$$V_{Cp} = \sqrt{\frac{L_m I_m^2 + L_{lkg} I_{Sp}^2}{C}}$$

$L_m$  - magnetizing inductance of the transformer

$L_{lkg}$  - primary leakage inductance

$I_m$  - magnetizing current of the transformer


$I_{s\text{ pk}}$  - switch current in the moment when the switch is turned off

Experimental results [40]

1)  $V_{in}=17V$ ;  $P_{out}=17W$ ;  $D=2/3$ ;  $V_{s\text{ pk}}=52V$

2)  $V_{in}=34V$ ;  $P_{out}=36W$ ;  $D=1/3$ ;  $V_{s\text{ pk}}=88V$
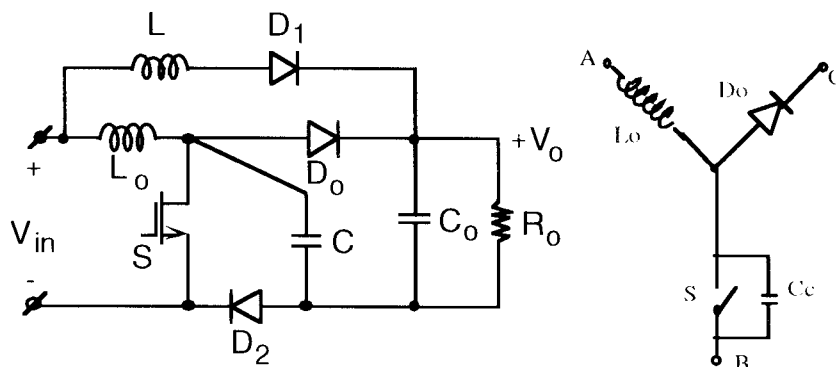
## A switch "turn-off" lossless snubber for a boost converter [30] (SNB4)




Snubber elements:


- L - the resonant inductor
- C - the resonant capacitor
- $D_1, D_2$  - snubber diodes

👁 No common ground !
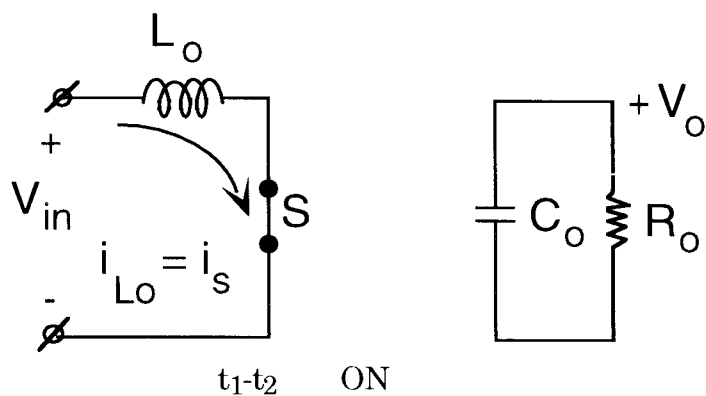
## Equivalent circuits for different time intervals





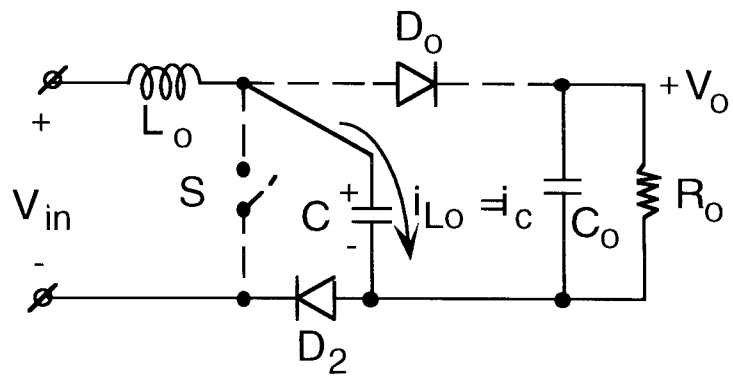


$t_2-t_3$  , snubbing


$$\frac{dv_S}{dt} = \frac{i_{Lo}}{C} \quad \text{ZVS!}$$

$$v_{D_o}(t) = v_C(t) - V_o$$
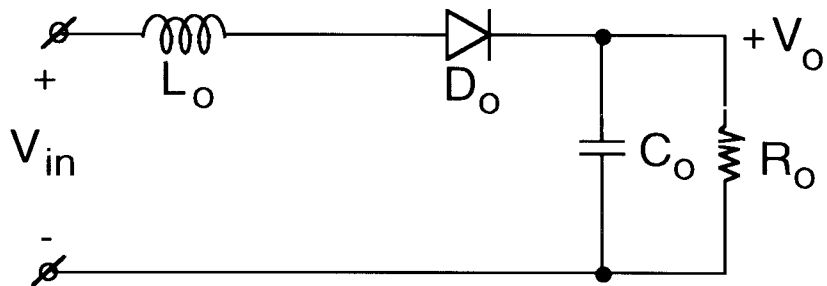
$$v_C(t_3) = V_o \quad v_{D_o}(t_3) = 0$$



$t_3-t_4$  OFF

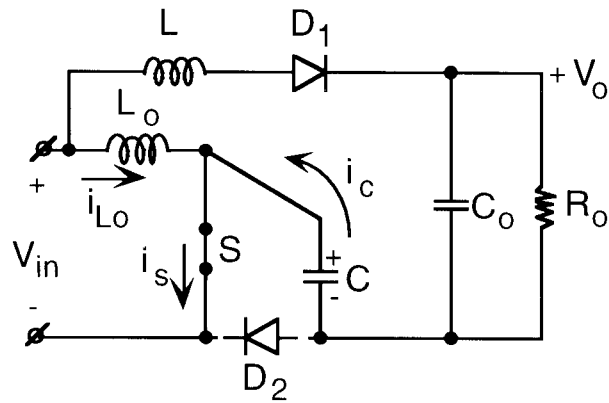


$t_4-t_5$ , reset

$$v_C(t_4) = V_o \quad i_L = i_C = \frac{V_{in}}{Z_r} \sin(\omega_r t) \quad \omega_r = \frac{1}{\sqrt{LC}}$$

$$Z_r = \sqrt{\frac{L}{C}}$$

$$i_S = i_{L0} + i_C \quad I_{Sp} = I_{L0} + \frac{V_{in}}{Z_r}$$

$$v_C(t_5) = v_{D2}(t_5) = 0$$

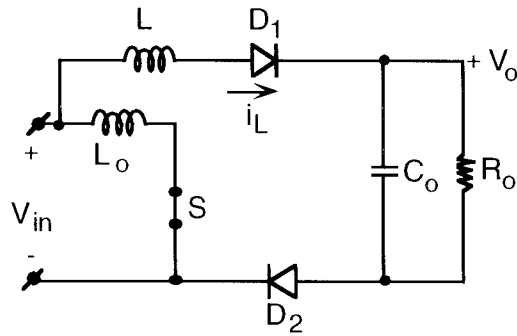

$t_5-t_6$ , linear discharge

$$i_L(t) = i_{D1}(t) = i_L(t_5) - \frac{V_o - V_{in}}{L} (t - t_5)$$

$$i_L(t_6) = i_{D1}(t_6) = 0$$

A switch "turn-off" lossless snubber for a boost converter [30]  
(SNB4)

Advantages

- Soft switching at turn off. Efficiency was reported to increase by 5% to 97% [30] .

Disadvantage

- Reverse recovery problems of diodes  $D_0$ ,  $D_1$ , and  $D_2$
- High current stress of main switch during the interval  $t_4 - t_5$
- No common ground between input and output


Chapter 5

SWITCH TURN-ON AND DIODE TURN-OFF SNUBBERS

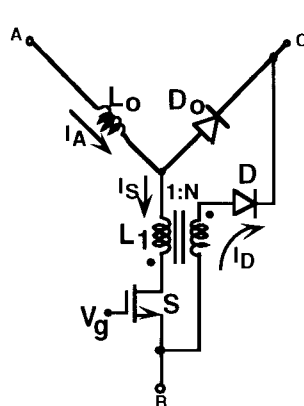
## SWITCH 'TURN ON' AND DIODE 'TURN OFF' SNUBBER

[35,39]



FLYBACK RESET SNUBBER (energy recovery via a catch winding)




Version 1 (SNB5)

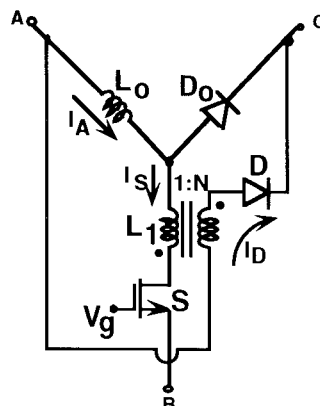

Version 2 (SNB6)

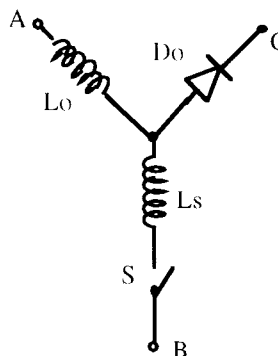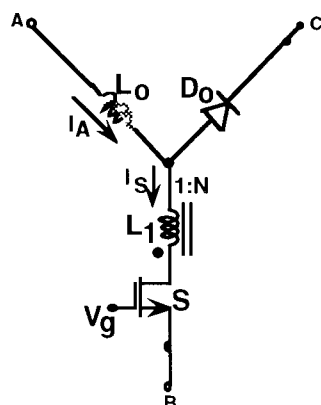


Snubbing

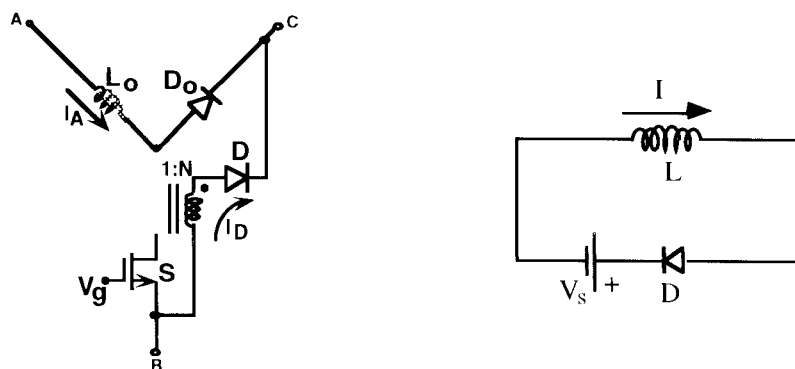

Reset


## Practical Aspects (5)

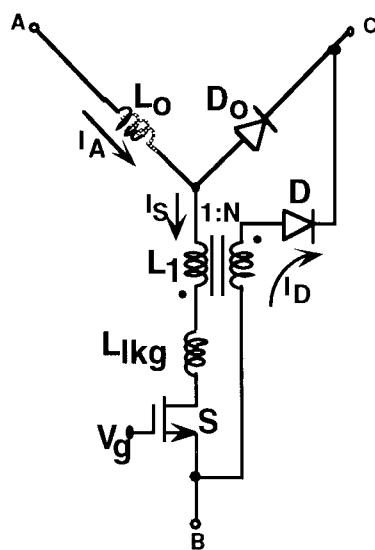

Beware of leakage inductance



Not practical for HF high power levels

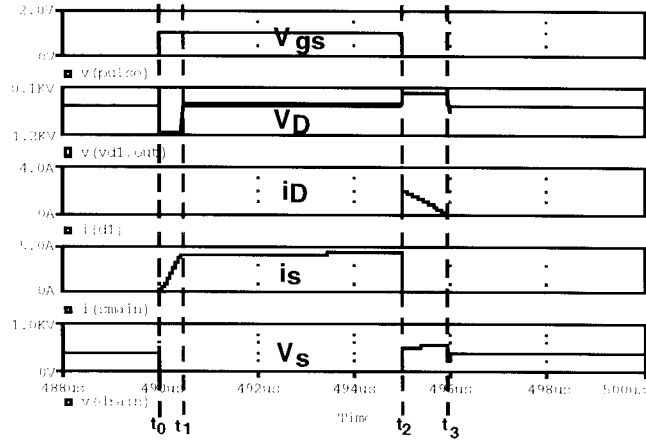

Waveforms of SNB5 (simulation)

Analysis: Version 1 (SNB5)

Interval  $t_0-t_1$  
$$i_s = \frac{V_{CB}t}{L_1}$$

$t_1-t_0$  is found from the condition:  $i_s(t_1)=I_A$

from where

$$t_1-t_0 = \frac{L_1 I_A}{V_{CB}}$$

$$V_{Do \max} = V_{CB}(1+N)$$

Interval  $t_2-t_3$  
$$i_D = \frac{I_A}{N} - \frac{V_{CB}}{N^2 L_1}(t-t_2)$$

$t_3-t_2$  is found from the condition:  $i_D(t_3)=0$

$$t_3-t_2 = \frac{I_A L_1 N}{V_{CB}} ; V_{S \max} = V_{CB}(1+\frac{1}{N})$$

$$t_3-t_2 = \frac{I_A L_1 N}{V_{CB}} ; f_{s \max} = \frac{1-D_{\max}}{t_3-t_2}$$

$$V_{S \max} = V_{CB}(1+\frac{1}{N}) ; V_{Do \max} = V_{CB}(1+N)$$

The lower  $N$ , the shorter is  $t_3-t_2$  and hence the higher is the upper limit of the switching frequency  $f_{s \max}$ . The lower  $N$ , the higher is  $V_{S \max}$ . The voltage across the main diode  $D_o$  is high when  $N$  is high.

A major disadvantage of the converter is the leakage inductance between the primary and secondary of the coupled inductor : it will cause a large voltage spike across the switch. Beware of reverse recovery problems of the auxiliary diode  $D$ .

## FLYBACK RESET SNUBBER Version 1 (SNB5)

### Typical Design

Given:  $V_{CB}$ ,  $I_A$ ,  $(\frac{di_s}{dt})_{t_0-t_1}$ ,  $D_{\min}$ ,  $D_{\max}$

$$1. L_1 \leq \frac{V_{CB}}{(\frac{di_s}{dt})_{t_0-t_1}} ; 2. t_{1-0} = \frac{L_1 I_A}{V_{CB}} ; 3. f_s \leq \frac{D_{\min}}{t_{1-0}}$$

$$4. t_{2-3} \leq \frac{1-D_{\max}}{f_s} ; 5. N = \frac{V_{CB} t_{2-3}}{L_1 I_A} ; 6. V_{S \max} = V_{CB} (1 + \frac{1}{N})$$

$$7. V_{D_o \max} = V_{CB} (1 + N)$$



### ✓ Check points

$$I_{pk}(\text{switch}) = I_A$$

$$V_{\max}(\text{switch}) = V_{CB} (1 + \frac{1}{N}) = V_{CB} \left( 1 + \frac{I_A}{t_{off \min} (\frac{di_s}{dt})_{t_0-t_1}} \right)$$

$$V_{\max}(\text{diode}) = V_{CB} (1 + N) = V_{CB} \left( 1 + \frac{t_{off \min} (\frac{di_s}{dt})_{t_0-t_1}}{I_A} \right)$$
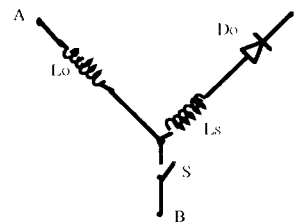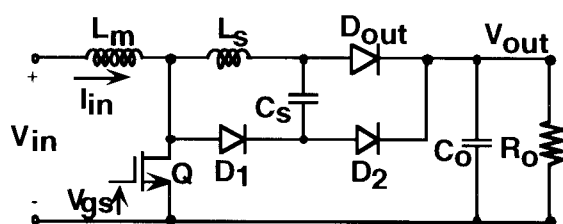
## LOW STRESS 'TURN ON' SNUBBER (SNB7) [17, 24]



Q - Main switch



Dout - Main diode

D1,D2 - Auxiliary diodes

LS, CS - Resonant network


## Basic waveforms of lossless snubber

Interval  $t_0$ - $t_1$

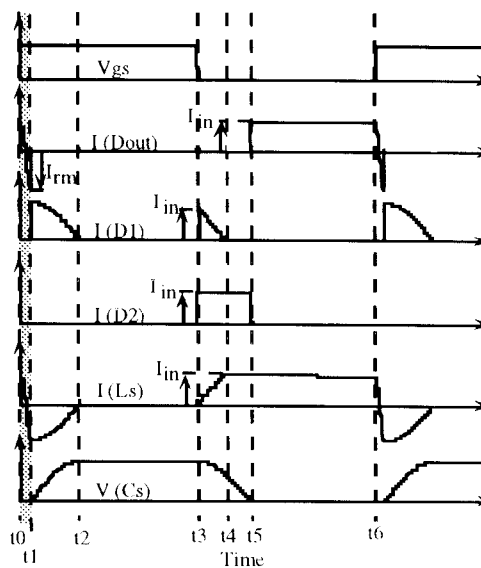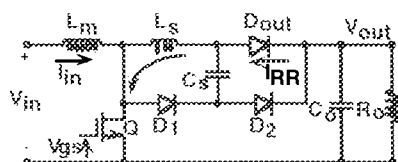






## Interval $t_1$ - $t_2$

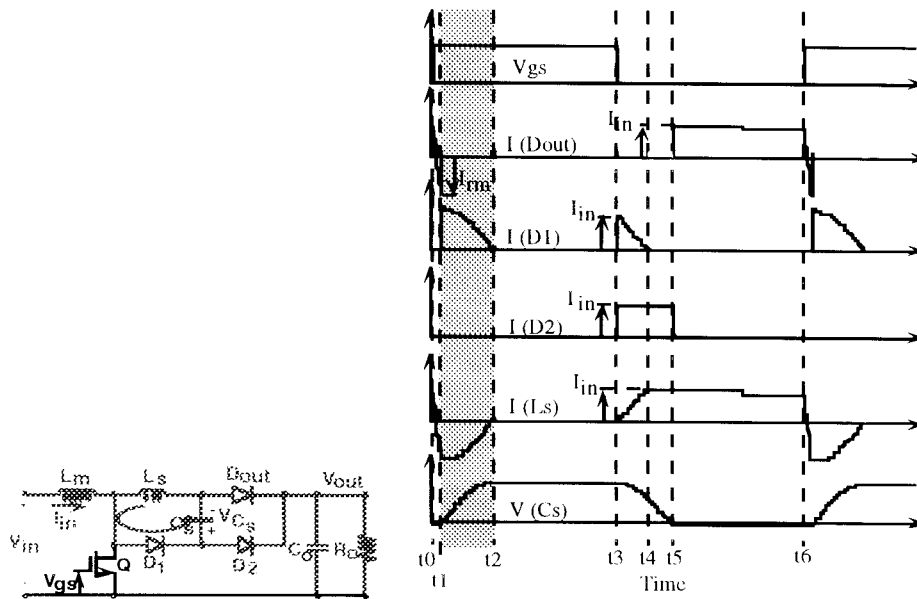



## Interval $t_2$ - $t_3$

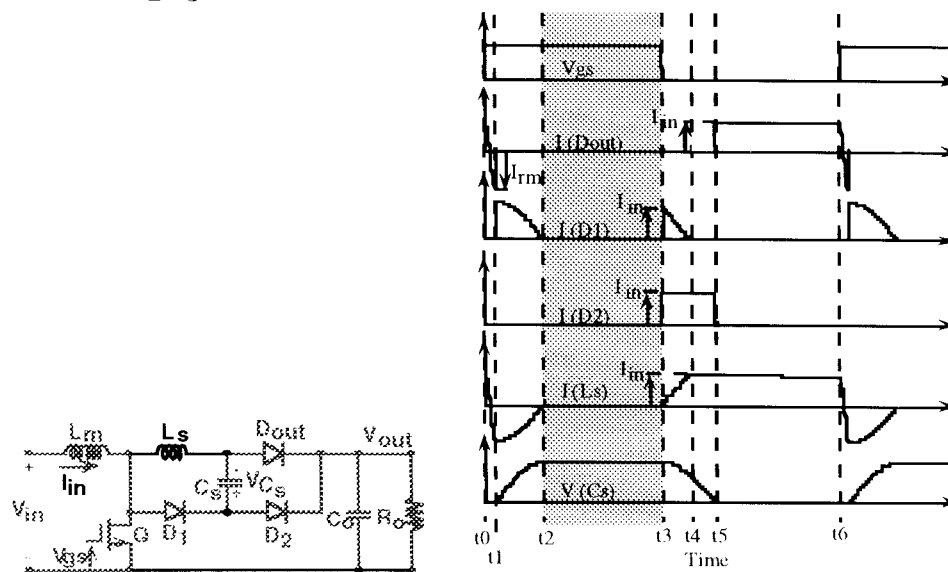



Interval  $t_3$ - $t_4$

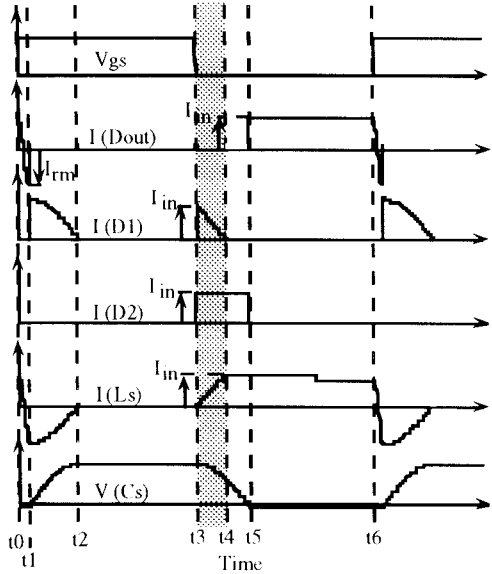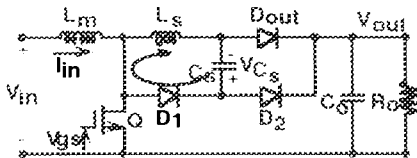

Interval  $t_4$ - $t_5$

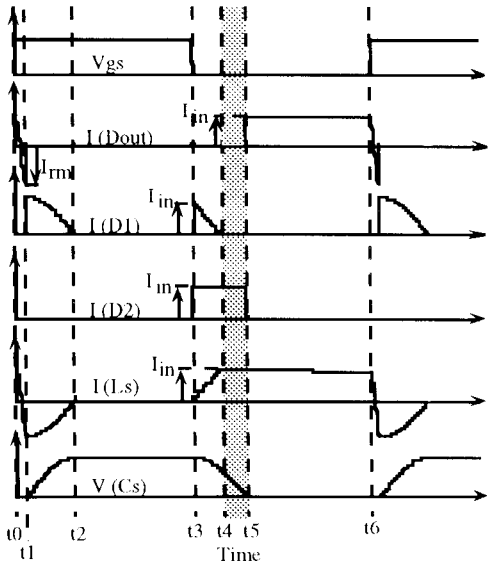
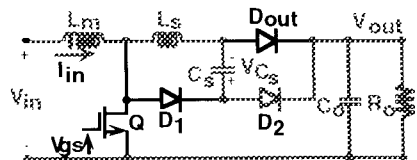


Interval  $t_5$ - $t_6$

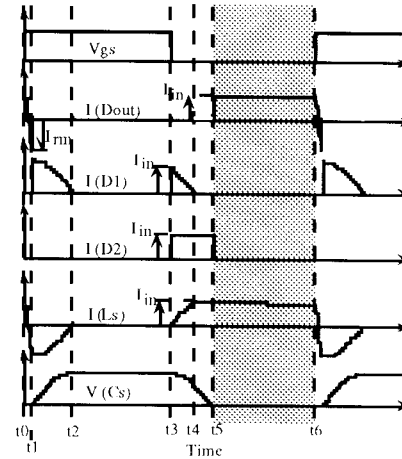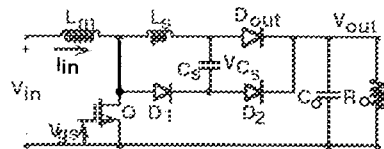

Practical requirement of peak reverse recovery current -  $I_{rm}$


If  $I_{rm} < I_{in}$

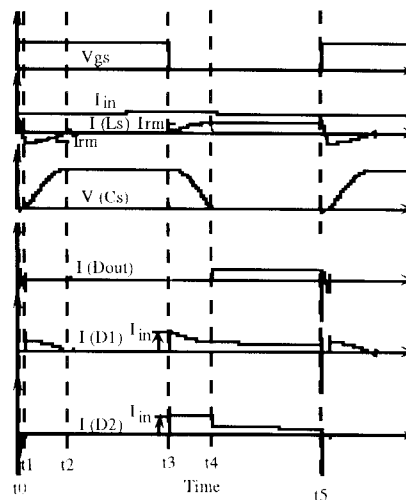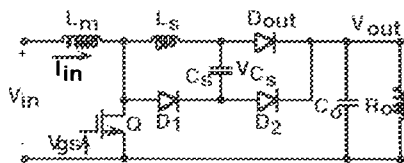

To avoid the above undesired condition

$$I_{rm} > I_{in}$$

The coupled inductor realization

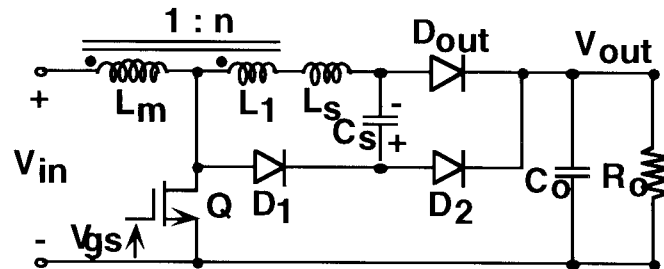

$D_{out}$  - Main diode

$D_1, D_2$  - Auxiliary diodes


$L_s, C_s$  - Resonant network

$L_m, L_1$  - Coupled inductors


$n$  - turn ratio

Simplified equivalent circuits of the resonant elements with coupling inductor

$V_{cpl\ on}$

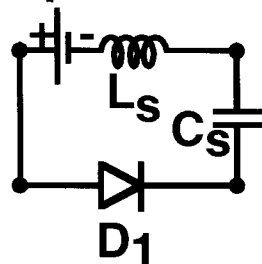


$V_{cpl\ off}$

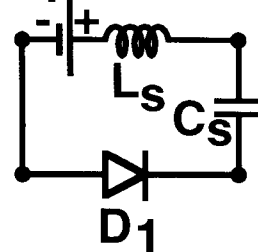

$$V_{cpl\ on} = nV_{in}$$

$$V_{cpl\ off} = \frac{n}{1+n} (V_{out} - V_{in})$$
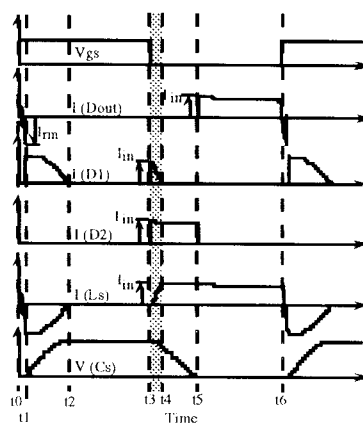
## Basic waveforms of the lossless snubber with coupling inductor



$V_{Cs}(t_3)$  is larger and therefore  $t_{3-4}$  is smaller

**Components Stress**

Transistor or diode	Current stress	Current stress instance or interval	Voltage stress	Voltage stress instance or interval
Q	$I_{in}+I_{rm}$	$t_1$	$V_{out}$	$t_3-t_4$
$D_o$	$I_{in}$ $I_{rm}$	$t_5-t_6$ $t_1$	$V_{out} +V_{Cmax}$	$t_2$
$D_1$	$\sqrt{I_{rm}^2 + \frac{V_{cpl\ on}^2 C_s}{L_s}}$	$t_1 < t_e < t_2$	$V_{out} -V_{cpl\ on}$	$t_0-t_1$
$D_2$	$I_{in}$	$t_3-t_5$	$V_{out}$	$t_1-t_2$

$$I_{rm} = \frac{(V_{out}+V_{cpl\ on})t_{rm}}{L_s}$$

$$t_{rm} \approx t_{rr} \quad t_{rr} = \text{ formal reverse recovery time}$$


$$V_{cpl\ on} = nV_{in} = n(1-D)V_{out}$$

$$D = \frac{t_{on}}{T_s}$$

$$V_{Cmax} = I_{rm} \sqrt{\frac{L_s}{C_s}} \sin(\omega_r t_{1-2}) + V_{cpl\ on} [1- \cos(\omega_r t_{1-2})]$$

$$\omega_r t_{1-2} = \tan^{-1}(-\frac{I_{rm} \sqrt{\frac{L_s}{C_s}}}{V_{cpl\ on}}) + \pi$$

## An experimental 1kW Boost converter

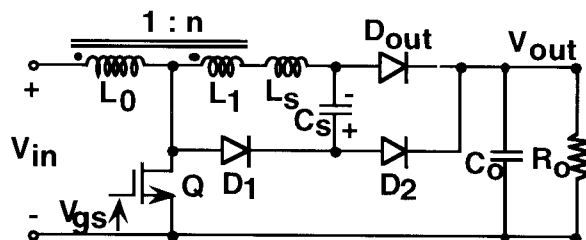

Q - IRF460

Dout - MUR860  $t_{rr} = 60\text{nsec.}$

D1, D2 - MUR460

Ls - 3uH

Cs - 100nF

n=1/7

Operational conditions

Fs - 100KHz

Pout - 1000W


Vin - 200V

Vout - 400V

Iin - 5.8A

D - 0.5
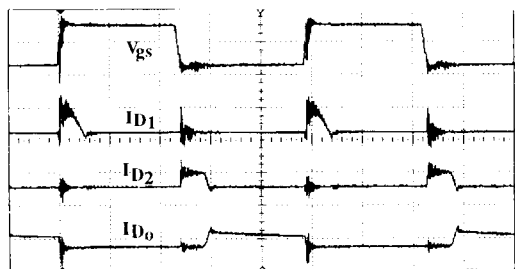
## Typical waveforms of the experimental Boost converter




Vertical scales: 10V/div, 5A/div

Horizontal scale: 2μSec/div

✓ Smaller reverse recovery current of Do

## Power dissipation

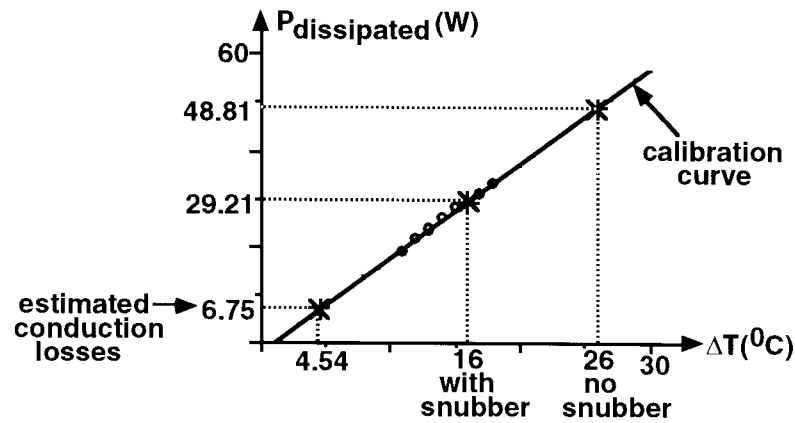

o DC calibration points


Power dissipation dropped by 19.6W

## Additional Comments

- ✓ The main advantages of the lossless snubber:
    - ZCS in turn-on
    - Smaller reverse recovery current
  - ✓ The preferred embodiment is coupled inductors
  - ✗ The main disadvantage of the snubber is limitation of the duty cycle range
  - ✓ The overall efficiency of the experimental Boost converter was found to increase by 1%-2%
- The snubber can be adopted to other PWM topologies




## Implementation in Buck converter

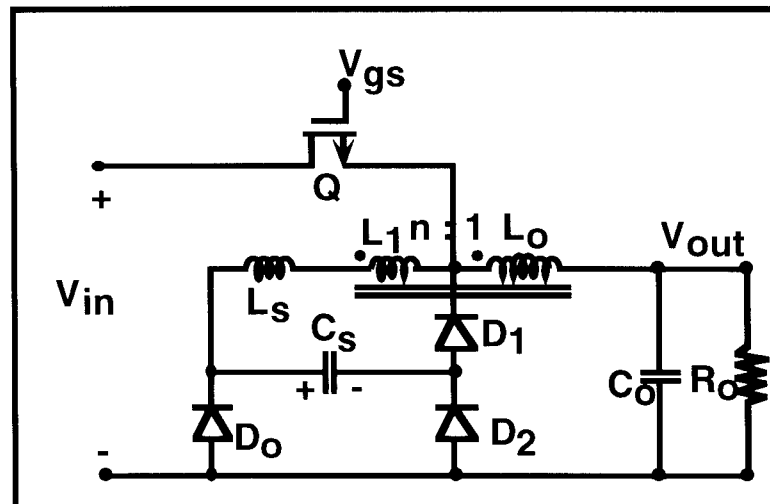


☞ Proven to increase efficiency by  $\approx 2\%$
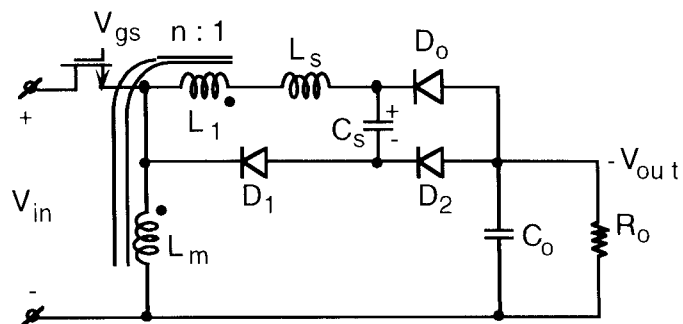
## Implementation in a buck-boost converter




## Implementation in APFC

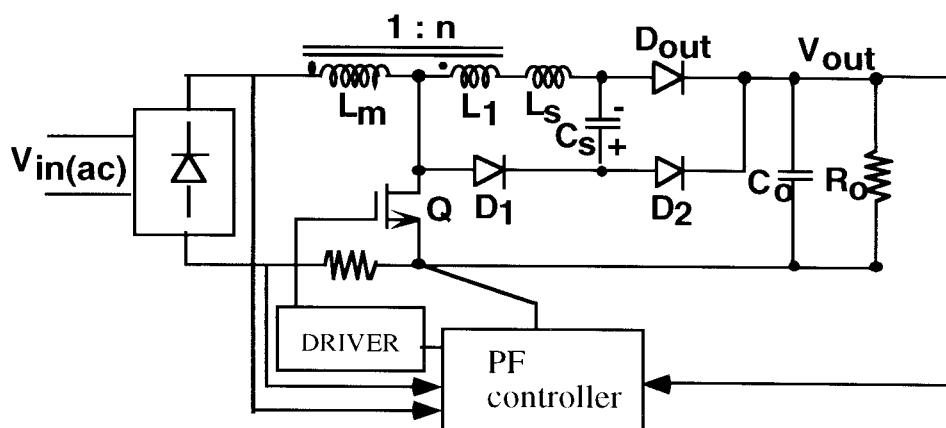

- Simple implementation
- 👁 Watch  $D_{onmin}$
- 👉 Proven to increase efficiency by  $\approx 2\%$
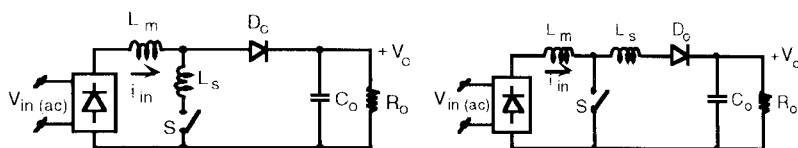
## RMS current of the snubber inductor in a boost converter implemented in APFC

Two ways of snubber inductor ( $L_s$ ) connection:



(a)

(b)


(snubber elements except  $L_s$  are not shown)

## RMS current of the snubber inductor in a boost converter implemented in APFC

### Main assumptions

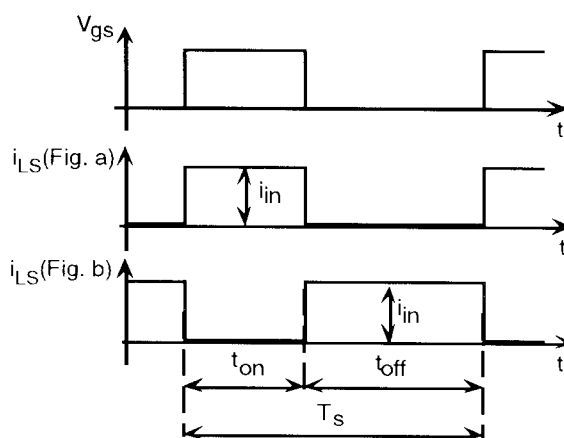1. The duration of transient processes after the switch S is turned on and after S is turned off are neglected.
2. The input inductance  $L_m$  is sufficiently large that their current  $i_{in}$  is practical constant during one high frequency switching cycle  $T_s$ .

Under these conditions the current  $i_{Ls}$  of the snubber inductor has a rectangular waveform during one high frequency switching cycle  $T_s$ .



For one switching cycle  $T_s$  (high frequency period)


$$I_{Ls \text{ rms hf (Fig. a)}} = i_{in} \sqrt{D}$$

$$I_{Ls \text{ rms hf (Fig. b)}} = i_{in} \sqrt{1-D}$$

$$\text{where } D = \frac{t_{on}}{T_s} \quad (\text{hf - high frequency})$$

## RMS current of the snubber inductor in a boost converter implemented in APFC

Ideal APFC

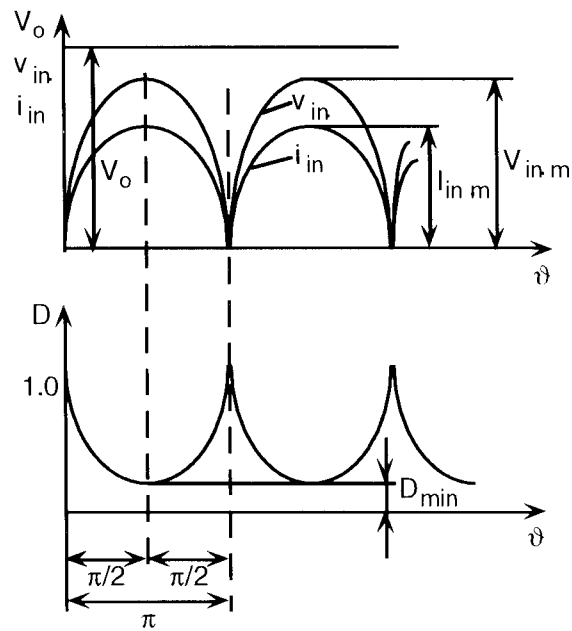

$$v_{in} = V_{in\ m} \sin \vartheta$$

$$i_{in} = I_{in\ m} \sin \vartheta$$

where

$$\vartheta = 2\pi f_{lf} t \quad (f_{lf} = 50 \text{ or } 60 \text{ Hz}) \quad (\text{lf - low frequency})$$

$$V_o = \text{const}$$

In boost converter

$$\frac{V_o}{v_{in}} = \frac{1}{1-D} \rightarrow D = 1 - (1 - D_{min}) \sin \vartheta$$

where

$$D_{min} = 1 - \frac{V_{in\ m}}{V_o}$$

RMS current of the snubber inductor  
in a boost converter implemented in APFC

Ideal APFC (cont.)


RMS current for low frequency period

$$I_{Ls \text{ rms lf}} (\text{Fig. a}) = \sqrt{\frac{1}{\pi} \int_0^{\pi} I_{in \text{ m}}^2 [\sin^2 \vartheta - (1-D_{\min}) \sin^3 \vartheta] d\vartheta} =$$

$$= I_{in \text{ m}} \sqrt{0.5 - \frac{4}{3\pi} (1-D_{\min})}$$

$$I_{Ls \text{ rms lf}} (\text{Fig. b}) = \sqrt{\frac{1}{\pi} \int_0^{\pi} I_{in \text{ m}}^2 (1-D_{\min}) \sin^3 \vartheta d\vartheta} =$$
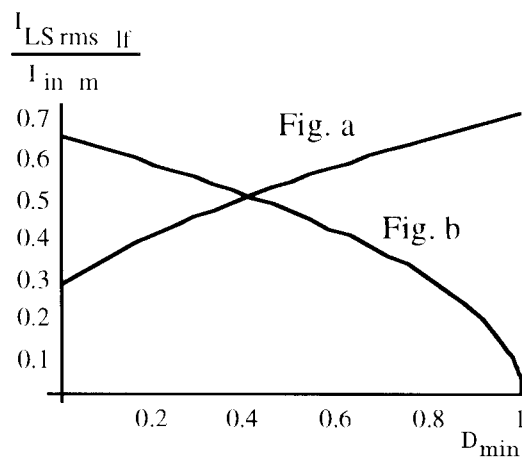
$$= I_{in \text{ m}} \sqrt{\frac{4}{3\pi} (1-D_{\min})}$$



Conclusion: Fig. a is preferable if  $D_{\min} < 0.4$  and Fig. b is preferable if  $D_{\min} > 0.4$ .

## Chapter 6

### TURN-ON AND TURN-OFF SINGLE SWITCH SNUBBERS

## TURN-ON AND TURN-OFF SINGLE SWITCH SNUBBERS


Possible Realizations:

LCC - one resonant inductor and two resonant capacitors  
[10, 16, 22, 31, 32, 34, 39, 46]

LLC - two resonant inductors and one resonant capacitor  
[1, 23, 29, 45]

LC - one resonant inductor and one resonant capacitor  
[2, 22, 36, 41]
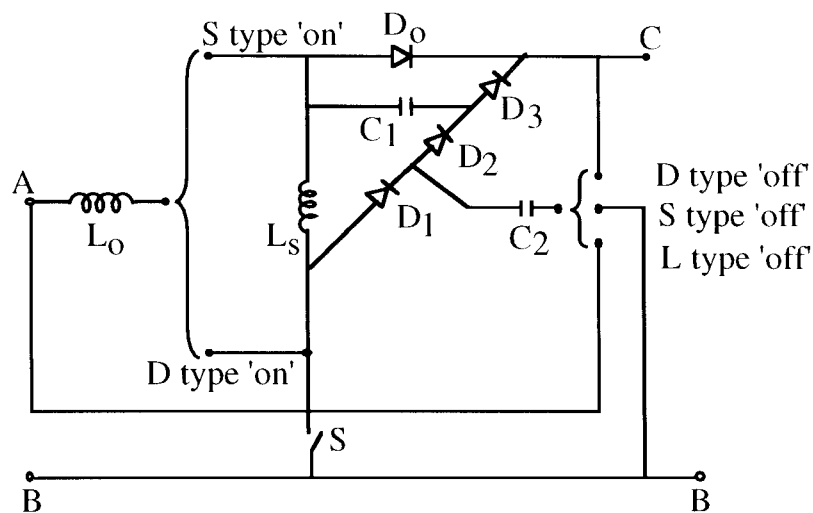
### Generic LCC 'turn-off' & 'turn-on' snubber topology (see also [32])




- Snubber analysis is identical for all connections


## TURN-ON AND TURN-OFF SINGLE SWITCH SNUBBERS

Boost converter with LCC snubber: D type 'on' and S type 'off'  
(SNB8) [22, 31, 32]



(Modified turn-on snubber SNB7)

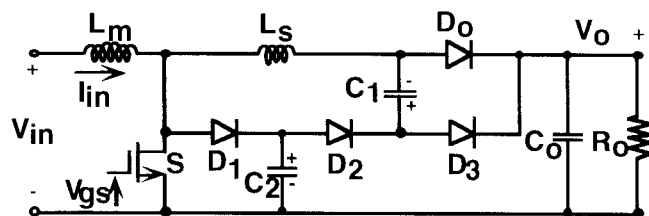

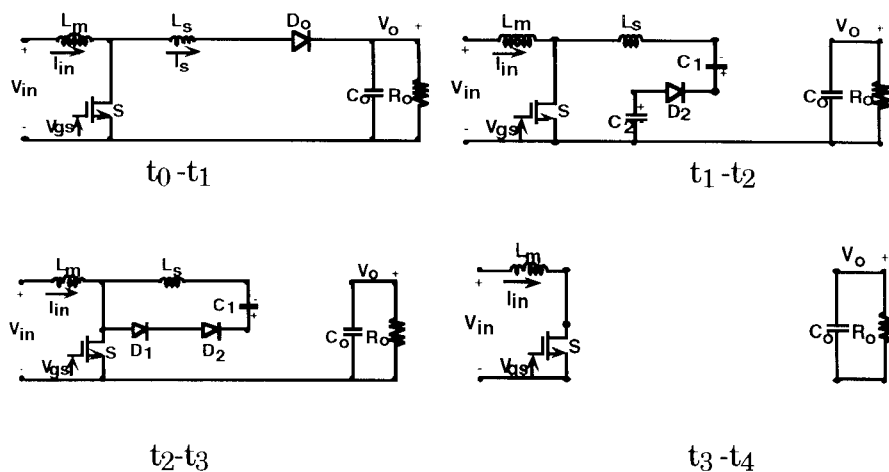S - main switch  
D<sub>0</sub> - main diode  
D<sub>1</sub>, D<sub>2</sub>, D<sub>3</sub> - auxiliary diodes





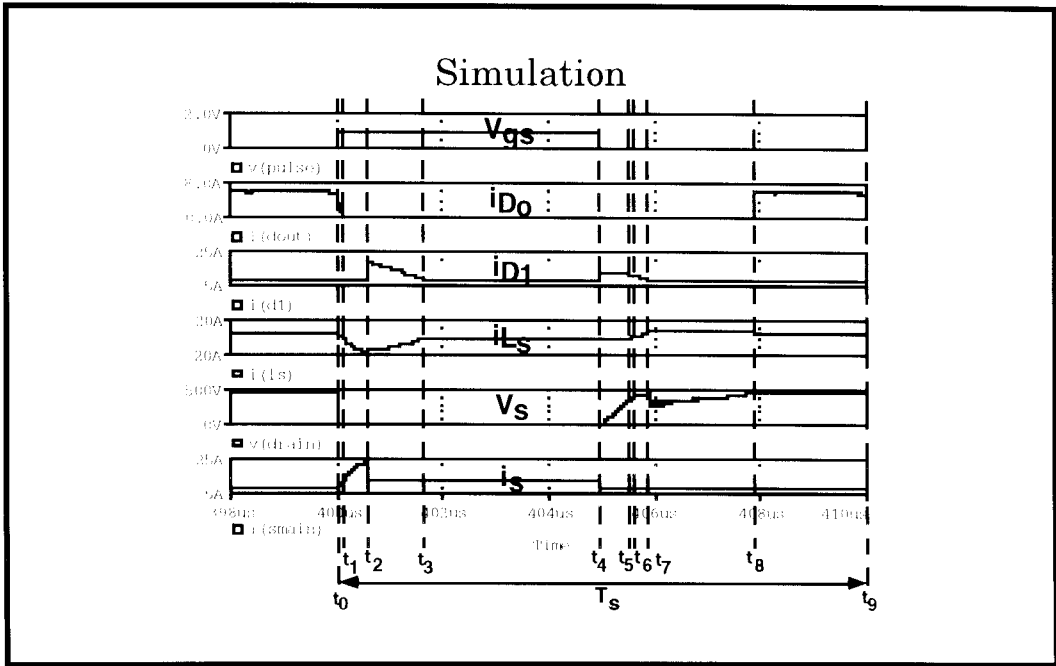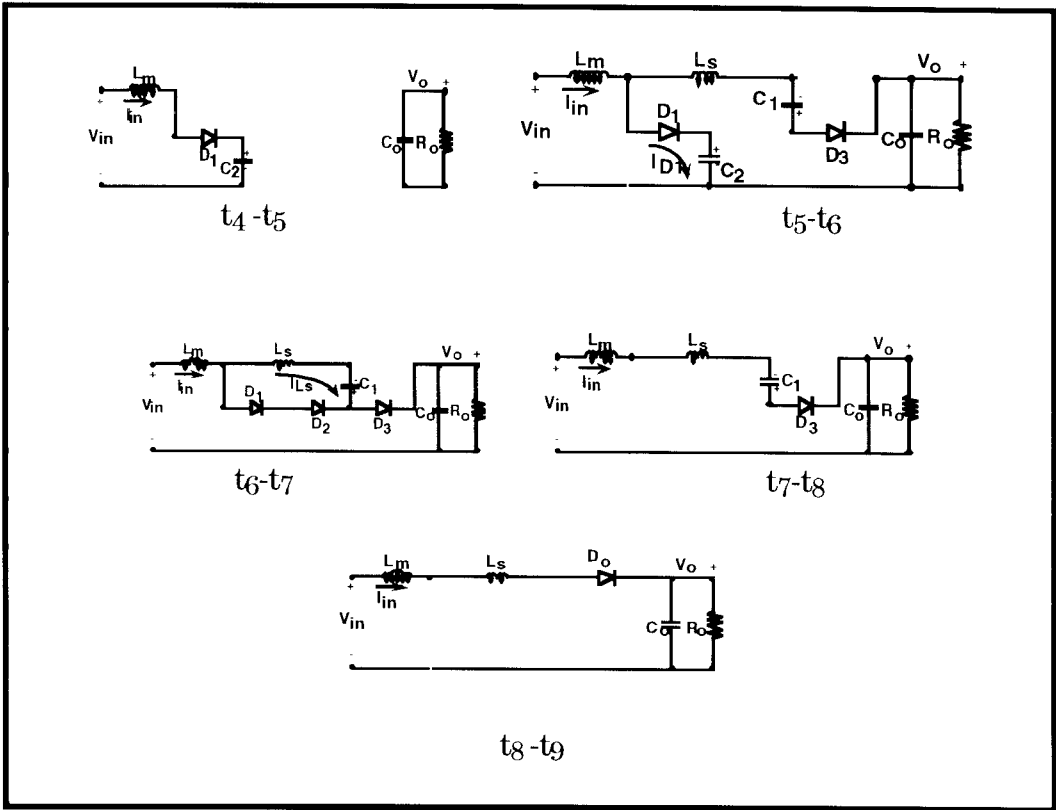

Interval  $t_0$ - $t_1$

$$i_s = \frac{V_o}{L_s} t \quad \text{ZCS!}$$

$$\frac{di_s}{dt} = \frac{V_o}{L_s}$$

$$i_{D0} = I_{in} - i_s$$

$t_1 - t_0$  is found from the condition:  $i_{D0}(t_1) = 0$

$$t_1 - t_0 = \frac{I_{in} L_s}{V_o}$$

$$v_{C1} = 0 \quad ; \quad v_{C2} = V_o$$

Interval  $t_1$ - $t_2$        $i_s = I_{in} + i_{Ls}$

$$i_{Ls} = i_{C1} = i_{C2} = i_{D2} = \frac{V_o}{\sqrt{\frac{L_s}{C_{12}}}} \sin[\omega_{r12}(t - t_1)]$$

where

$$C_{12} = \frac{C_1 C_2}{C_1 + C_2} ; \quad \omega_{r12} = \frac{1}{\sqrt{L_s C_{12}}}$$

$$v_{C1} = V_o \frac{C_2}{C_1 + C_2} \{1 - \cos[\omega_{r12}(t - t_1)]\}$$

$$v_{C2} = -v_{D1} = V_o \frac{C_2}{C_1 + C_2} \left\{1 + \frac{C_1}{C_2} \cos[\omega_{r12}(t - t_1)]\right\}$$

$t_2 - t_1$  is found from the condition:  $v_{D1}(t_2) = 0$

$$t_2 - t_1 = \frac{1}{\omega_{r12}} \cos^{-1}\left(-\frac{C_2}{C_1}\right) = \sqrt{L_s C_{12}} \cos^{-1}\left(-\frac{C_2}{C_1}\right)$$

$$i_{D0} = i_{D1} = i_{D3} = 0$$

Interval  $t_2-t_3$   $i_s=I_{in}$

$$i_{Ls}=i_{C1}=i_{D1}=i_{D2}=-\frac{V_{C1}(t_2)}{\sqrt{\frac{L_s}{C_1}}}\sin[\omega_{r1}(t-t_2)]+i_{Ls}(t_2)\cos[\omega_{r1}(t-t_2)]$$

where

$$\omega_{r1}=\frac{1}{\sqrt{L_s C_1}}$$

$t_3-t_2$  is found from the condition:  $i_{D1}(t_3)=i_{D2}(t_3)=0$

$$t_3-t_2=\frac{1}{\omega_{r1}}\tan^{-1}\left(\frac{i_{Ls}(t_2)\sqrt{\frac{L_s}{C_1}}}{v_{C1}(t_2)}\right)=\frac{1}{\omega_{r1}}\tan^{-1}\left(\sqrt{\frac{C_1-C_2}{C_2}}\right)$$

$$\begin{aligned} v_{C1} &= v_{C1}(t_2)\cos[\omega_{r1}(t-t_2)]+i_{Ls}(t_2)\sqrt{\frac{L_s}{C_1}}\sin[\omega_{r1}(t-t_2)] \\ &= V_0\frac{C_2}{C_1}\cos[\omega_{r1}(t-t_2)]+V_0\frac{\sqrt{C_2(C_1-C_2)}}{C_1}\sin[\omega_{r1}(t-t_2)] \end{aligned}$$

$$v_{C1}(t_3)=V_0\sqrt{\frac{C_2}{C_1}}$$

Interval  $t_3-t_4$   $i_s=I_{in}$

$$i_{D0}=i_{D1}=i_{D2}=i_{D3}=0$$

$$v_{D0}=-V_0$$

$$v_{C1}=v_{C1}(t_3)=V_0\sqrt{\frac{C_2}{C_1}} \quad (C_2 < C_1)$$

$$v_{C2}=0$$

Interval  $t_4-t_5$   $i_s=0$

$$i_{D1}=I_{in}$$

$$v_s=v_{C2}=\frac{I_{in}(t-t_4)}{C_2} \quad \frac{dv_s}{dt}=\frac{I_{in}}{C_2} \quad \text{ZVS!}$$

$$C_1=v_{C1}(t_3)=V_0\sqrt{\frac{C_2}{C_1}} \quad v_{D3}=v_{C2}+v_{C1}-V_0$$

$t_5-t_4$  is found from the condition:  $v_{D3}(t_5)=0$

$$t_5-t_4=\frac{V_0 C_2 (1-\sqrt{\frac{C_2}{C_1}})}{I_{in}}$$

Interval  $t_5$ - $t_6$

$$i_s=0; \quad i_{D0}=i_{D2}=0$$

$$i_{D1}=I_{in} \frac{C_1}{C_1+C_2} \left\{ \frac{C_2}{C_1} + \cos[\omega_{r12}(t-t_5)] \right\}$$

$$v_{C2}=V_o \left( 1 - \sqrt{\frac{C_2}{C_1}} \right) + \frac{I_{in}}{\omega_{r12}(C_1+C_2)} \left\{ \omega_{r12}(t-t_5) + \frac{C_1}{C_2} \sin[\omega_{r12}(t-t_5)] \right\}$$


Two operating modes are possible. They depend on the condition at  $t_6$  of the interval  $t_5$ - $t_6$ :

$$\text{Mode 1 will prevail if :} \quad (v_{C2})_{t_6} = V_o \quad (i_{D1})_{t_6} > 0$$

$$\text{Mode 2 will prevail if :} \quad (i_{D1})_{t_6} = 0 \quad (v_{C2})_{t_6} < V_o$$

$$\text{Necessary condition for Mode 1:} \quad \frac{V_o}{I_{in}} \sqrt{\frac{C_2}{L_s}} < k_C$$
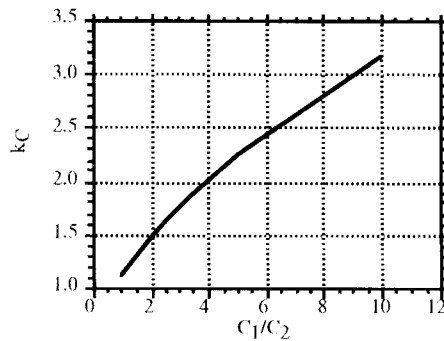
$$\text{where :} \quad k_C = \frac{1}{\left(1 + \frac{C_2}{C_1}\right) \sqrt{\frac{C_1}{C_2} + 1}} \left[ \cos^{-1}\left(-\frac{C_2}{C_1}\right) + \sqrt{\left(\frac{C_1}{C_2}\right)^2 - 1} \right]$$



The dependence of  $k_C$  on  $\frac{C_1}{C_2}$

- For Mode 1:  $\frac{V_o}{I_{in}} \sqrt{\frac{C_2}{L_s}} < k_C$

$t_6-t_5$  is found from the condition:  $v_{D2}(t_6)=0$ ;  $v_{C2}(t_6)=V_o$

Interval  $t_6-t_7$  , Mode 1,  $i_s=0$ ;  $v_s=V_o$

$$i_{D3}=I_{in}$$

$$i_{D1}=i_{D2}=I_{in}-i_{Ls}$$

$$i_{Ls}=\frac{V_{C1}(t_3)}{\sqrt{\frac{L_s}{C_1}}}\sin[\omega_{r1}(t-t_6)]$$

$t_7-t_6$  is found from the condition:  $i_{D1}(t_7)=i_{D2}(t_7)=0$

$$t_7-t_6=\frac{1}{\omega_{r1}}\sin^{-1}\left(\frac{I_{in}\sqrt{\frac{L_s}{C_1}}}{v_{C1}(t_3)}\right)=\frac{1}{\omega_{r1}}\sin^{-1}\left(\frac{I_{in}\sqrt{\frac{L_s}{C_2}}}{V_o}\right)$$

Interval  $t_7-t_8$  , Mode 1,  $i_s=i_{D0}=i_{D1}=i_{D2}=0$ ;  $i_{D3}=I_{in}$

$$v_{C1}=v_{C1}(t_7)-\frac{I_{in}(t-t_7)}{C_1}$$

$t_8-t_7$  is found from the condition:  $v_{C1}(t_8)=0$

$$t_8-t_7=\frac{v_{C1}(t_7)C_1}{I_{in}}$$

$$v_s \approx V_o - v_{C1}$$


Interval  $t_8-t_9$  , Mode 1,  $i_s=i_{D1}=i_{D2}=i_{D3}=0$ ;

$$i_{D0}=I_{in}$$

$$v_s \approx V_o ; \quad v_{C1}=0 ; \quad v_{C2}=V_o$$
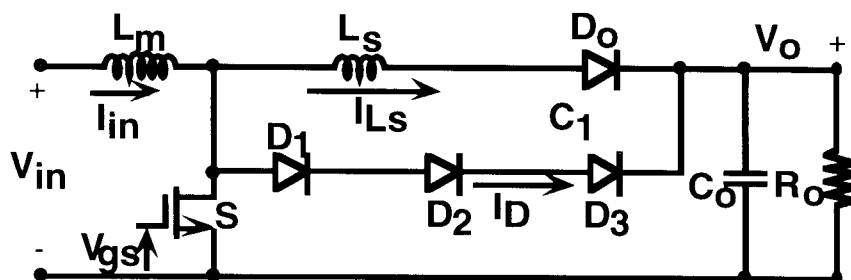
## LOSSLESS TURN-ON AND TURN-OFF SNUBBER (SNB8)

Mode 2. Time interval before the switch Q is turned on



- Three auxiliary diodes are conducting
- Hard switching
- Coupling will help to avoid Mode 2.

## TURN-ON TURN-OFF SNUBBER (SNB8)

Typical Design

Given:  $V_o$ ,  $I_{in}$ ,  $(\frac{di_S}{dt})_{t_0-t_1}$ ,  $(\frac{dv_S}{dt})_{t_4-t_5}$ ,  $D_{min}$ ,  $D_{max}$

$$1. L_s \geq \frac{V_o}{(\frac{di_S}{dt})_{t_0-t_1}} \quad 2. C_2 \geq \frac{I_{in}}{(\frac{dv_S}{dt})_{t_4-t_5}}$$

$$3. k_C > \frac{V_o}{I_{in}} \sqrt{\frac{C_2}{L_s}} > 1$$

4. Select  $C_1/C_2$  using the plot  $k_C = \phi(\frac{C_1}{C_2})$ .

$$5. \quad t_{on \min} = \frac{I_{in} L_s}{V_o} + \sqrt{L_s C_{12}} \cos^{-1} \left( -\frac{C_2}{C_1} \right) + \sqrt{L_s C_1} \tan^{-1} \left( \sqrt{\frac{C_1 - C_2}{C_2}} \right)$$

$$6. \quad t_{off \min} \approx \frac{V_o C_2}{I_{in}} \left[ 1 + \sqrt{\frac{C_1}{C_2} \left( 1 - \frac{I_{in}^2 L_s}{V_o^2 C_2} \right)} \right] + \sqrt{L_s C_1} \sin^{-1} \left( \frac{I_{in} \sqrt{\frac{L_s}{C_2}}}{V_o} \right)$$

$$7. \quad D_{\min} = (t_{on \min}) f_s ; D_{\max} = (1 - t_{off \min}) f_s$$

8. Current stress of the switch S


$$I_{s \text{ pk}} = I_{in} + V_o \sqrt{\frac{C_{12}}{L_s}}$$

9. Voltage stress of the switch S

$$V_{s \text{ pk}} = V_o$$

Apply iteration to approach desired design goals

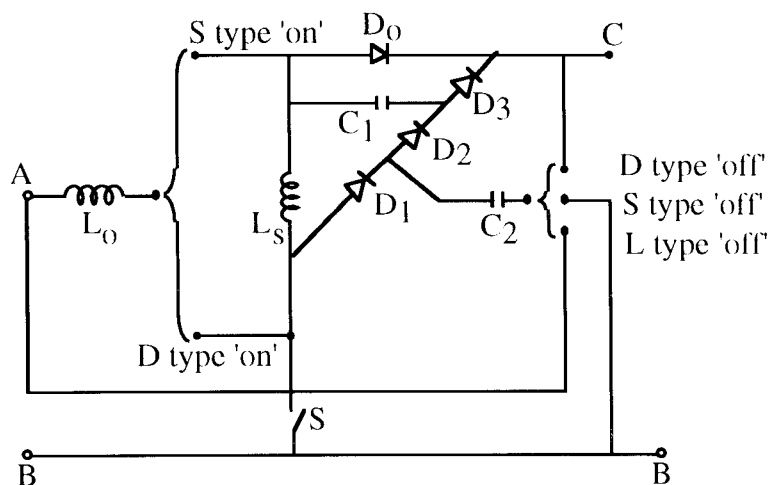
## Some Additional Recent Turn-On & Turn-Off Passive Lossless LCC Snubbers



- Generic LCC 'turn-off' & 'turn-on' snubber topology

SNB8 discussed above (drawn differently)

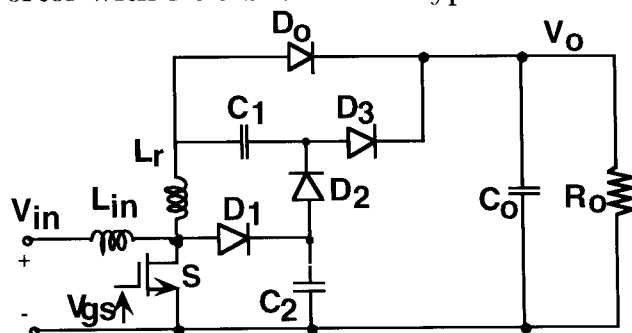
Boost converter with LCC snubber: D type 'on' and S type 'off'






Moving the connection point to main inductor

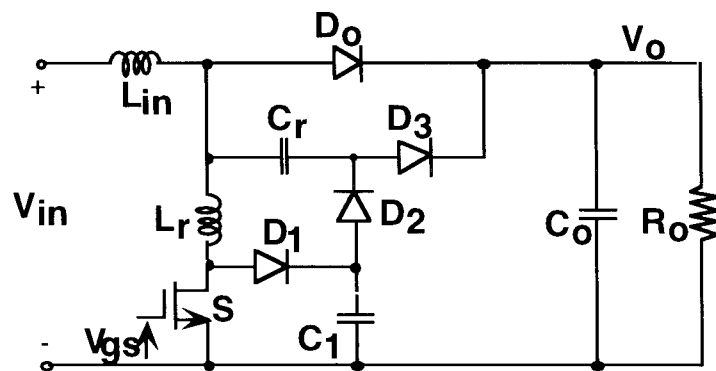Boost converter with LCC snubber: S type 'on'  
and S type 'off' (SNB9) [16, 32, 39]




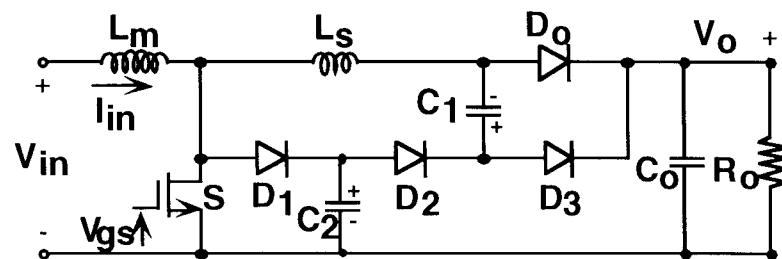Topologies similar to SNB8 and SNB9  
with different capacitor  $C_2$  connections [31, 32, 34, 46]



Original

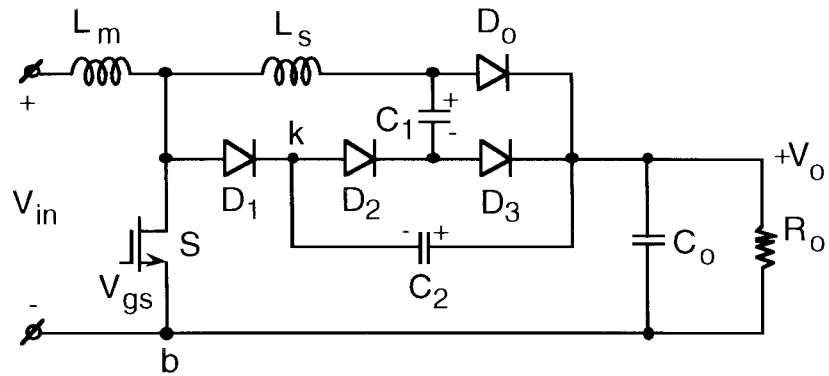SNB10: D type 'on' and D type 'off' [34, 46]




$C_2$  connected to output



Ripple to output

SNB11: D type 'on' and L type 'off' [32]

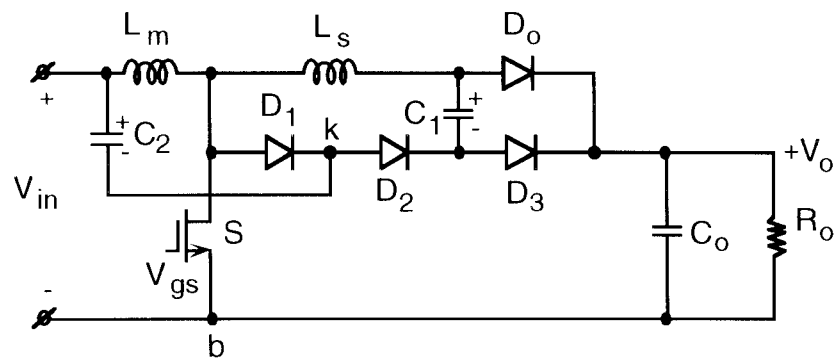


$C_2$  connected to input



Ripple stored to input

SNB12: D type 'on' and L type 'off' [31]

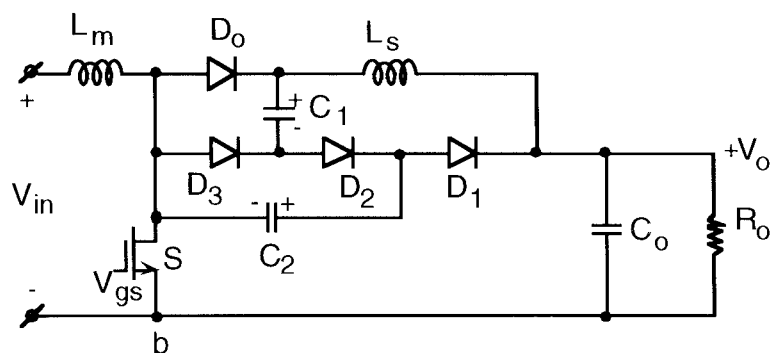


$C_2$  connected to switch



Stirs ripple to output

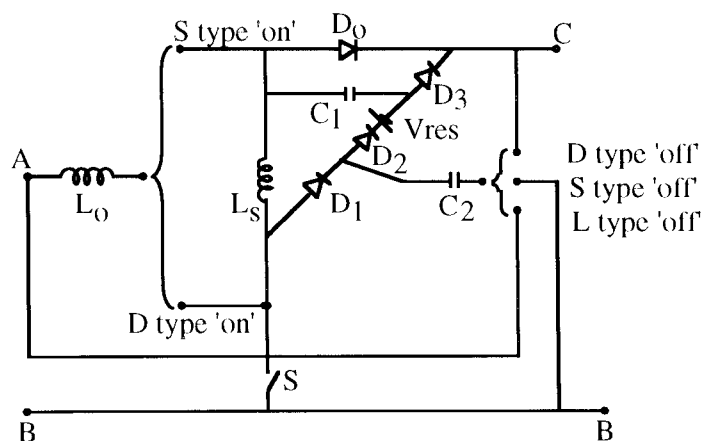
Generic LCC 'turn-off' & 'turn-on' snubber topology with improved reset



- $V_{res}$  accelerates the reset phase

## Turn-on and turn-off snubber for single switch converter

### Improved Williams snubber SNB13 [10]

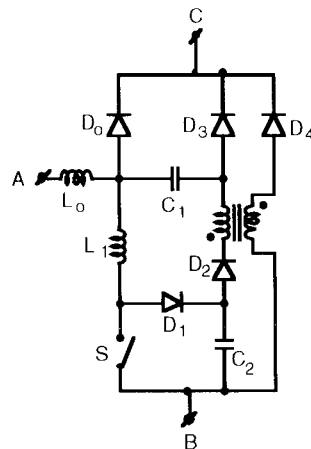

Operating process is based on a dual energy recovery circuit, improvement on SNB9.

- $V_{res}$  replaced by transformer


Claimed to have:

1. Lower peak current in the switch S.
2. Shorter discharge time is needed for the capacitor  $C_1$  at low load . Hence, wider operation range of load current and higher switching frequency.


👁 Reset through transformer (leakage and reset problems ?)

See also snubbers with recovery transformers [11-13]

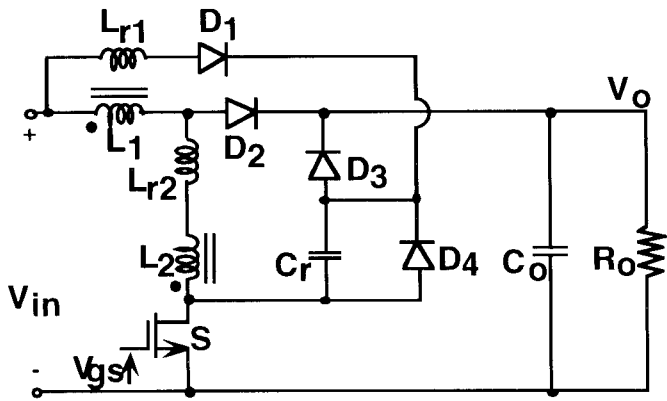Boost converter with LLC-type snubber (SNB14)  
[1, 23, 45]



Coupled inductor

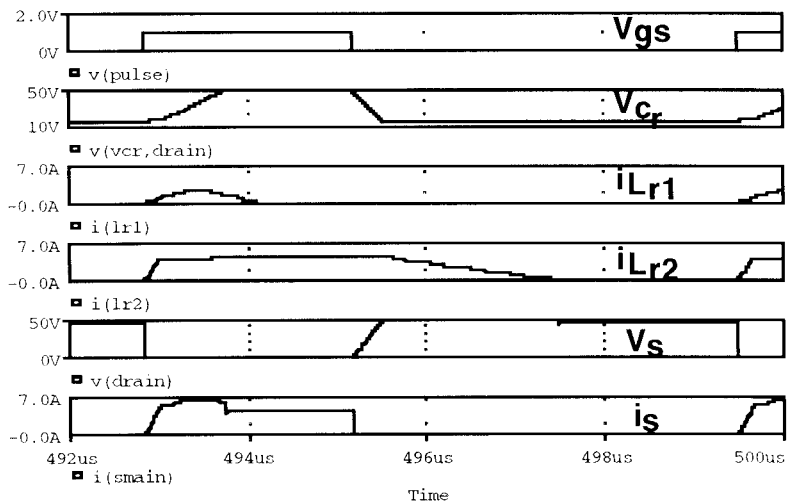

Basic waveforms of SNB14

## SNB14 Features


### Pro

1. Soft switching at turn-on and turn-off in a wide load range without high current and voltage stresses.
2. Coupling decreases the minimal needed value of turn-off time of the switch.

### Con


1. The resonant circuit  $L_1C_r$  is fed from the input voltage  $V_{in}$ . Hence, the peak capacitor's voltage cannot be higher  $2V_{in}$ . Consequently, when  $V_o > 2V_{in} \Rightarrow$  hard switching.
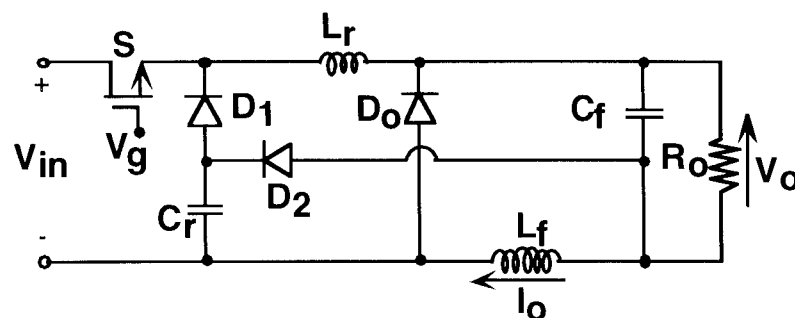
## Buck converter with LC type snubber (SNB15) [2, 36] (one inductor and one capacitor)



- No common ground !

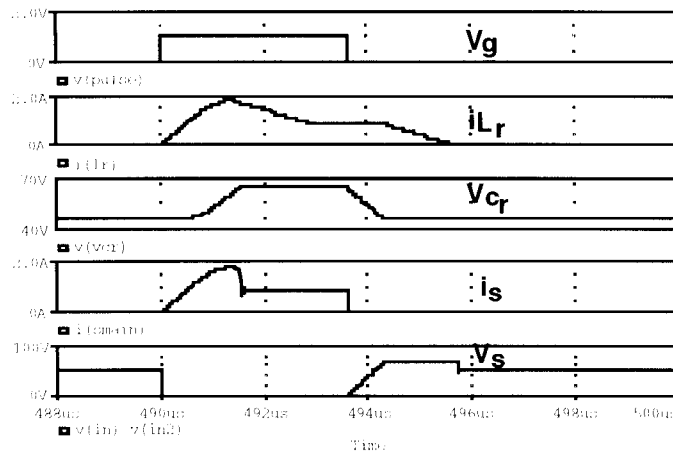See boost converter with LC type snubber in [41]




Waveforms of SNB15

{'Turn-on'}, {'turn-off'} and {'turn-on' - 'turn-off'}  
snubbers


Can parasitic elements be used ?

1. 'Turn on'

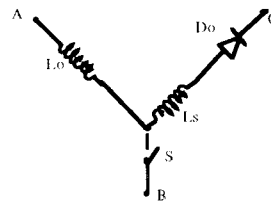

- $L_s$  relatively large inductance to lower  $\frac{dI}{dt}$  and hence diode peak reverse current and trapped energy
- Need a mechanism for recovering trapped energy
- 👁 Impractical to obtain by stray inductance such as interconnections
- 👁 Can be part of transformer or flyback coupled inductor

## 2. 'Turn off'

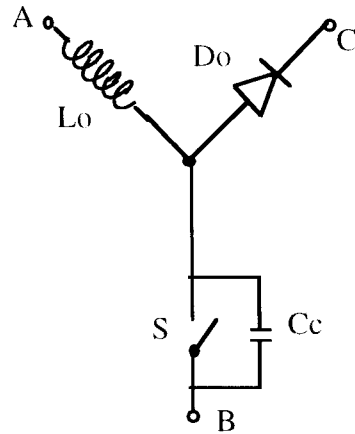

- $C_c$  significant inductance to lower  $\frac{dV}{dt}$
- $C_c$  is mainly needed while voltage on switch is low



Switch output capacitance would be helpful and sometime sufficient

## 2. 'Turn off' - cont.



If internal capacitance is used:


- fast gate 'turn off'
- high sink current
- low source inductance "fast switch"



Look up new MOSFET generations (APT V)



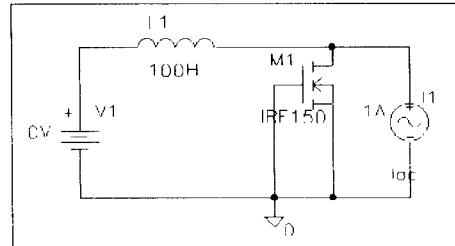
## Output Capacitance of MOSFETs A study by Simulation



- Nested AC analysis
- $V_1$  is swept from 0V to 100V
- $I_{ac}$  is set to 1A (not to worry, used after linearization)
- Capacitance is calculated from:

$$C_{out} = \frac{1}{2 \pi \text{ frequency } V_{ds}}$$

'frequency' -> PSPICE variable

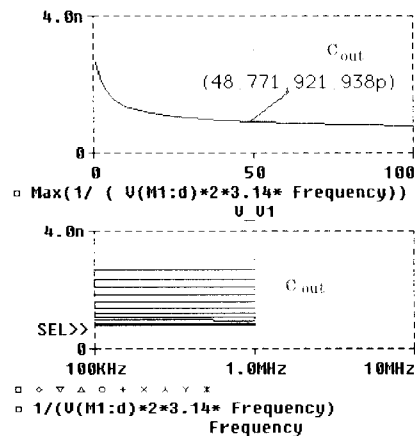


Upper trace:  $C_{out}$  as a function of  $V_{DS}$

Lower trace:  $C_{out}$  as a function of frequency for various  $V_{DS}$  values.


- About 1 nF at 50V
- For significant improvement added snubber capacitance > 1nF
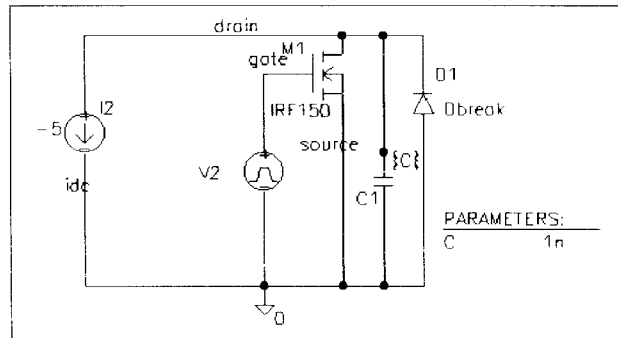
## Simulating Snubbing Effects 'turn-off'



- Transient analysis
- C is swept 0nF - 10nF

C=0

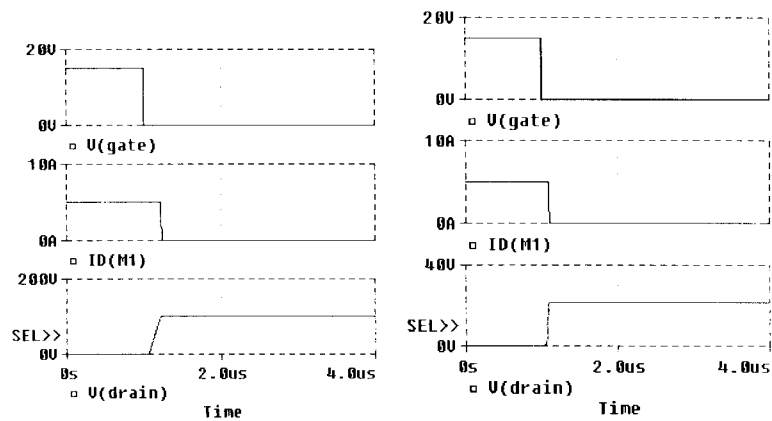


Drain clamped to 100V

Drain clamped to 20V


- Drain current reflects charging of internal capacitor
- Part of energy stored as  $\frac{C V^2}{2}$  --> losses at 'turn-on' !
- Not all of  $\{I_D * V_{DS}\}$  at 'turn off' duration is lost to heat

$C = 0 \text{ \& } 1\text{nF}$

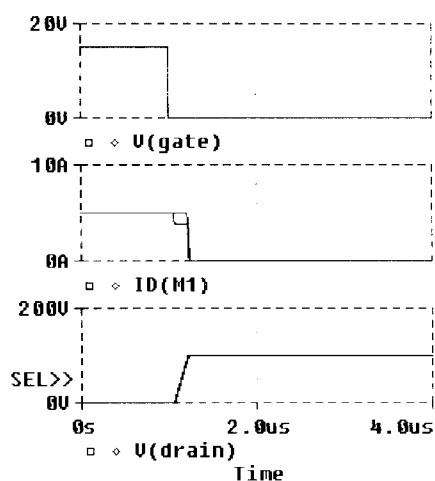

- Small part of current channeled to snubbing capacitor

$C = 0 \text{ \& } 10\text{nF}$

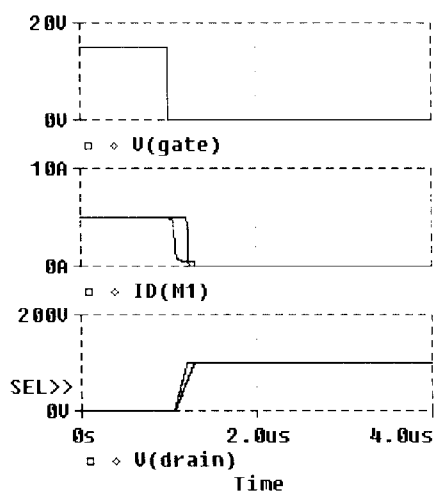


- Current channeled to 10nF capacitor
- Internal capacitor still charges to the same voltage !

## Chapter 7



### RECTIFIER DIODES LOSSLESS SNUBBERS


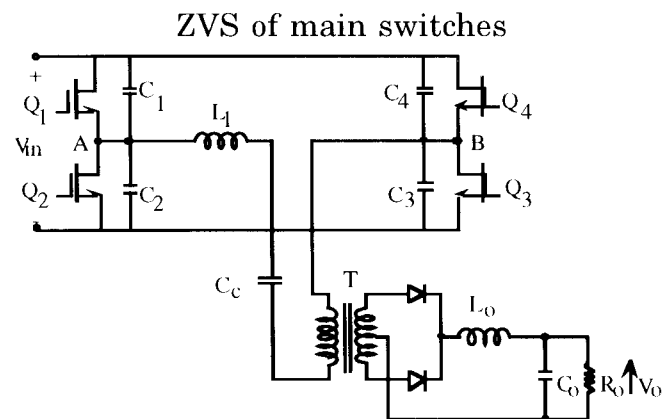
### PHASE SHIFTED PWM (PSPWM) [18, 19, 27]




#### Basic Phase Shifted PWM Stage


- Leading and lagging legs (bridge non-symmetrical)
- Coupling capacitor  $C_c$  needed to block current
  - Asymmetry of control (+noise !)
  - Can be eliminated by applying peak current mode control

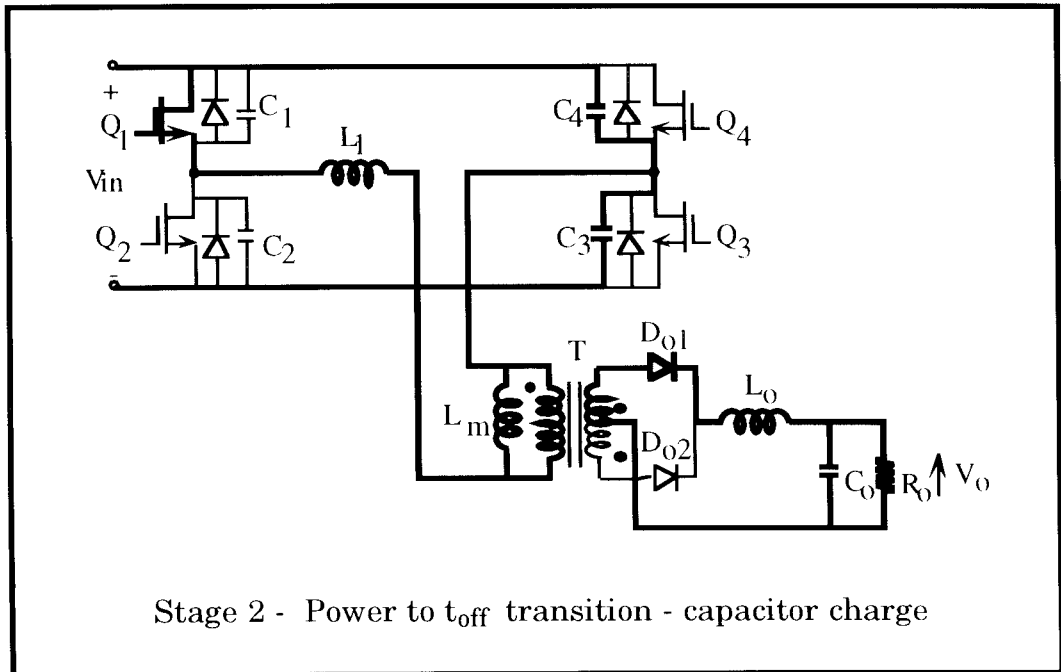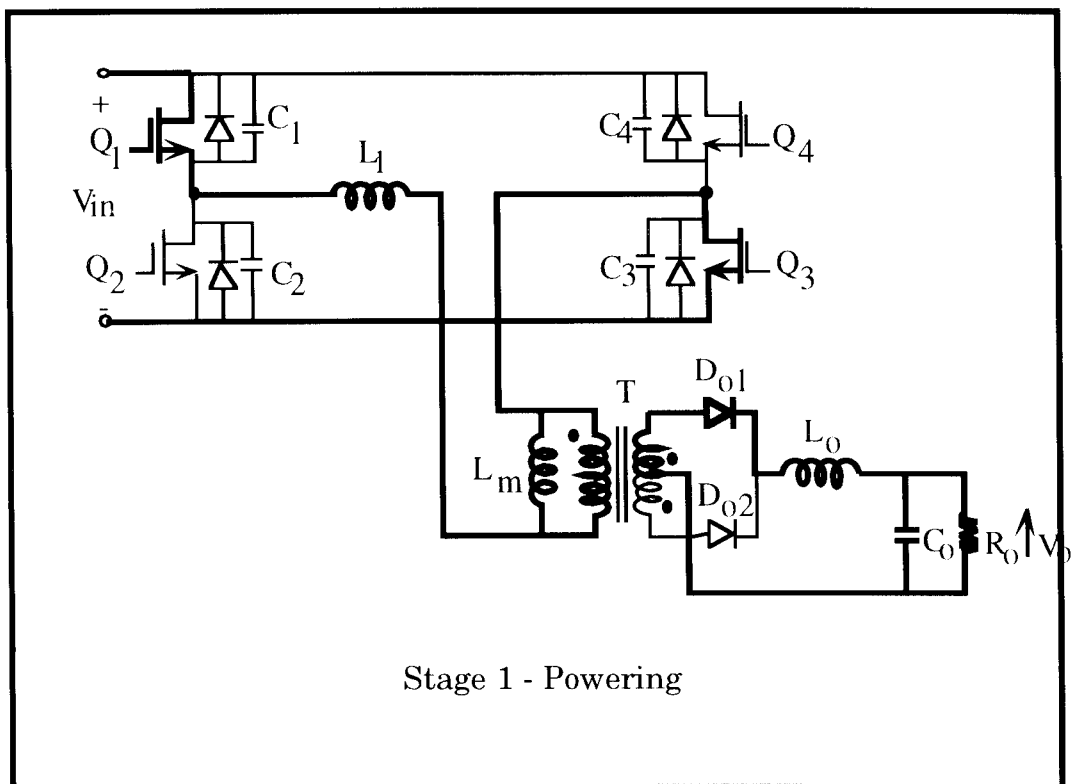

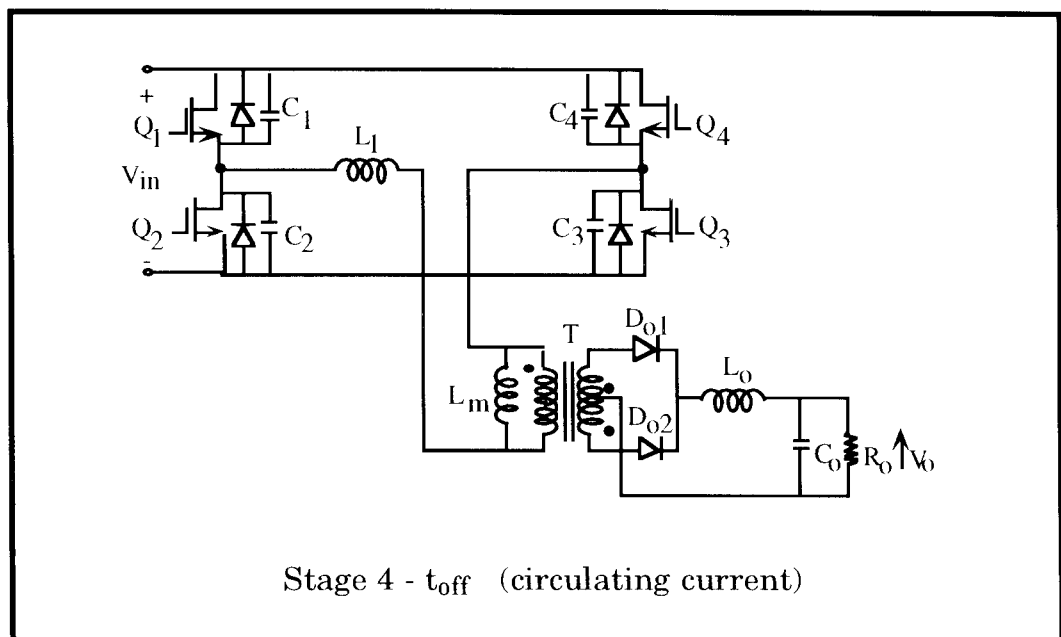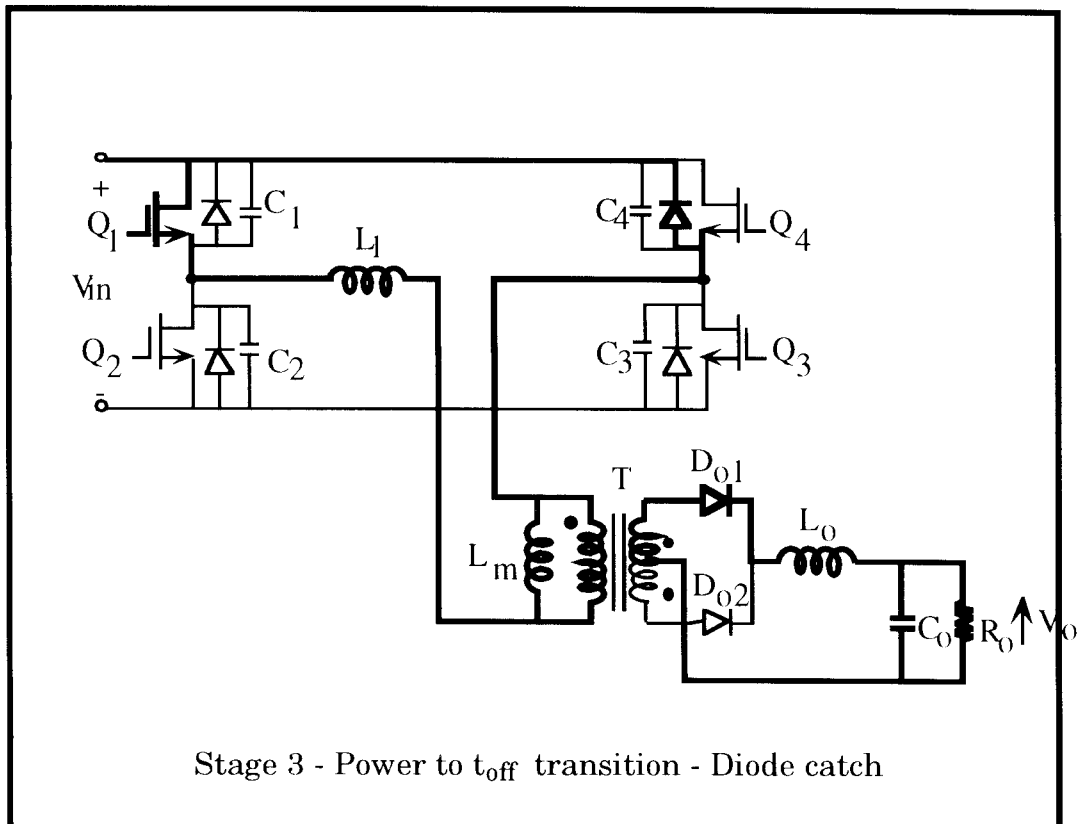


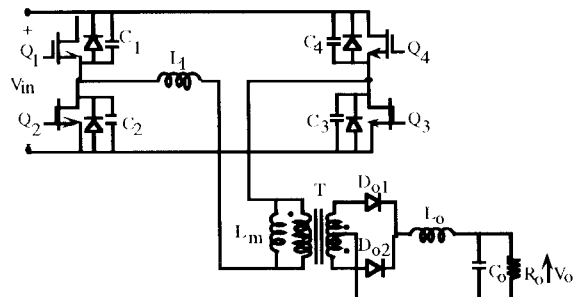

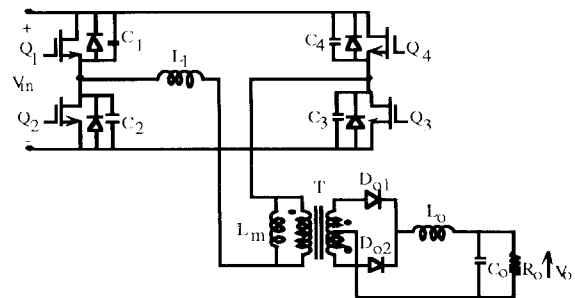Stage 5 -  $t_{off}$  to Power Transition



Back to Power Mode

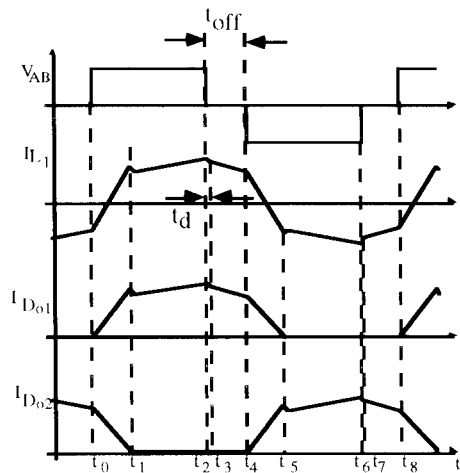

Waveforms

Two rectifier diodes are conducting during  $t_{off}$

## PSPWM DESIGN OVERVIEW

Basic Conventional Phase Shift PWM design equations

$$\frac{I_{off}^2 L_r}{2} \geq \frac{(C_A + C_B) V_{BUS}^2}{2}$$

$C_A + C_B$  = total leg capacitance

or:

$$I_{off} \sqrt{\frac{L_r}{C_A + C_B}} > V_{BUS} \implies I_{off} Z_r > V_{BUS}$$

where the characteristic impedance is defined as usual:

$$Z_r = \sqrt{\frac{L_r}{C_A + C_B}}$$

The transition time (need to be larger than 1/4 of the resonant period

$$t_d \geq \frac{2\pi \sqrt{L_r (C_A + C_B)}}{4}$$





In the conventional scheme,  $L_1$  need to be relatively large to store sufficient energy at low load current . This can be somewhat improved by making the primary current larger (lower  $L_m$  transformers magnetization inductance) .



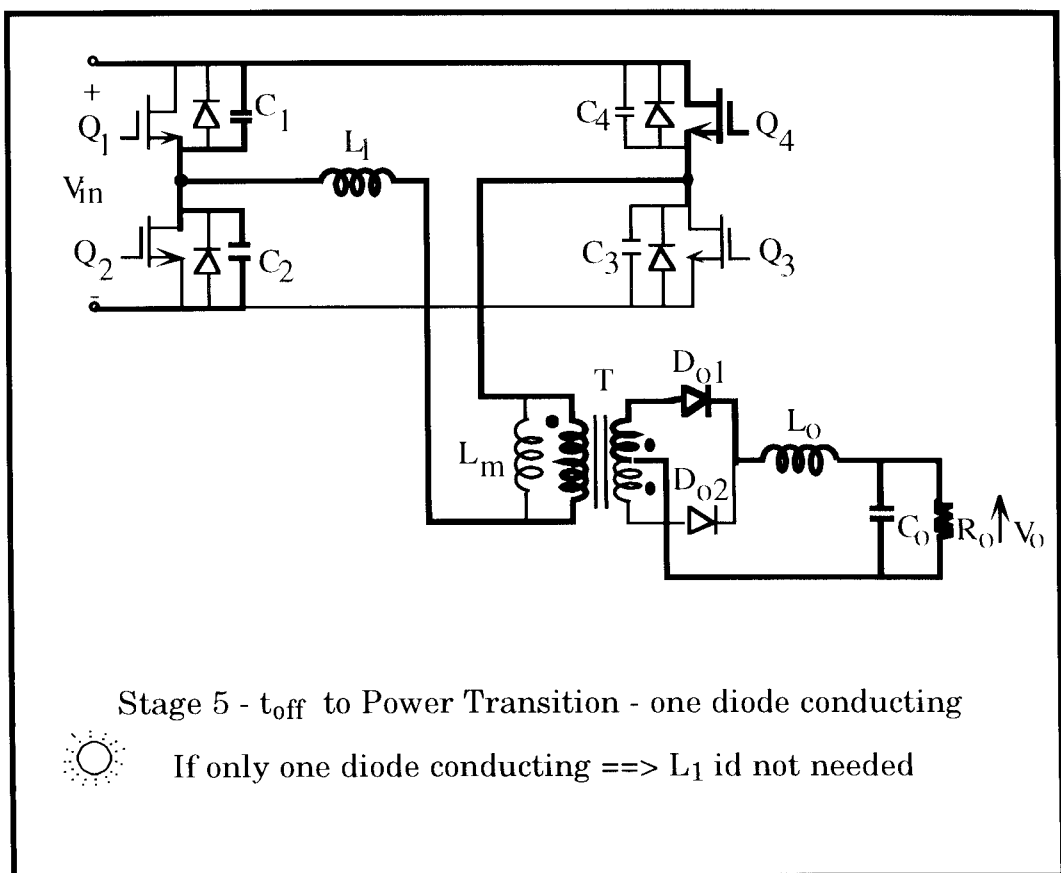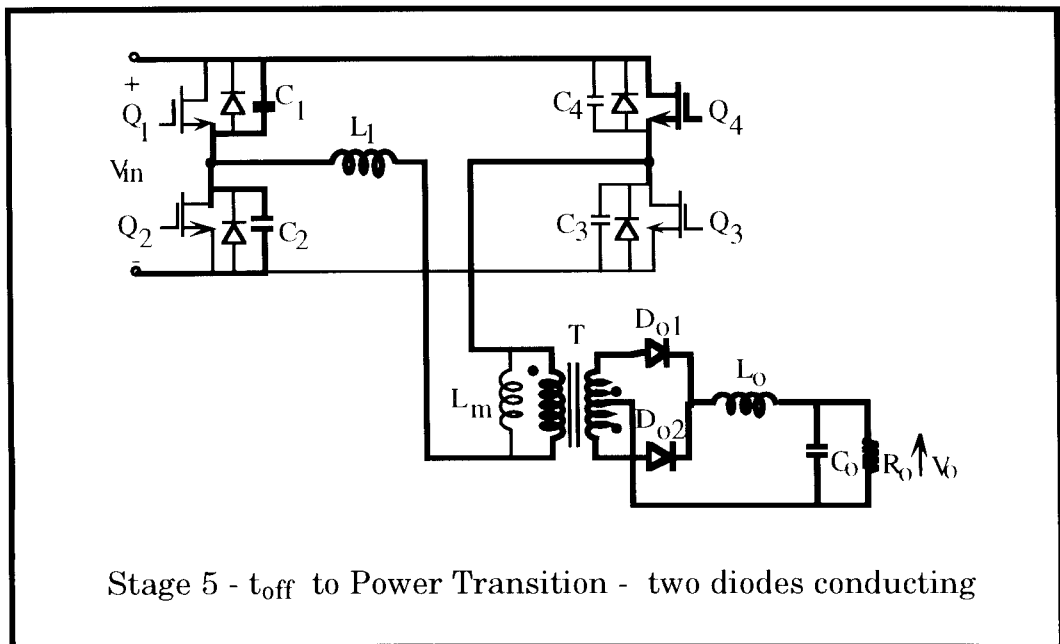
If the short circuit ( two diodes conducting) during  $t_{off}$  is avoided (only one diode conducts )  $L_1$  can be small since the energy comes from the secondary





## RESIDUAL ISSUES IN PSPWM


### 1. Circulating Current

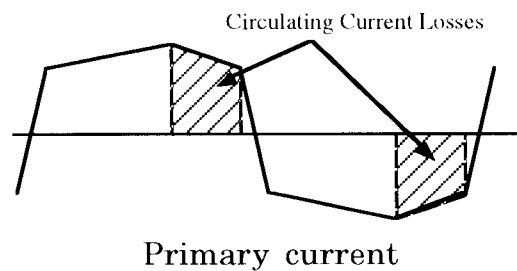

- Thermal design of power stage for duty cycle  $D \Rightarrow 1$   
 $\Rightarrow$  The circulating current at  $D < 1$  not a major problem

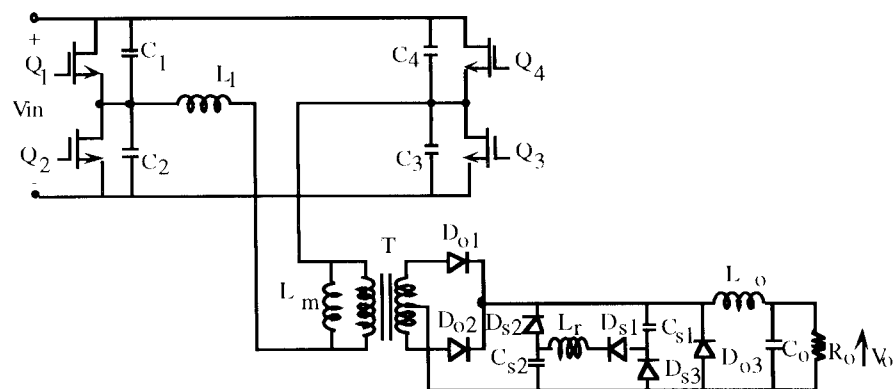
### • Possible Solution

Apply the 'One Way' capacitor to block primary current at  $t_{off}$



Lossless output snubber SNB16 [18]

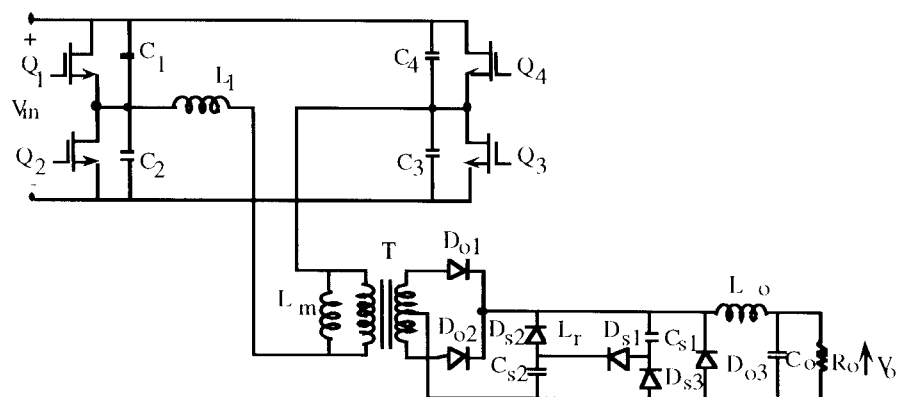
- $L_r$  and  $C_s$  form a resonant circuit



Modified lossless output snubber SNB17 [19]



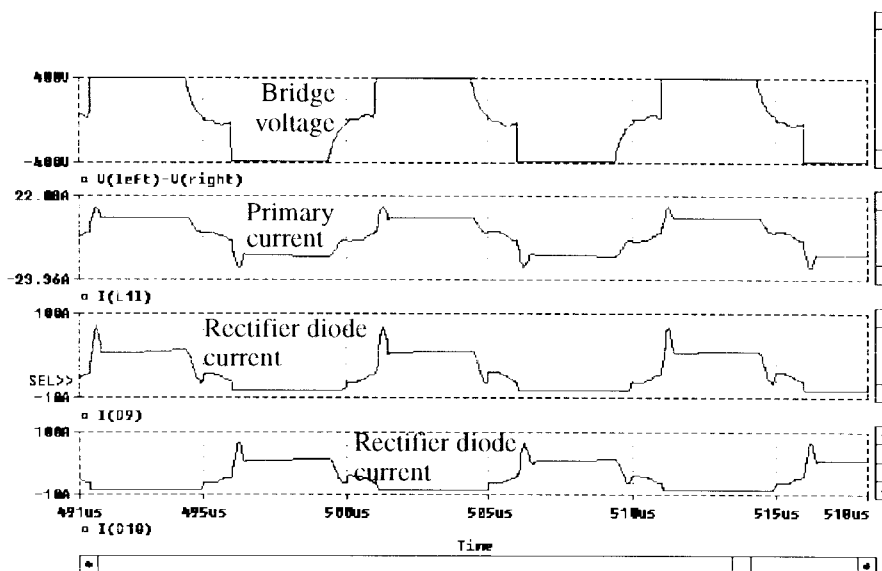Resonant inductor can be moved to primary




Basic waveforms of SNB17 (Simulation)


- Suitable for IGBT (zero current at  $t_{off}$  combats current tail)

## RESIDUAL ISSUES IN PSPWM
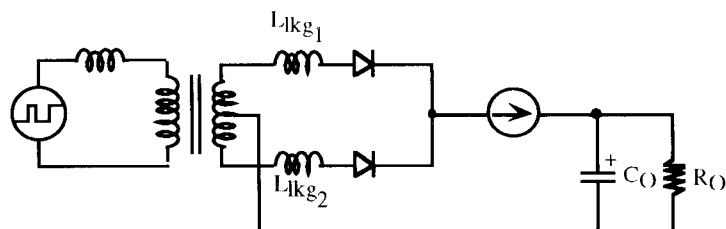
### 2. Rectifier's diodes reverse recovery



Leakage inductance at secondary

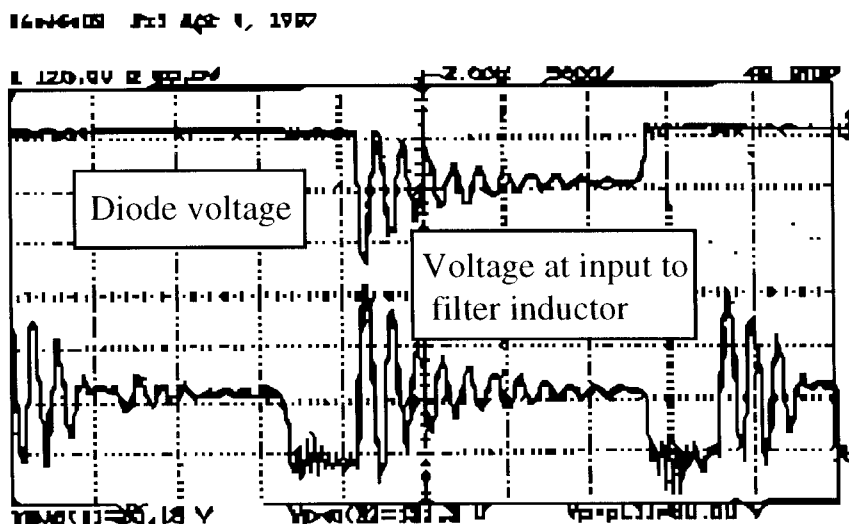



Experimental waveforms

- Greatly influenced by transformer leakage

## RESIDUAL ISSUES IN PSPWM

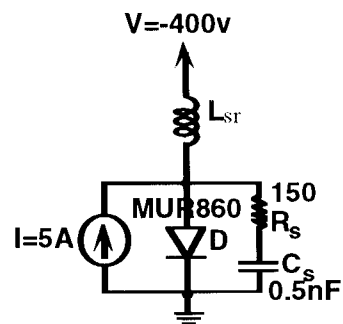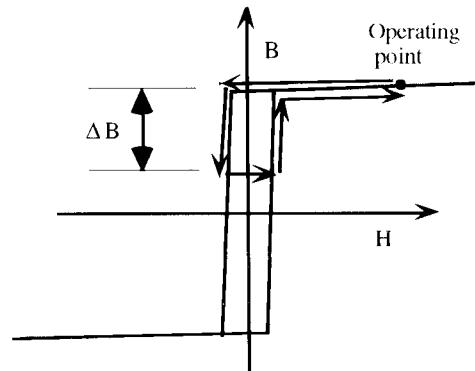
### 2. Rectifiers' diodes reverse recovery

- Possible Remedy -> Saturable reactor (SR) [7, 8, 9, 14, 43]



Simulation Circuit

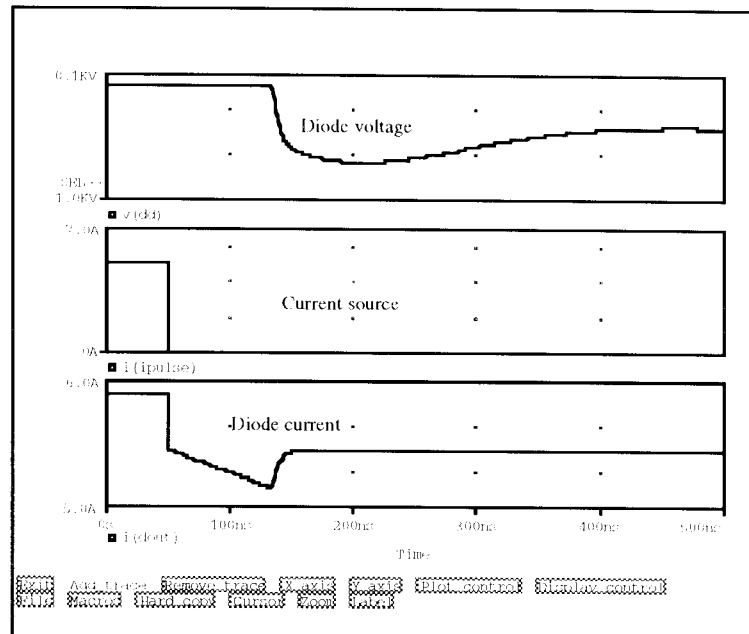- Using fast diode
- Current source establishes the forward current and abrupt change
- $L_{sr}$  emulate "large" back inductance



Simulation waveforms ( $L_{sr} = 50\mu H$ )

## RESIDUAL ISSUES IN PSPW

### 2. Rectifiers' diodes reverse recovery

- Design equations overview

Magnetic flux swing (one sided)

$$\Delta B = \frac{VT}{2 n A_c}$$

VT = volt-second across SR

$A_c$  = core effective cross section area


n = number of turns

For Amorphous Alloy 2714AF (Allied):

Core Losses :  $P_{core} (W/Kg, mW/gr) = 10^{-6} (f_s)^{1.73} (\Delta B)^{1.88}$

B = Magnetic flux (T) ;  $f_s$  = Switching frequency (Hz)

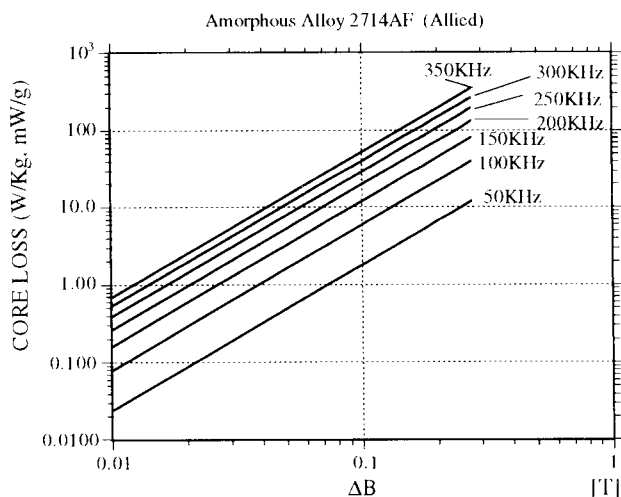$\Delta B = (P_{core} / (10^{-6} (f_s)^{1.73}))^{1/1.88}$




👁 Extrapolated from Allied's data (originally given up to 200KHz)

## RESIDUAL ISSUES IN PSPWM [42, 43]

### 2. Rectifiers' diodes reverse recovery

- Implementation in PSPWM

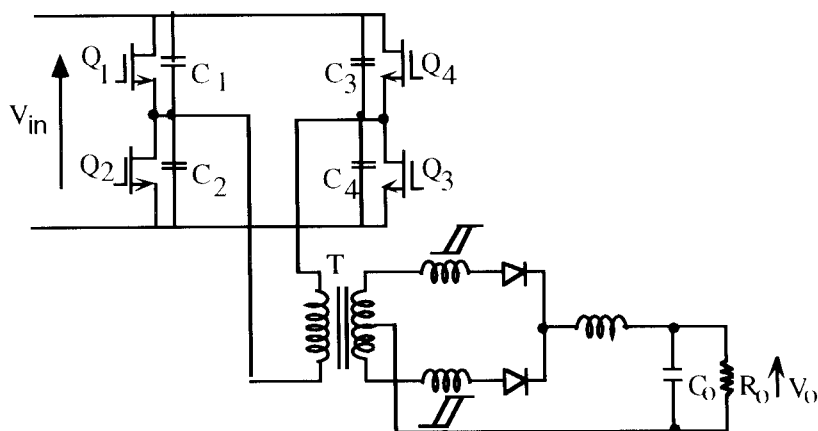


PSPWM with SR at output (SNB18)


## RESIDUAL ISSUES IN PSPWM

### 2. Rectifiers' diodes reverse recovery

- Implementation in PSPWM

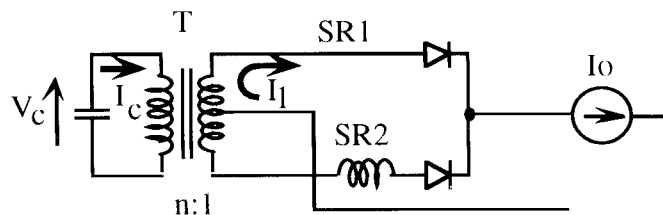


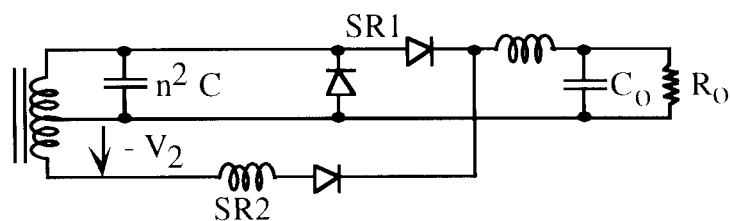
Situation at first commutation instance (power to  $t_{off}$ )






Equivalent circuit during  $t_{off}$

## RESIDUAL ISSUES IN PSPWM


- Theoretical considerations

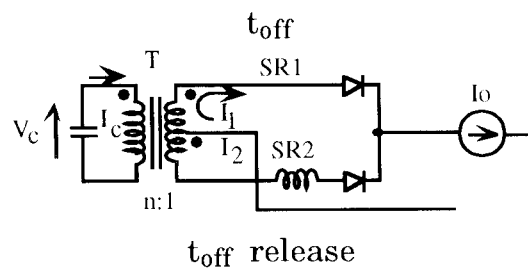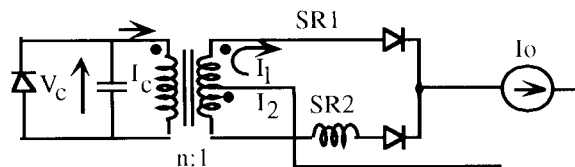



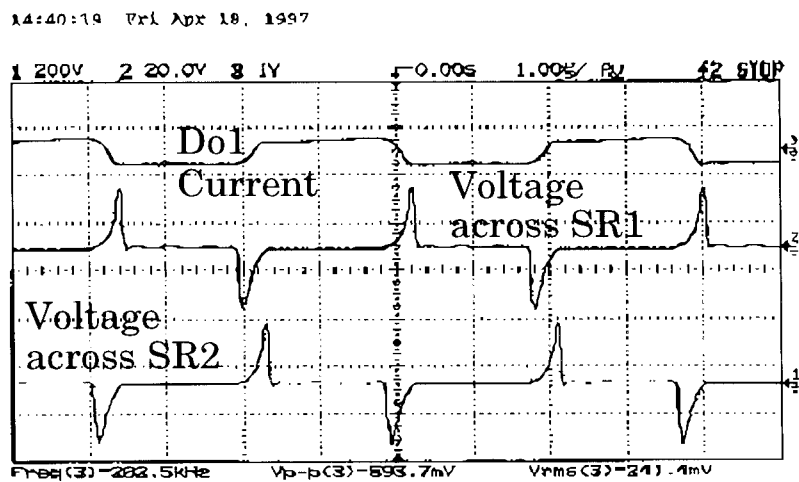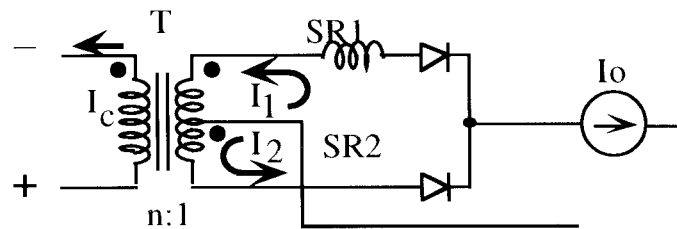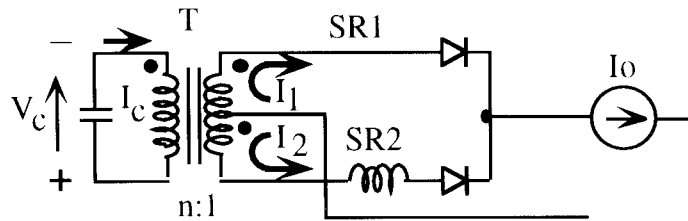

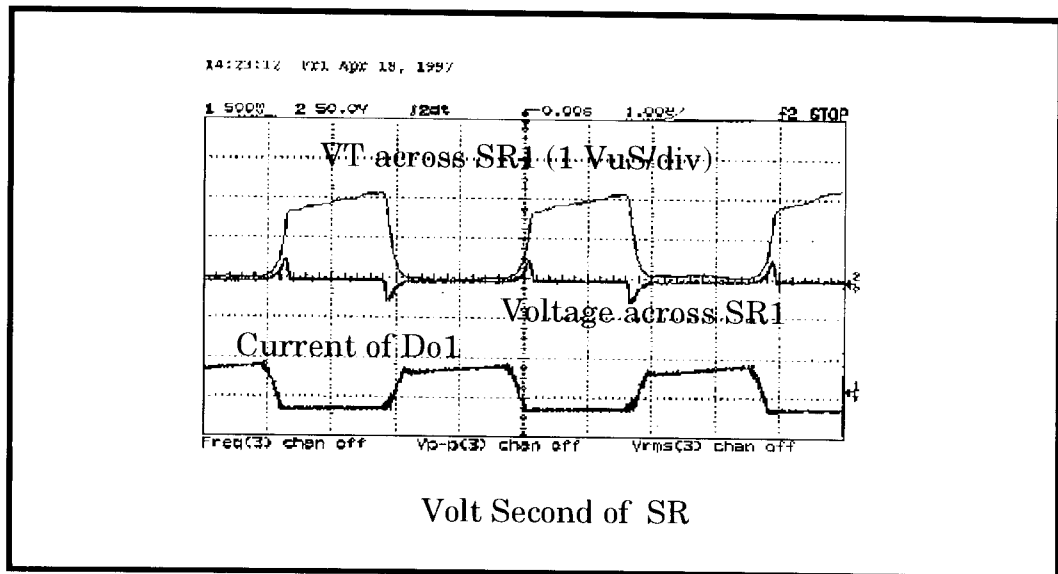Current through rectifier leg and voltage across SR



## Design Guidelines

1. Choose SR to keep core losses low say : 50 mW/gr
2. Estimate VT


Example: Diode reverse voltage 100V

$$t_{rr} \approx 100 \text{ nSec} \Rightarrow VT \approx 10 \text{ V}\mu\text{S}$$

For Amorphous Alloy 2714AF (Allied):

$$P_{core} (\text{W/Kg, mW/gr}) = 10^{-6} f^{1.73} \Delta B^{1.88}$$

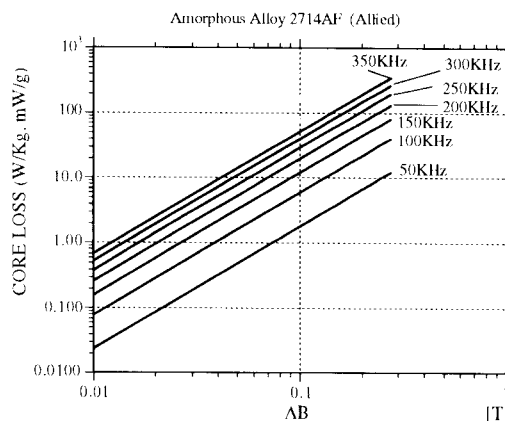Assume  $P_{core} = 50 \text{ mW/gr}$ ;  $f = 270 \text{ KHz}$



From loss equation  $\Rightarrow \Delta B = 0.125T$

$$\text{From } \Delta B = \frac{V T}{2 n A_c} \quad \Rightarrow \quad A_c = 0.4 \text{ cm}^2$$

Using MP1906P-4AF (Allied):

OD = 21mm; ID = 10mm;  $A_c = 0.16 \text{ cm}^2$ ;  $n=1$ ; 6.1 gr



Need at least 3 units per leg



Effective frequency is much higher than switching frequency



Being a small body (small surface area), might get very hot. 4 units per leg were used in experimental converter.

## Experimental PSPWM Converter

Transformer: Payton 3000W T250-12-4C

Nominal Operating frequency = 350KHz

Input Voltage = 360 -390 Volt

Max.  $V_T = 864 \text{ V}\mu\text{S}$

Primary to half secondary 6:1

Primary Max rms current: 11 Amp


Dielectric strength (primary to secondary) 2500 Vrms

Dielectric strength ( secondary to core ) 500 Vdc


Estimated power loss 65W (@ 60°C base plate)

Estimated hot spot 110°C


Mechanical dimensions 88\*65\*30(h) mm

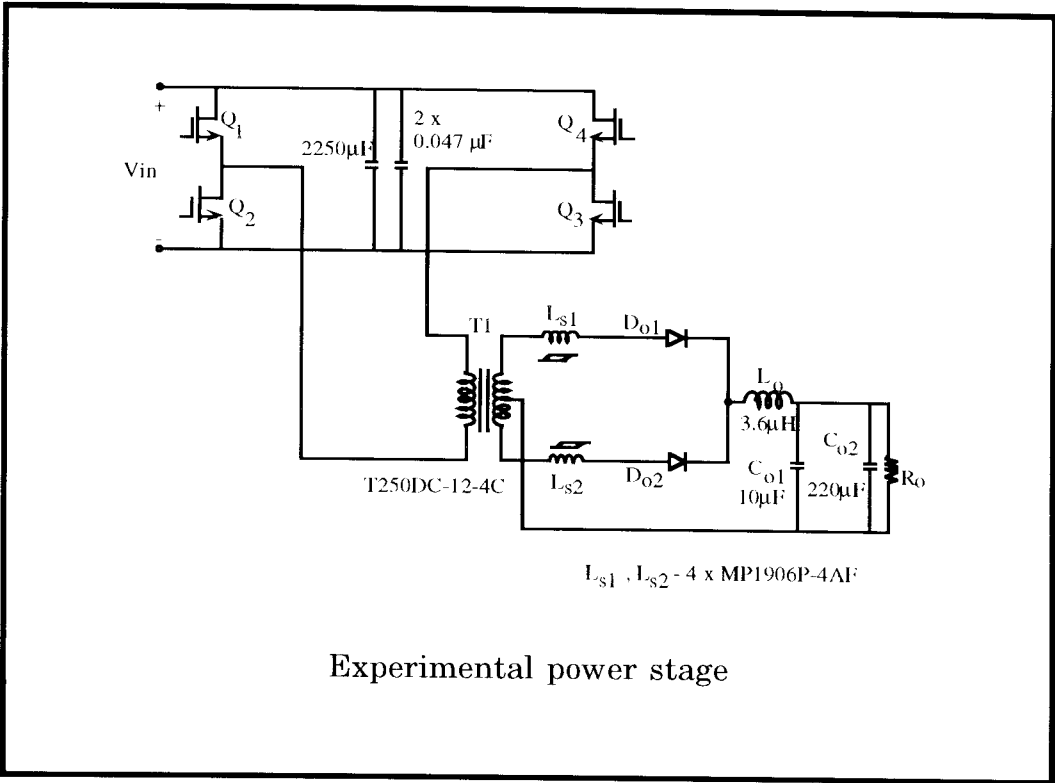


Experimental Results

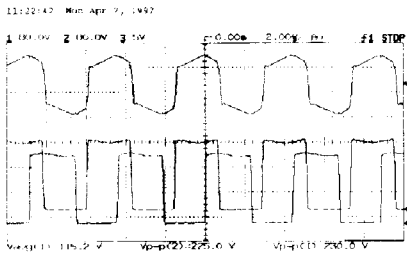

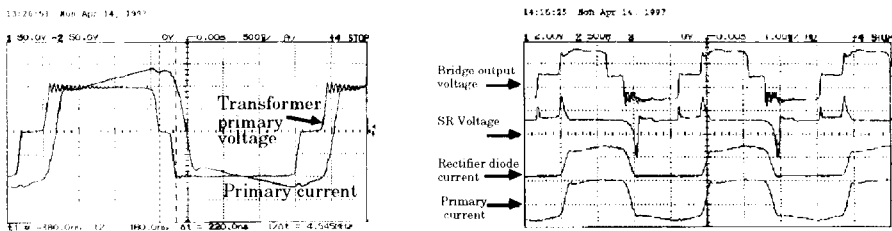
Primary current (upper) and leg voltages (lower)




In circuit SR Performance`

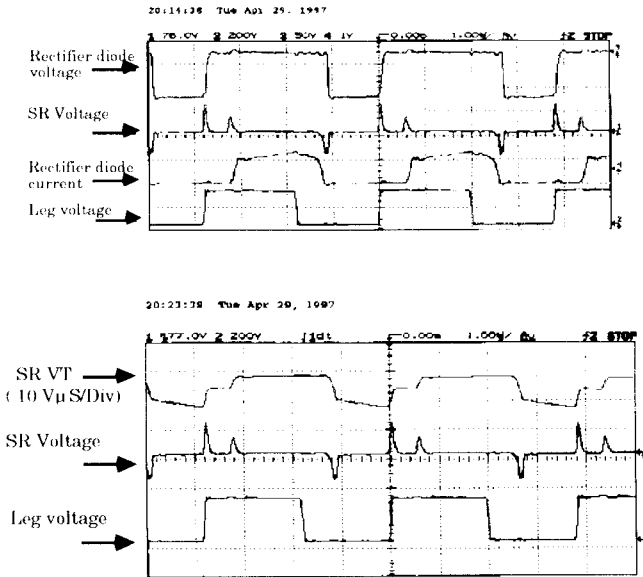

## Experimental Results

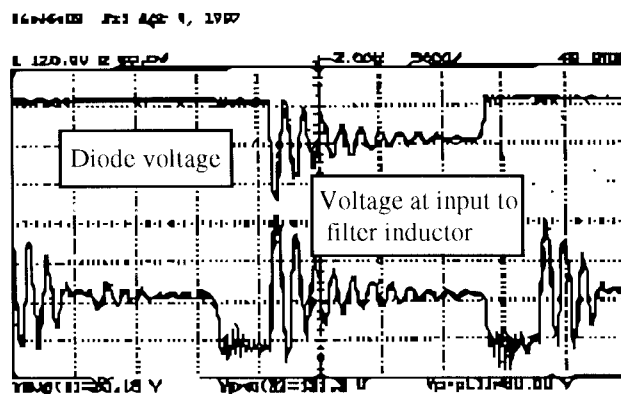


Experimental waveforms (no SR snubber)

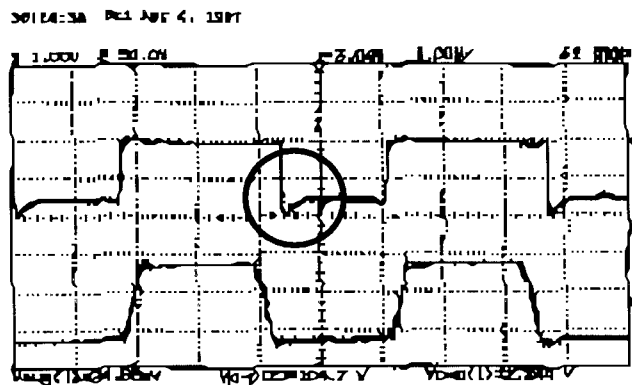

Rectifier diode voltage (upper trace) and current (lower) with amorphous core


- Some overshoot due to energy stored in SR
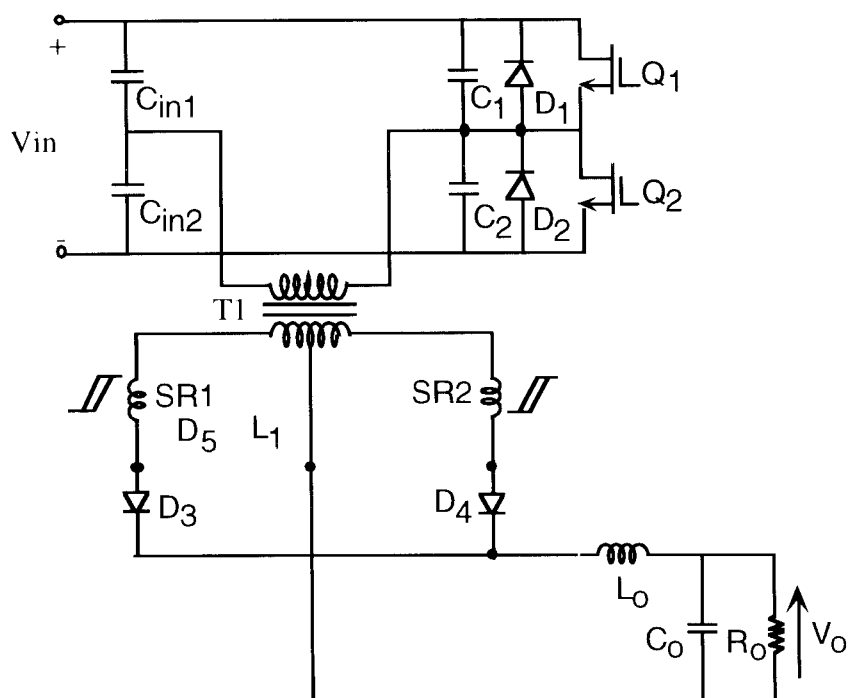
## Improved magnetic snubber for rectifier diodes in DC/DC converters



- Basic solution [42,43]


## Dependence on L - Simulation

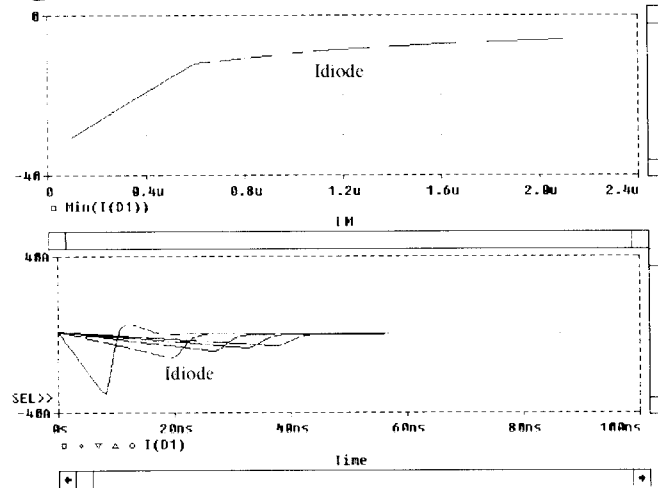

Diode reverse recovery switching waveforms



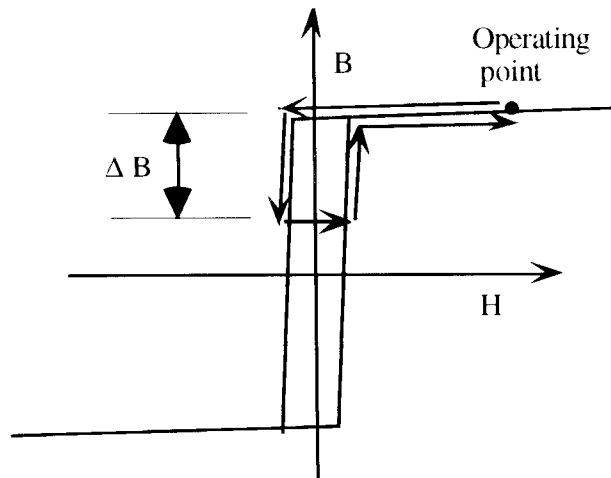
Actual reverse recovery time is a function of series inductance



Long reverse recovery time will increase core losses



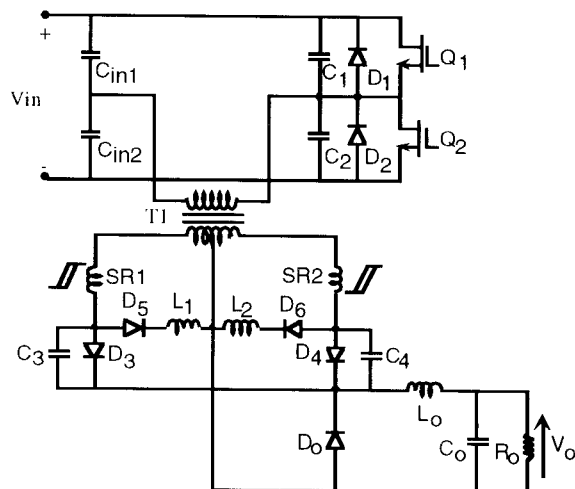
## Improved magnetic snubber for rectifier diodes in DC/DC converters [44]



Added elements:  $C_3$ ,  $C_4$ ,  $D_0$ ,  $L_1$   $D_5$  &  $L_2$   $D_6$

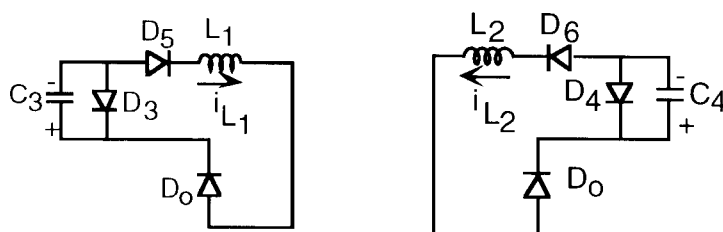-> Extra resonant circuit to sweep out stored charge




The stored charge of the diode  $D_3$  ( $D_4$ ) is pulled out rapidly ; therefore  $(t_{rr}) D_3$  and  $(t_{rr}) D_4$  decrease and hence core losses in SR1 and SR2 also reduce.

## Chapter 8
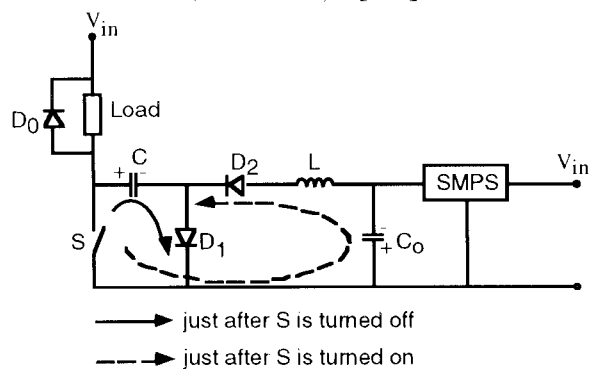
### COMBINING SNUBBER AND POWER SUPPLY FUNCTIONS

Turn-off snubber with energy recovery  
back to the input bus or into a local power supply  
(SNB20) [39]



$C$  = Snubber capacitor

$C_0$  = Filter capacitor


Negative polarity of voltage across  $C_0$  !

- The main purpose of the device: turn-off snubber
- Additional appointment: local power supply



Watch for power level (in PS applications), might be too high
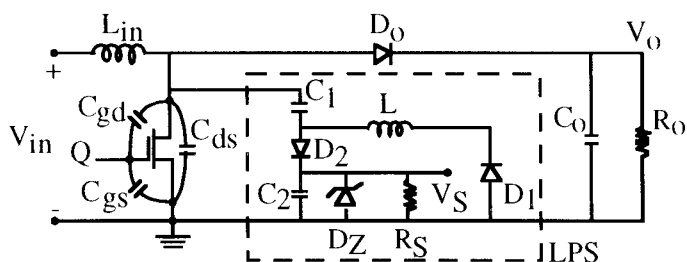
## A local power supply with turn off snubber features [47]



LPS - local power supply

$R_S$  - load resistance

$C_2 \gg C_1$ ;  $DZ$  - Zener diode

- Positive polarity of output voltage  $V_S$
- The main purpose of the device: A local power supply.


Secondary objective: turn-off snubber

## A local power supply with turn off snubber features

Main assumptions of analysis


1. Ideal diodes and ideal transistor. Parasitic capacitances of MOSFET are taken into account. It is assumed that these capacitances are linear.
2.  $L_{in}$ ,  $C_0$  and  $C_2$  are infinitely high

Equivalent circuits

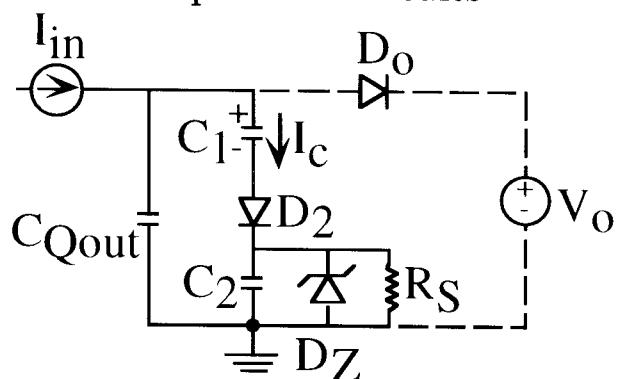


- $t_0$ - $t_1$ : energy injection into LPS

Equivalent circuits

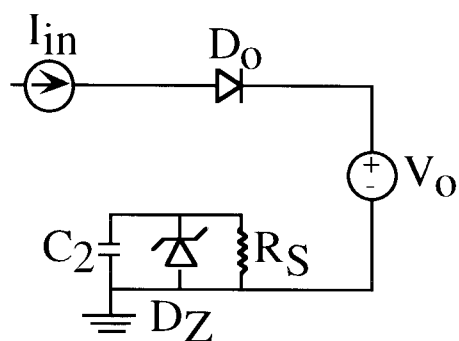


- $t_1$ - $t_2$ : no interconnection between the processes in the LPS and in the converter

## Equivalent circuits

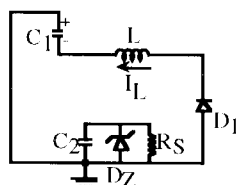


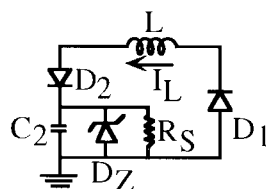$t_2$ - $t_3$ : energy transfer from the capacitor  $C_1$  to the inductor  $L$



- $t_3$ - $t_4$ : energy transfer from the inductor  $L$  to the  $C_2$  -  $D_2$  -  $R_S$  circuit

## Current and voltage waveforms

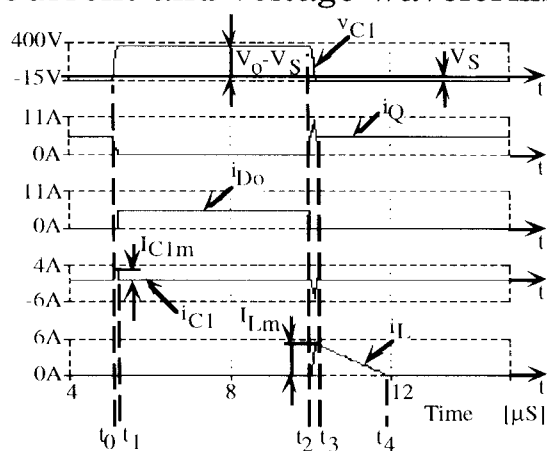

## Proposed Local Power Supply (LPS) connected in a boost converter

Main relationships


Energy injected to LPS during one switching period

$$E = \frac{C_1 V_0^2}{2} = V_s (I_s + I_Z) T_s$$

$$I_s + I_Z = f_s C_1 \frac{V_0^2}{2 V_s}$$

$$I_{s \max} = f_s C_1 \frac{V_0^2}{2 V_s} \quad (\text{when } I_Z=0)$$
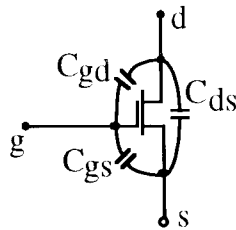
## LPS loaded by the MOSFET's controller driver



The average input current to the gate of the MOSFET

$$I_{g \text{ av}} = C_{Qin} V_{gs} f_s = k I_{s \max}$$

$k$  = fraction of  $I_s$  used to power the gate ( $k < 1$ )

The required value of  $C_1$

$$C_1 = \frac{2 V_{gs}}{k V_0} \left[ C_{gd} \left( 1 + \frac{V_{gs}}{V_0} \right) + C_{gs} \frac{V_{gs}}{V_0} \right]$$

If  $V_{gs} \ll V_o$

$$C_1 \approx \frac{2}{k} \frac{V_{gs}}{V_o} C_{gd}$$




$C_1$  is of the same order of magnitude as the parasitic capacitences of the transistor!



If additional power is required (e. g. DC fans)  $C_1$  will be larger.
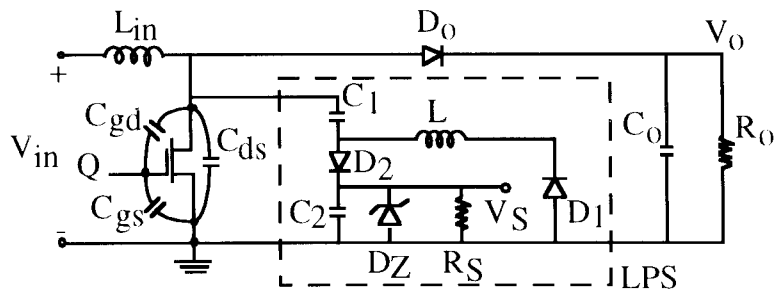
## Experimental boost converter with proposed LPS



$Q=IRFP460$ ;  $D_0=MUR460$ ;  $D_1=1N5819$ ;  $D_2=MUR160$


Power stage:

$f_s=100kHz$ ;  $L_{in}=1mH$ ;  $L=24.2\mu H$ ;  $C_0=1mF$ ;  $V_o = 260V$ ;  $P_o=85W$

Snubber:


$V_S=15V$ ;  $C_2=100\mu F$ ;  $R_S=10-64\Omega$ ;  $C_1=1.0-5.5nF$

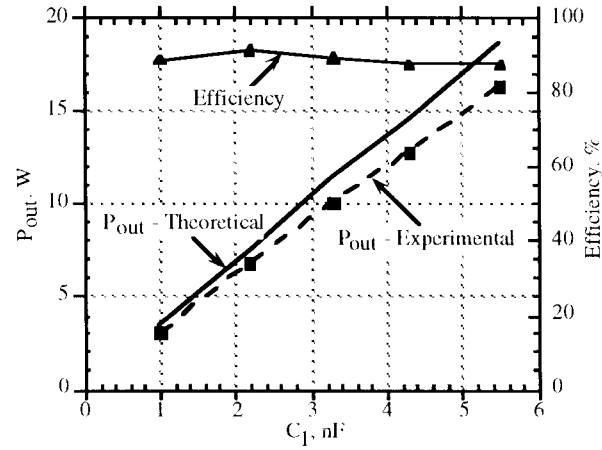Output power and efficiency as functions of the charge pump capacitor C<sub>1</sub>




$$P_{out(theor)} = f_s E = \frac{f_s C_1 V_0^2}{2}$$

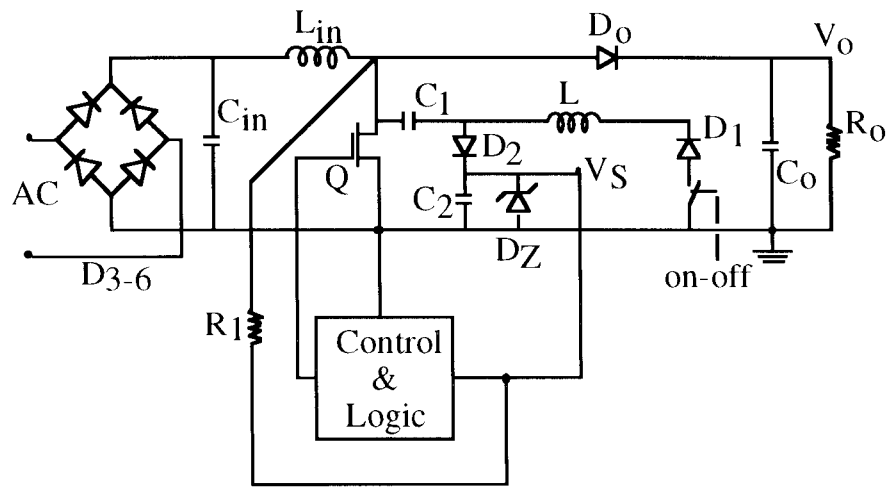Application of proposed local power supply in a boost APFC




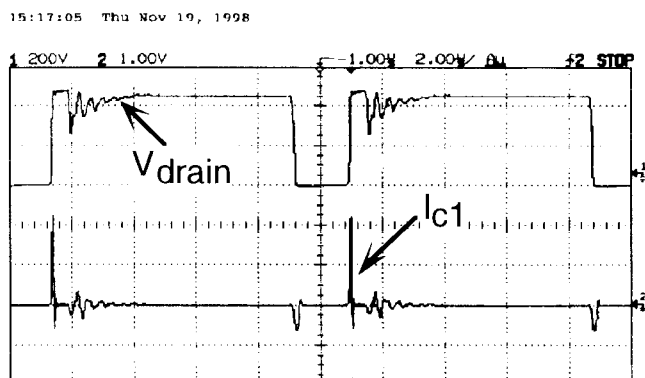
## Experimental waveforms of the LPS operating in a soft switched APFC circuit



$C_1 \approx 220\text{pF}$ ,  $V_{in} = 220\text{V}_{\text{rms}}$ ,  $V_o = 380\text{V}$ ,  $V_s = 12.4\text{V}$ ,  $R_s \approx 170\Omega$

## CONCLUSIONS

- Passive lossless snubbers can improve performance of switch mode systems:
  - Controlled  $\frac{di}{dt}$  and  $\frac{dv}{dt}$
  - Increased efficiency at high switching frequency
  - Reduction of voltage and current spikes
  - Relatively low cost
  - High reliability
- The magnitude of the reverse recovery current of the diode may affect performance of the snubber
- Check points to watch:
  - Extra stresses
  - Duty cycle limitation
  - Current limitation



Snubber/LPS combination could be useful in some applications



Methods to increase the snubbing capacitor without increasing LPS power - are now under investigation

## REFERENCES

- [1] L. R. Barbosa, J. B. Vieira Jr., L. C. de Freitas, V. J. Farias, "A family of PWM soft-single-switched converters with low voltage and current stresses", *Proceedings PESC' 97*, pp. 1192-1197.
- [2] L. R. Barbosa, J. B. Vieira Jr., L. C. de Freitas, M. Vilela, V. J. Farias, "A buck quadratic PWM soft-switching converter using a single active switch", *Proceedings PESC' 96*, pp. 69-75.
- [3] S. Ben-Yaakov, "Average simulation of PWM converters by direct implementation of behavioral relationships", *Int. J. Electronics*, vol. 77, no. 5, 1994, pp. 731-746.
- [4] S. Ben-Yaakov, G. Ivensky, O. Levitin, A. Treiner, "Optimization of the auxiliary switch components in ZVS PWM converters", *Int. J. Electronics*, vol. 81, no. 6, 1996, pp. 699-712.
- [5] S. Clemente, A. Dubhashi, B. Pelly, "IGBT characteristics and applications", *IGBT Designer's Manual (IGBT-2, Second Printing)*, International Rectifier, 1991, pp. 93 - 108, AN-983.
- [6] M. Domb, R. Redl, N. O. Sokal, "Nondissipative turn-off snubber alleviates switching power dissipation, second breakdown stress and  $V_{CE}$  overshoot: analysis, design procedure and experimental verification", *Proceedings PESC'82*, pp. 445-454.
- [7] S. Hachamov and S. Ben-Yaakov, "Reduction of reverse recovery losses in soft switched PWM converters by saturable reactors", *Proceedings ICPE'95*, pp. 361-365.
- [8] S. Hamada, T. Mii, E. Hiraki, M. Nakaoka, "Saturable reactor & lossless capacitor-assisted soft-switching asymmetrical PWM DC-DC converter with forward-flyback transformer link", *Proceedings PESC'96*, pp. 100-105.
- [9] S. Hamada, J. M. Sun, T. Shimizu, A. Kanbe, E. Hiraki, M. Nakaoka, "A novel zero-voltage soft-switched asymmetrical PWM DC-DC converter with high-frequency transformer link", *Proceedings PCIM'96*, pp. 275-287.
- [10] X. He, S. J. Finney, B. W. Williams, T. C. Green, "An improved passive lossless turn-on turn-off snubber", *Proceedings APEC'93*, pp. 385-392.

- [11] X. He, S. J. Finney, B. W. Williams, Z. M. Qian, "Novel passive lossless soft-clamped snubber for voltage source inverters", *Proceedings APEC'96*, pp. 200-206.
- [12] X. He, S. J. Finney, B. W. Williams, Z. M. Qian, "Novel passive lossless turn-on snubber for voltage source inverters", *IEEE Trans. on Power Electronics*, vol. 12, no. 1, January 1997, pp. 173-179.
- [13] J. Holtz, S. Salama, K. H. Werner, "A nondissipative snubber circuit for high-power GTO inverters", *IEEE Trans. on Industry Applications*, vol. 25, no.4, July/August 1989, pp. 620-626.
- [14] G. Hua, F. C. Lee, M. M. Jovanovic, "An improved zero-voltage-switched PWM converter using saturable inductor," *Proceedings APEC'91*, pp. 189-194.
- [15] G. Ivensky, D. Sidi, S. Ben-Yaakov, "A soft switcher optimized for IGBTs in PWM topologies", *Int. J. Electronics*, vol. 83, no. 5, 1997, pp. 703-716.
- [16] D. Izvorska, J. Leisten, I. Izvorski, R. Petkov, "Frequency limitation of IGBT devices in energy recovery snubber circuits", *Proceedings PCIM'96*, pp. 585-592.
- [17] I. D. Jitaru, "Soft transitions power factor correction circuit", *Proceedings HFPC*, May 1993, pp. 202-208.
- [18] E. S. Kim, K.Y. Joe, M. H. Kye, Y. H. Kim, B. D. Yoon, "An improved soft switching PWM FB dc/dc converter for reducing conduction losses", *Proceedings PESC'96*, pp. 651-656.
- [19] E. S. Kim, K. Y. Joe, M. H. Kye, Y. H. Kim, B. D. Yoon, "An improved ZVZCS PWM FB DC/DC using energy recovery snubber", *Proceedings APEC'97*, pp. 1014-1019.
- [20] A. Kurnia, H. Cherradi, D. M. Divan, "Impact of IGBT behavior on design optimization of soft switching inverter topologies", *IEEE Trans. on Industry Applications*, vol. 31, no. 2, March/April 1995, pp. 280-286.
- [21] A. Kurnia, O. H. Stielau, G. Venkataramanan, D. M. Divan, "Loss mechanisms in IGBT's under zero voltage switching", *Proceedings PESC'92*, pp.1011-1017.
- [22] N. H. Kutkut and K. W. Klontz, "Design considerations for power converters supplying the SAE J-1773 electric vehicle inductive coupler", *Proceedings APEC'97*, pp. 841-847.

- [23] J. A. Lambert, J. B. Vieira Jr., L. C. de Freitas, M. S. Vilela, V. J. Farias, "A boost PWM soft-single-switched converter without high stresses of voltage and current", *Proceedings APEC'96*, pp. 469-474.
- [24] H. Levy, I. Zafrany, G. Ivensky, S. Ben-Yaakov, "Analysis and evaluation of lossless turn-on snubber", *Proceedings APEC'97*, pp. 757-763.
- [25] N. Mohan, T. M. Undeland, W. P. Robbins, "Power electronics", Second edition, *John Wiley & Sons, Inc.*, 1995, 802 p.
- [26] T. Ninomiya, T. Tanaka, K. Harada, "Analysis and optimization of a nondissipative LC turn-off snubber", *IEEE Trans. on Power Electronics*, vol. 3, no.2, April 1988, pp. 147-156.
- [27] H. Ould-Amrouche, D. Sadarnac, W. Abida, "New soft switching phase shifted PWM technique in DC-AC power supply", *Proceedings PCIM'96*, pp. 707-717.
- [28] R. Petkov, L. Hobson, "Optimum design of a nondissipative snubber", *Proceedings PESC'94*, pp. 1188-1195.
- [29] J. Pinto, A. Pereira, V. Farias, L. Freitas, J. Vieira Jr., "A new boost converter using a non-dissipative snubber", *Proceedings PESC'96*, pp. 397-401.
- [30] L. D. Salazar, P. D. Ziogas, G. Joos, "On the minimization of switching losses in dc-dc boost converters", *Proceedings APEC'92*, pp. 703-708.
- [31] K. M. Smith Jr. and K. M. Smedley, "Engineering design of lossless passive soft switching methods for PWM converters. I. With minimum voltage stress circuit cells", *Proceedings APEC'98*, pp. 1055-1062.
- [32] K. M. Smith Jr. and K. M. Smedley, "Properties and synthesis of passive, lossless soft-switching PWM converters", *Proceedings of the 1<sup>st</sup> International Congress in Israel on Energy Power & Motion Control*, May 1997, pp. 112-119.
- [33] R. Streit and D. Tollik. "High efficiency telecom rectifier using a novel soft-switched boost-based input current shaper", *Proceedings of Intelec'91*, November 1991, pp. 720-726.
- [34] Ching-Junk Tseng and Chern-Lin Chen, "Passive lossless snubbers for DC/DC converters", *Proceedings APEC'98*, pp. 1049-1054.
- [35] Ph. C. Todd, "Snubber circuits: theory, design and application", *Unitrode Corporation*, May 1993, pp. 2-1 - 2-17.

- [36] M. S. Vilela, E. A. A. Coelho, J. B. Vieira Jr., L. C. de Freitas, V. J. Farias, "PWM soft-switched converters using a single active switch", *Proceedings APEC'96*, pp. 305-310.
- [37] K. Wang, G. Hua, F. C. Lee, "Analysis, design and experiment results of ZCS-PWM boost converters", *VPEC Seminar Proceedings*, Blacksburg, Virginia, USA, 1994, pp. 251-256.
- [38] K. Wang, F. C. Lee, G. Hua, D. Borojevic, "A comparative study of switching losses of IGBT's under hard-switching, zero-voltage-switching and zero-current-switching", *Proceedings PESC'94*, pp. 1196-1204.
- [39] B. W. Williams, "Power electronics. Devices, drivers, applications, and passive components", Second edition, *McGraw-Hill, Inc.*, 1992.
- [40] E. H. Wittenbreder, V. D. Baggerly, H. C. Martin, "A duty cycle extension technique for single ended forward converters", *Proceedings APEC'92*, pp. 51-57.
- [41] L. R. Barbosa, J. B. Vieira Jr., L. C. de Freitas, V. J. Farias, "A boost PWM soft-single-switched converter", *Proceedings PESC'98*, pp. 401-406.
- [42] R. Farrington, M. M. Jovanovic, F. C. Lee, "A new family of isolated zero-voltage-switched converters", *Proceedings PESC'91*, pp. 209-215.
- [43] S. Hamada and M. Nakaoka, "Analysis and design of a saturable reactor assisted soft-switching full-bridge DC-DC converter", *Proceedings PESC'91*, pp. 155-162.
- [44] K. Harada, Y. Ishihara, T. Todaka, "An improved magnetic snubber circuit for the diode reverse recovery in DC-to-DC converters", *Proceedings PESC'98*, pp. 701-706.
- [45] J. A. Lambert, J. B. Vieira Jr., L. C. de Freitas, L. R. Barbosa, V. J. Farias, "A boost PWM soft-single-switched converter with low voltage and current stresses", *IEEE Trans. on Power Electronics*, vol. 13, no.1, January 1998, pp. 26-35.
- [46] Ching-Junk Tseng and Chern-Lin Chen, "A passive lossless snubber cell for nonisolated PWM DC/DC converters", *IEEE Trans. on Industry Electronics*, vol. 45, no. 4, August 1998, pp. 593-601.
- [47] S. Ben-Yaakov, I. Zeltser, G. Ivensky, "A resonant local power supply with turn off snubber features", *Proceedings APEC'99*.

