

A collage background for the title slide. It includes a group of people in business attire, a close-up of a circuit board, a large industrial power transformer, and a woman wearing glasses and talking on a mobile phone.

Study of Auxiliary Power Solution with High Input Voltage

Presenter : Steel Huang
Date: 6/18 2014

仙童™



Agenda

- Background
- Two Traditional Solutions Introduction
- Phase Cut Regulator Introduction



Background - Application Area

Smart Meter:



Industrial/Solar:




Input Specification:

- 1) Single Phase:
85V~450VAC
- 2) 3 Phases:
45V~720VAC



Background - Design Challenge (1)

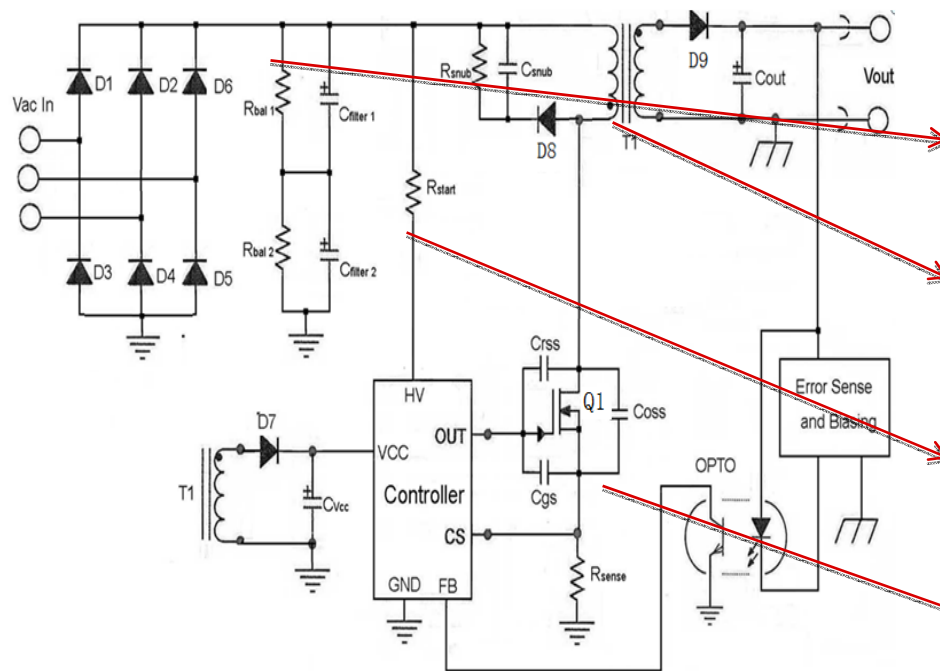

- 1) Bulk-cap:**
Must use 2 or 3 bulky cap and relevant balance circuit.
- 2) Transformer design :**
The duty cycle is very small in high line.
- 3) Startup circuit :**
Startup current is difficult to balance due to wide range input voltage.
- 4) HV switching circuit:**
Difficult to balance high switching loss and low conduction loss.



Background - Design Challenge (2)

1) Big Space and Circuit Complexity

- a) Need 2 or 3 Bulk-caps and relevant balance circuit
- b) Complex transformer design

2) Low Efficiency


- a) Need use HV MOSFET , big conduction loss and switching loss.
- b) High DC link voltage, small duty cycle setting, lower system efficiency.
- c) High DC link voltage, high VF secondary diode , big conduction loss.

3) High Cost

- a) Device is expensive if adopting single MOSFET structure.
- b) Too many components if adopting Cascode FET or ESBC™ structure.



- Background
- Two Traditional Solutions Introduction
- Phase Cut Regulator Introduction

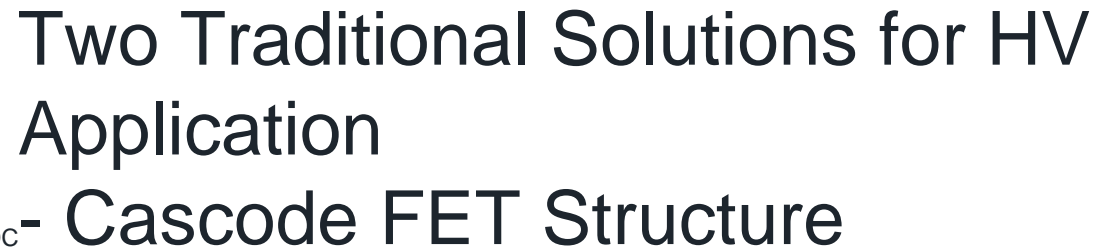[illegible]

- 1) 2 Bulk –caps
- 2) Resistor balance circuit
- 3) 2 MOSFETs in series
- 4) Upper MOSFET driver circuit
- 5) Transformer
- 6) Feedback circuit



Cascode FET Structure - Advantage and Disadvantage

Advantage:

- 1) MOSFET could use popular ones.

Disadvantage:


- 1) Need 2 or 3 Bulk-cap and balance circuit.
- 2) Must use 2 MOSFETs.
- 3) More components
- 4) The switching frequency could not be too high, suggest below 50KHz.

Proposal Solution:

- 1) FSL Series + discrete MOSFETs
- 2) Three in one solution



FSL Series + discrete MOSFET solution

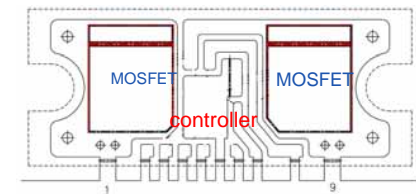

Integrated MOSFET solution



Two Traditional Solutions for HV Application - ESBC™ structure

What's the ESBC™ device?


◆ ESBC™ (Emitter Switched Bipolar/MOSFET Cascode) device is actually a Emitter Switching, which stack a high voltage bipolar transistor with a low voltage MOSFET.

Marriage of Bipolar High-Voltage with Low-Voltage MOSFET


- ◆ Negates weaknesses of both devices while taking advantage of their strengths
- ◆ Results in a higher breakdown voltage
- ◆ Minimum switching loss and conduction loss
- ◆ Easy to drive, allows use of standard controllers



ESBC™ Device's Structure

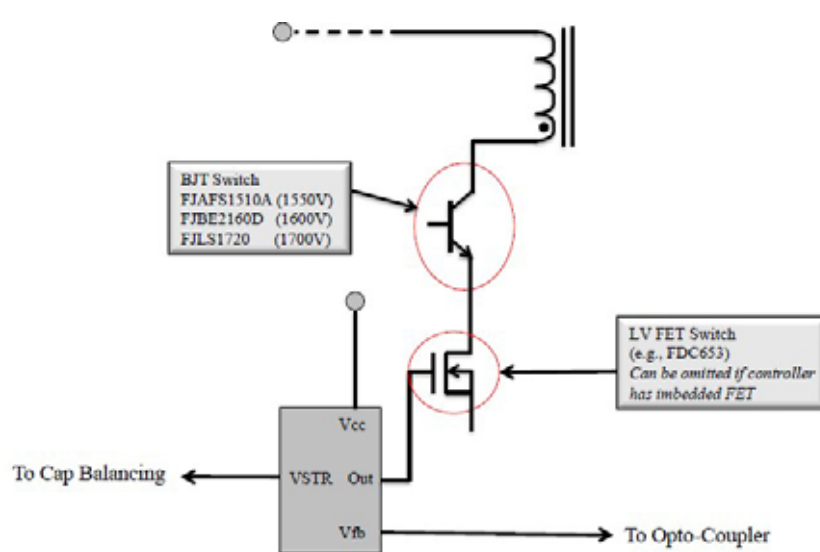

ESBC™ Device's basic structure

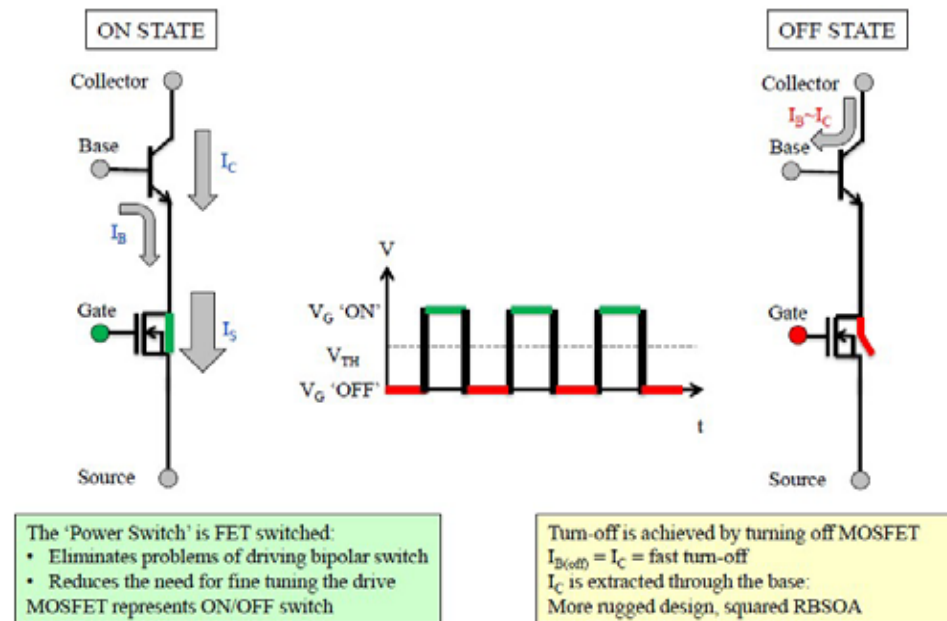


ESBC™ Device's on/off status




2 kinds of Driver Circuit of ESBC™

Bias supply drive

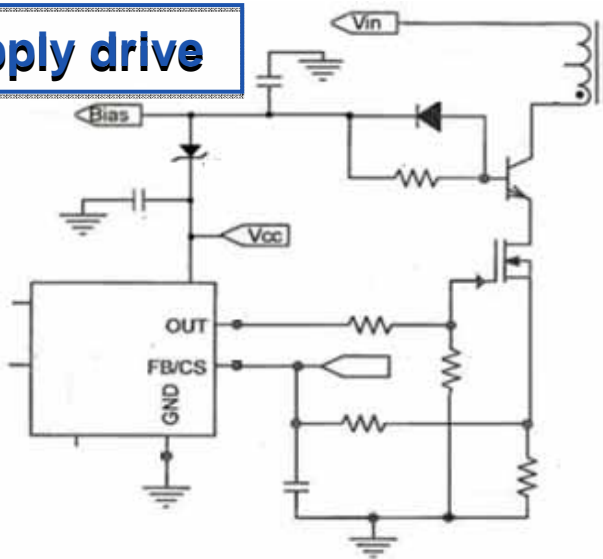

Proportional drive

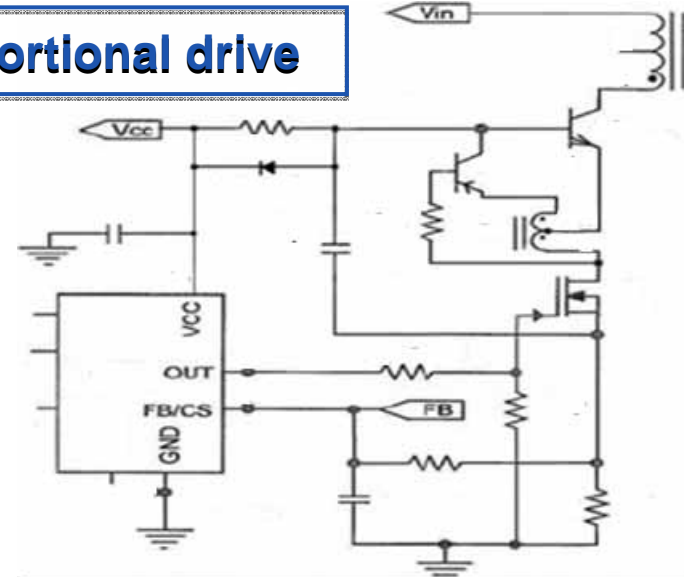

For ESBC™ application, we must consider if the bipolar can provide a proper current gain H_{fe} , this H_{fe} not only guarantee the saturation conduction of the transistor at turn on, but also decrease the storage time of transistor at turn off. So, Proportional transformer drive is a good choice. It can guarantee the transistor's H_{fe} not changing at no load or high load. generally, we advice DC bias supply drive use under low power condition (such as <10Watt), for high power, adopting proportional drive is the best solution.



ESBC™ Device's Structure - Advantage and Disadvantage

Advantage:

- 1) Easy to drive big power

Disadvantage:

- 1) Also need 2 or 3 Bulk-caps and balance circuit.
- 2) The driver circuit is a little bit complex.

Proposal solution:

- 1) FJAFS1510A (1550V,6A) + FDMA86551L(60V,7.5A)



Comparison of Two Traditional Solutions (1) - Efficiency

Solutions	Vin/Vout	Devices	Freq.	Balance Circuits	60Vac	220Vac	380Vac	600Vac
Cascode FET	45Vac-600Vac/ 15V/670mA	FSL137MRIN+ FQP4N90C	67KHz	Yes	63.41%	78.26%	76.92%	71.16%
ESBC™	45Vac-600Vac/ 15V/670mA	FJBE2160D+ FDC653N	67KHz	Yes	67.21%	79.56%	76.15%	65.68%

From above efficiency data ,we could see the different point is at the low line and high line , but
In middle area, the efficiency is almost same.



Comparison of Two Traditional Solutions (2) - General Features

- 1) For Cascode FET solution, there need two MOSFETs and upper MOSFET driver circuit, the switching loss is big.
- 2) For ESBC™ solution, it just needs one bipolar transistor and a low side MOSFET, it can driver more big power, but the driver circuit is a little complex.


This 2 kinds of solutions all need 2 or 3 bulk-caps and relative balance circuit, this need more big space and more cost. So could we find some simple methods to solve these problems? Could we just use one bulk-cap? Could we adopt more simple driver circuit?



- Background
- Two Traditional Solutions Introduction
- Phase Cut Regulator Introduction




What's Phase Cut Regulator?

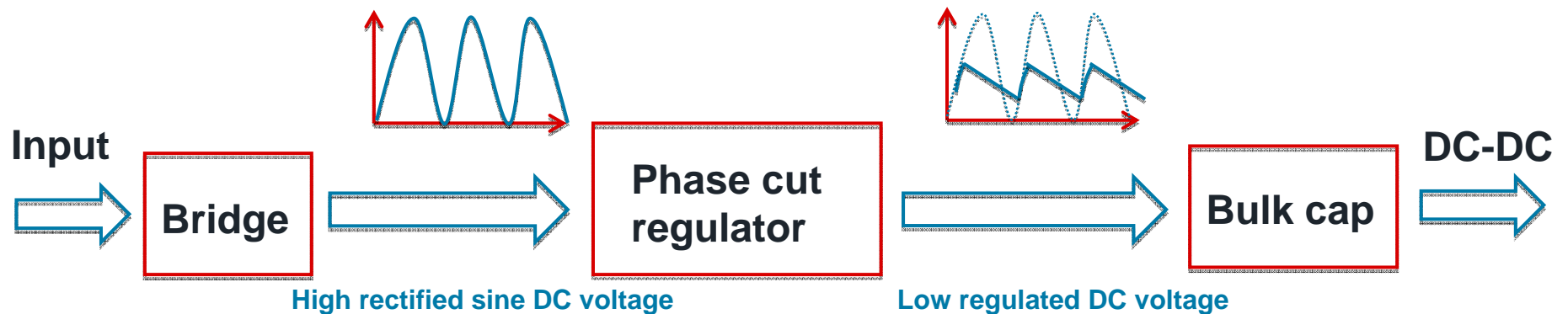

The phase cut regulator is circuit which insert between bridge and bulk-cap, which working in switching mode, it can regulate the high sine DC voltage from bridge to a low peak voltage DC voltage for bulk-cap.



Phase Cut Regulator Working Time Diagram

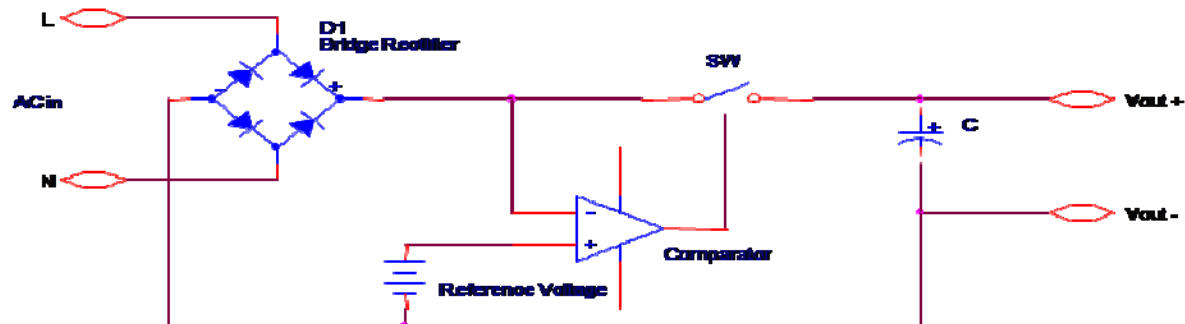


As right pictures shown :

T1: SW on, bulk-cap not charge
($V_{line_on} < V_{ref} \ \& \ V_{line} < V_{bulk}$)

T2: SW on, bulk-cap charge
($V_{line_on} < V_{ref} \ \& \ V_{line} > V_{bulk}$)

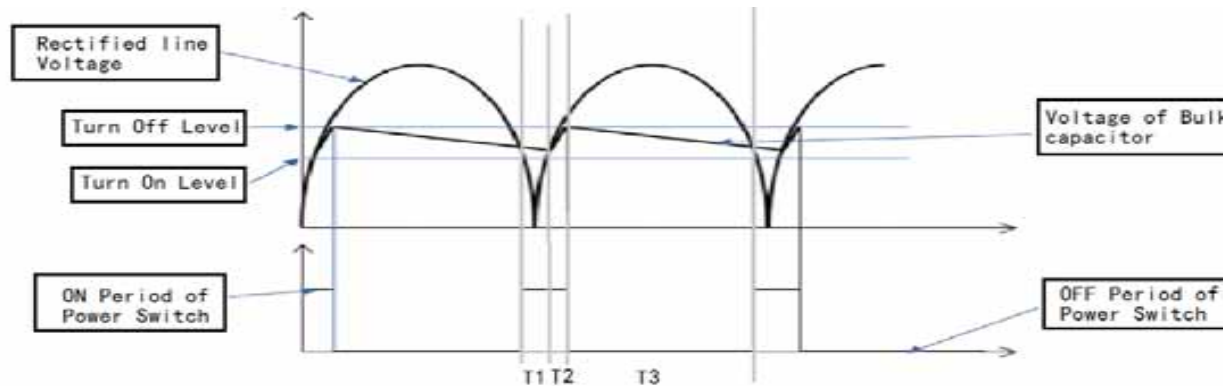T3: SW off, bulk-cap discharge
($V_{line_on} > V_{ref}$)





Three Solution's Efficiency Comparison

Solutions	Vin/Vout	Devices	Freq.	Balance Circuits	60Vac	220Vac	380Vac	600Vac
Cascode FET	45Vac- 600Vac/15V/670mA	FSL137MRIN+FQP4N90C	67KHz	Yes	63.41%	78.26%	76.92%	71.16%
ESBC™	45Vac- 600Vac/15V/670mA	FJBE2160D+FDC653N	67KHz	Yes	67.21%	79.56%	76.15%	65.68%
Pre-regulator	45Vac- 600Vac/15V/670mA	FSL136+HGTD1N120	67KHz	No	77.84%	78.54%	75.32%	66.49%




The Benefit of Phase Cut Regulator

- Just need one Bulk-cap ,save cost and space.
- Don't need Bulk-cap balance circuit , more simple.
- Could use a low breakdown voltage MOSFET , more cheaper.
- As input DC voltage go down, the DC-DC part could set more big duty cycle, the efficiency will increase.



Schematic

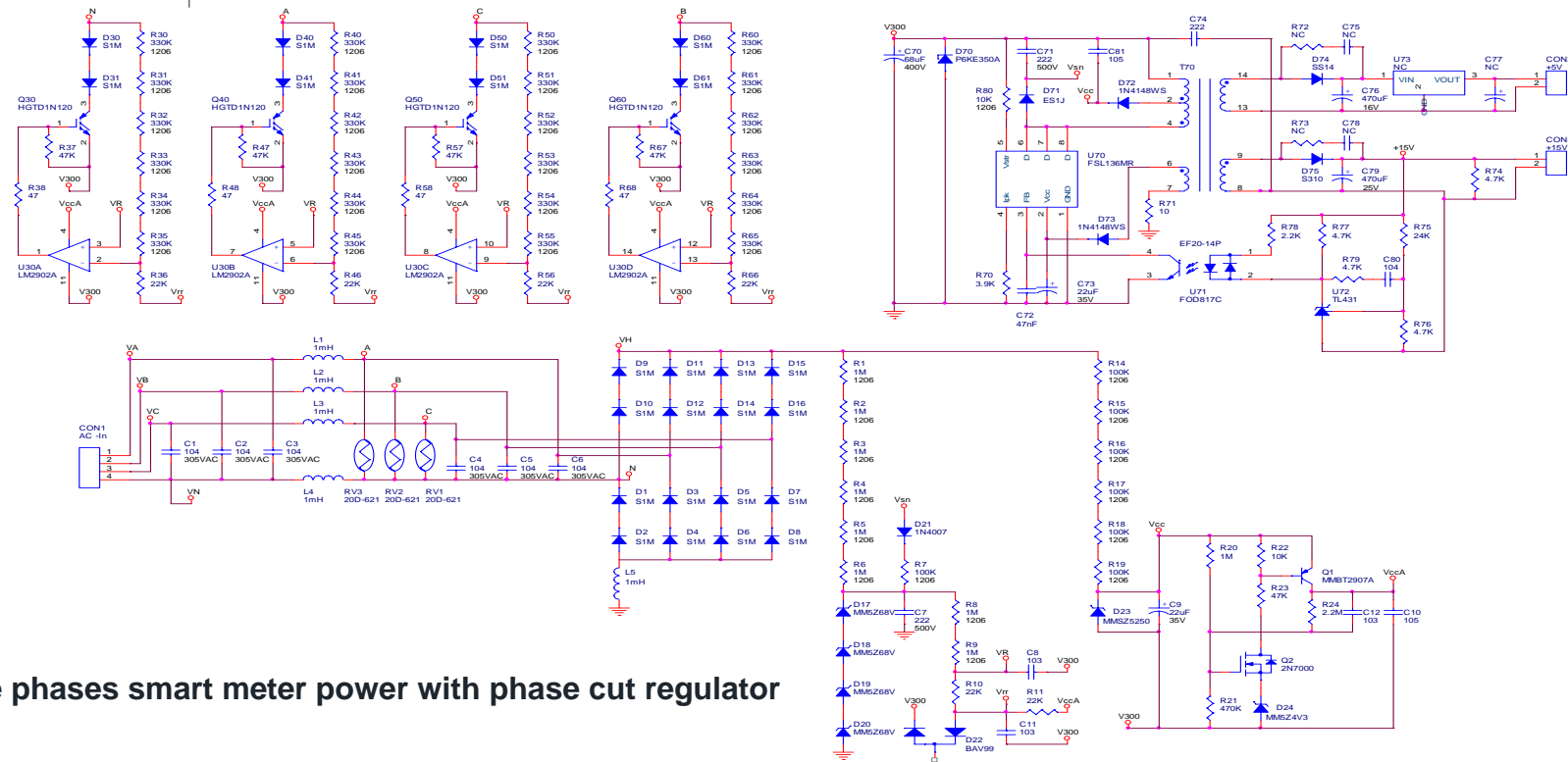

Three phases smart meter power with phase cut regulator



THANK YOU

仙童™